

Pre-Lab 5: Operational Amplifiers Part 3


ECEN 325 - 511

TA: Zhiyong Zhang

Due Date: October 12, 2021

Calculations

Lossy Integrator

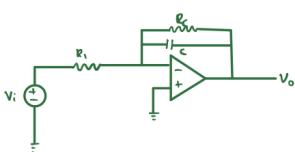


We have $R_1 = 22k\Omega$, $C = 220nF$, $\frac{V_o(s)}{V_i(s)} = 22$

$$V_o(t) = V_c(0) + C \cdot v_c(t) - V_c(0) e^{-t/\tau}$$

$\tau \rightarrow$ constant time

$v_c(t) = \text{voltage across capacitor}$

To get thevenin voltage across C we have

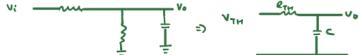

Voltage across R_2 will be V_{TH} and $R_{TH} = R_1 || R_2$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_i = 0$$

$$\frac{V_c(t)}{V_c(0)} = \frac{V_o(t)}{V_{TH}} = e^{-t/\tau}$$

$$\text{we have } \tau = R_{TH} C = \frac{R_1 R_2 C}{R_1 + R_2} = 0$$

$$i) \boxed{V_o(t) = \frac{R_2}{R_1 + R_2} e^{-t(\frac{R_1 + R_2}{R_1 + R_2} C)}$$

$$2) \text{ Voltage Gain} \quad \frac{V_o(s)}{V_i(s)} = \frac{-R_2 || Z_L}{R_1} \\ = \frac{R_2 Z_L}{R_1 + Z_L} \frac{1}{R_1} \\ = \frac{-R_2}{R_1} \left(\frac{1}{R_1 s + 1} \right) \\ \boxed{\frac{V_o(s)}{V_i(s)} = \frac{-R_2}{R_1}} \quad \text{Final gain}$$

$$\text{now } -22 = -R_2/R_1$$

$$R_2 = 22k\Omega$$

$$R_1 = 1k\Omega$$

$$\text{The } 3\text{dB frequency } = \frac{1}{\tau} = \frac{R_1 + R_2}{R_1 R_2 C}$$

$$= \frac{1k\Omega + 22k\Omega}{22k\Omega * 1k\Omega * 220nF}$$

$$= 4.75 \text{ kHz}$$

$$3) \boxed{\frac{V_o(s)}{V_i(s)} = \frac{-R_2}{R_1} \left(\frac{1}{R_2 s C + 1} \right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-22k\Omega}{1k\Omega} \left(\frac{1}{22k\Omega s 220nF + 1} \right) \\ = \frac{-22}{4.84 \times 10^{-3} s + 1} = \frac{-22}{206.61} = \frac{-22}{1 + \frac{s}{206.61}}$$



$$\text{compare } \omega = \frac{-1j}{1 + \frac{s}{206.61}} \quad f = 206.61$$

$$\omega = 206.61$$

$$\text{phase } [\tau(s)] = -\tan^{-1} \left(\frac{s}{206.61} \right)$$

$$\lim_{s \rightarrow 0} \text{phase } [\tau(s)] = -\tan^{-1} \left(\frac{0}{206.61} \right) = 0^\circ$$

Magnitude Response

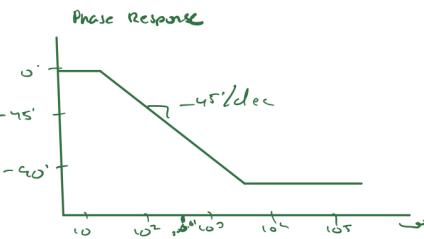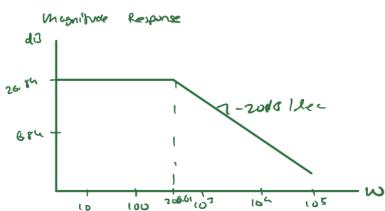

$$4) \frac{V_o(s)}{V_i(s)} = \frac{22}{1 + \frac{5}{206.61}} = \frac{22}{\sqrt{1 + \frac{\omega^2}{206.61}}} < -\tan^{-1}\left(\frac{\omega}{206.61}\right)$$

at $\omega = 2\pi 1000\text{ rad/s}$


$$= \frac{22}{\sqrt{1 + \frac{(2000\pi)^2}{(206.61)^2}}} < -\tan^{-1}\left(\frac{2000\pi}{206.61}\right) = -0.723 < -88.11$$

$$V_o = -0.723 < -88.11 \times 0.5 < 0^\circ$$

$$V_o = -3615 < -88.11$$

$V_o(t) = -0.3615 \sin(2\pi 1000t - 88.11)$

5) Given square wave

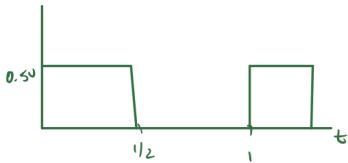

From previous circuit


$V_{TH} = \frac{R_L}{R_1 + R_2} V_i = \frac{22}{1 + 22} V_i = 0.95 V_i$

$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 0.95 \text{ k}\Omega$


$$T = R_{TH} C = 0.95 \times 220 \text{nF} = 210.43 \text{ }\mu\text{s}$$

$$\text{since } V_i = 0.5V \quad V_{TH} = 0.9 \times 0.5V$$
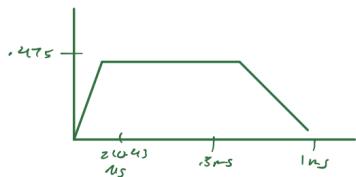
$$V_o(t) = (V_{TH} - V_{TH} e^{-t/T}) = 0.475V - 0.475V e^{-t/210.43} = 0.475V - 0.475V e^{-t/210.43} = 0.475V - 0.475V e^{-t/210.43}$$



Pseudo Differentiator

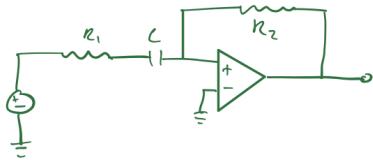

we have
gain = -22
 $R_1 = 1k\Omega$
 $C = 33nF$

$$V_i \xrightarrow{R_1} \int \xrightarrow{C} V_o$$

As $t \rightarrow \infty$ $V_o = 0$ $\tau = (R_1 + R_2)C$

$$V_o(t) = V_i(t) \left(\frac{R_2}{R_1 + R_2} \right) \text{ for } t=0 \text{ to } \tau$$

$$V_o(t) = V_i(t) \times \frac{R_2}{R_1 + R_2} \text{ for } t=0 \text{ to } \tau$$

$$V_o(t) = V_i(t) \times \frac{R_2}{R_1 + R_2} e^{-t/\tau}$$

$$\boxed{V_o(t) = V_i(t) \frac{R_2}{R_1 + R_2} e^{-t/(R_1 + R_2)C}}$$

for high freq $\omega \rightarrow \infty$ $i.e. \frac{1}{sC} = 0$ and C acts as a short circuit

$$\frac{V_o}{V_i} = A_v = -\frac{R_2}{R_1} = -22, \quad R_2 = 22 \times 1k = 22k\Omega$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \frac{R_2}{R_2 + (R_1 + 1/C)s} = \frac{\frac{R_2}{C}}{1 + (R_1 + R_2)s/C}$$

$$= \frac{7.26 \times 10^{-4} s}{1 + 7.59 \times 10^{-4} s} = 7.26 \times 10^{-4} \frac{s}{1 + \frac{s}{7.59 \times 10^{-4}}}$$

here the transfer function has zero at 1317.3 and pole at 0


3dB freq at 1317.3 rad/sec

$$\frac{1}{\sqrt{2}} = (R_1 + R_2)C$$

$$= (23k)(33nF) = \boxed{7.59 \times 10^{-4} \text{ Hz}}$$

$$\text{for magnitude: } \lim_{\omega \rightarrow 0} \left| \frac{V_o(s)}{V_i(s)} \right| = -20 \log (7.26 \times 10^{-4}) \\ = \underline{-62.78 \text{ dB}}$$
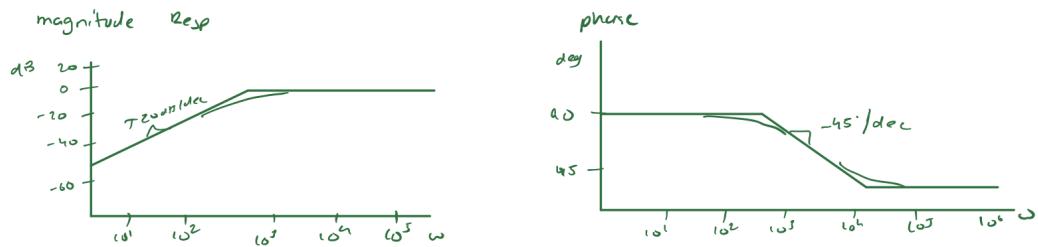
$$\text{for phase: } \lim_{\omega \rightarrow 0} \angle \frac{V_o(s)}{V_i(s)} = \tan^{-1}\left(\frac{0}{\infty}\right) - \tan^{-1}\left(\frac{0}{1317.3}\right) = 90^\circ$$



4) $V_i = 0.1 \sin(2\pi 1000t)$
 $V_i = 0.1 \angle 0^\circ$ \rightarrow transfer func. 1317.5 Hz

$$\frac{V_o(1317.5)}{V_i(1317.5)} = \frac{7.26 \times 10^{-4} \times 2000\pi j}{(1 + 7.26 \times 10^{-4} \times 2000\pi j)}$$



$$= 0.936$$

$$\angle \frac{V_o}{V_i} = \tan^{-1}\left(\frac{7.26 \times 10^{-4} \times 2000\pi}{1}\right) - \tan^{-1}\left(\frac{7.26 \times 10^{-4} \times 2000\pi}{1}\right)$$

$$= 11.84$$

$$V_o = 0.0936 \angle 11.84$$
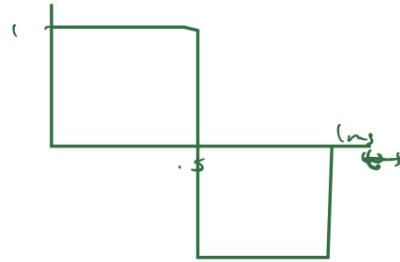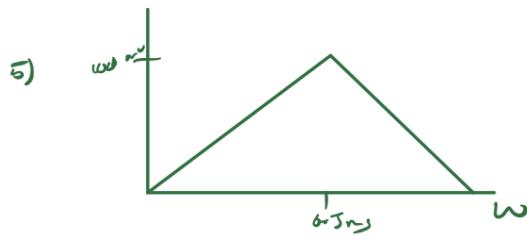
$$= \boxed{0.0936 \sin(2\pi 1000t + 11.84)}$$



Finite GBW Limitations

D) gain = 23 $R_2 = 1k\Omega$
 $\text{gain} = 1 + \frac{R_2}{R}$
 so $R_2 = 22k\Omega$

gain = 57 $57 = 1 + \frac{R_2}{1k\Omega}$
 $R_2 = 56k\Omega$


gain for P3 $83 = 1 + \frac{R_2}{1k\Omega}$
 $R_2 = 82k\Omega$

2) $\frac{V_o}{V_i} = \frac{G_o}{1 + j\omega/\omega_0}$

for 23 $\rightarrow \frac{V_o}{V_i} = \frac{23}{1 + j\frac{\omega}{\omega_0}}$

for 57 $\rightarrow \frac{V_o}{V_i} = \frac{57}{1 + j\frac{\omega}{\omega_0}}$

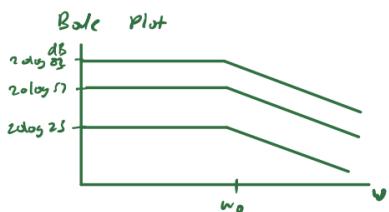
for P3 $\rightarrow \frac{V_o}{V_i} = \frac{83}{1 + j\frac{\omega}{\omega_0}}$, phase resp. = $-\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$



Slew rate limitation

from circuit $\frac{V_o}{W} = 1$

Bode Plot

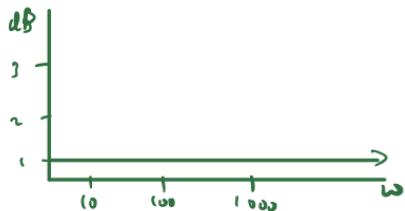

Here slew rate = $0.5V/\mu s$

$$V_{in} = 1V$$

$$V_{in} = \sin \omega t = V_0$$

$$\frac{dV_o}{dt} = \omega \cos \omega t = 0.5V/\mu s \quad (j) \quad f = \frac{0.5}{2\pi} = \frac{0.5 \times 10^6}{2\pi} = 79.58 \text{ kHz}$$

slew rate = $0.5V/\mu s$

$$V_{max} = ?$$

$$f = 75 \text{ kHz}$$


$$0.5V/\mu s = 2\pi \times 75 \text{ kHz}$$

$$V_m = \frac{0.5 \times 10^6}{2\pi \times 75 \text{ kHz}}$$


$$V_m = 1.0610$$

Simulations (on Multisim)


Lossy Integrator *Schematic*

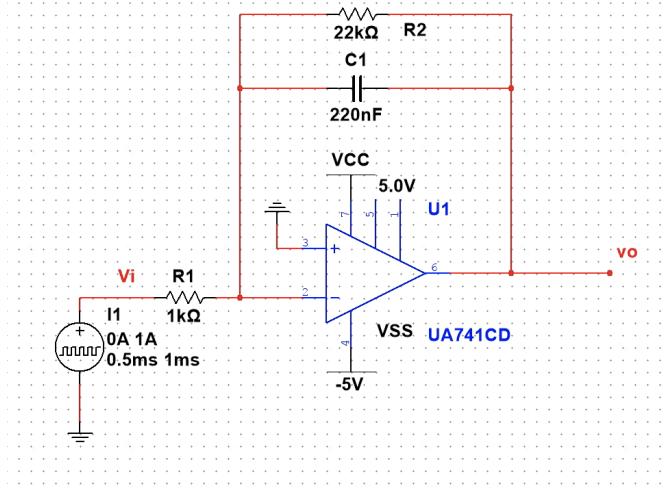


Bode

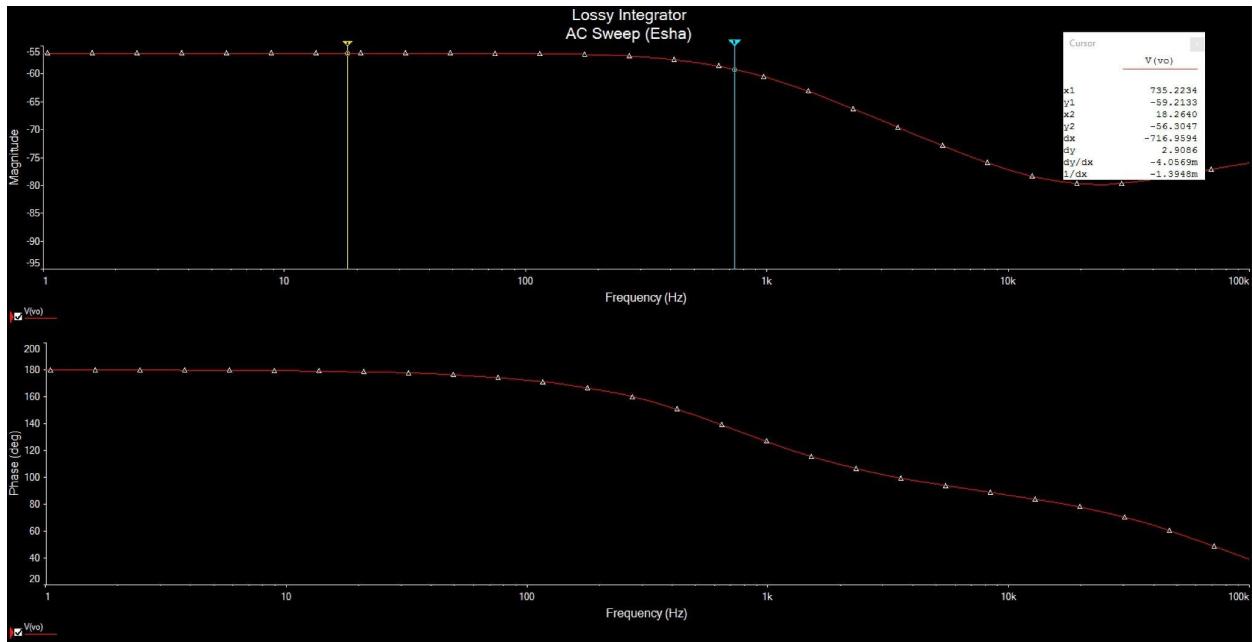

Sin Transient

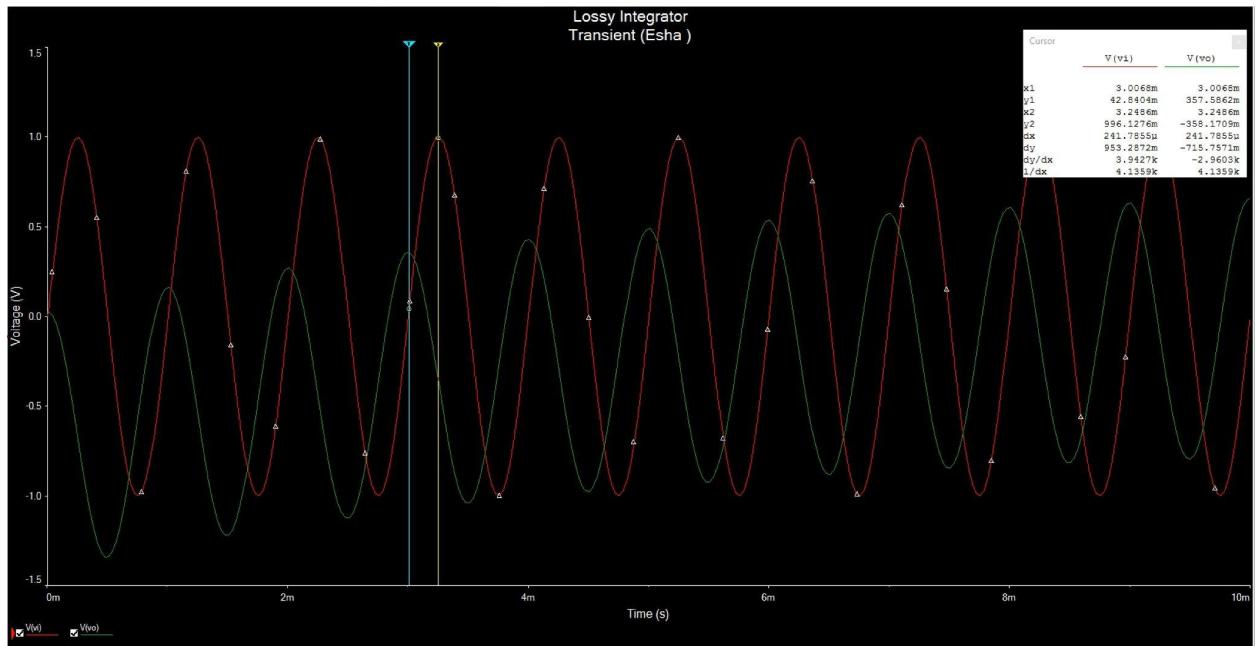


Square Transient

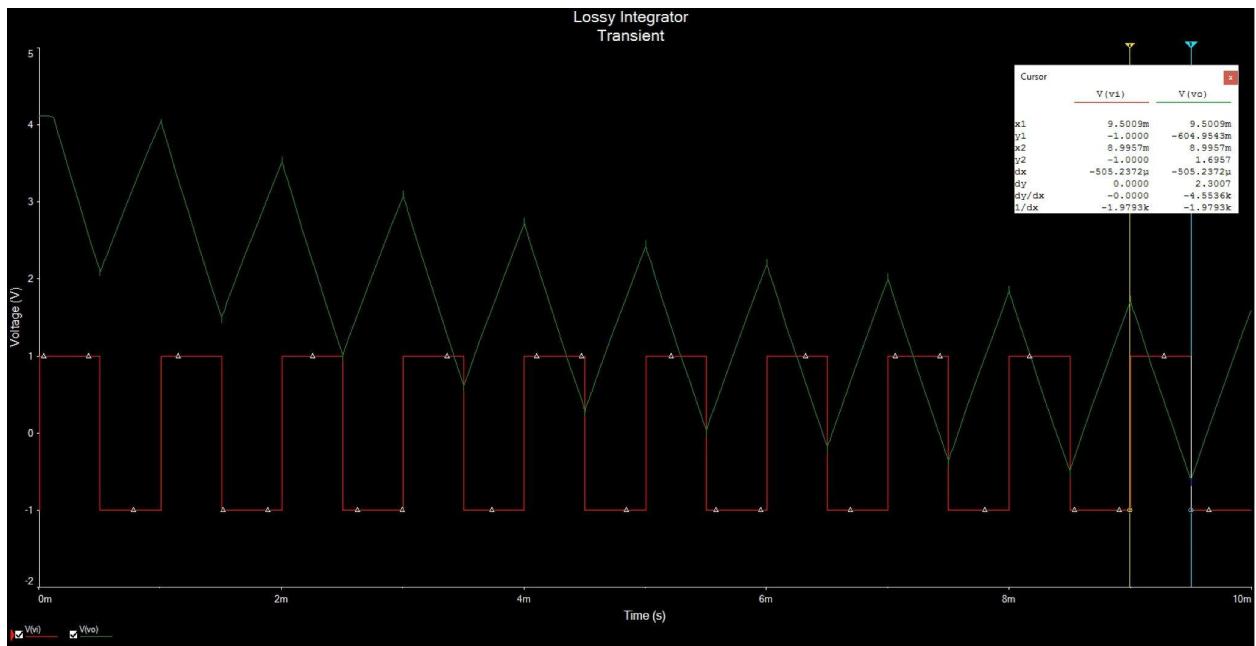


Pseudo Differentiator


Schematic

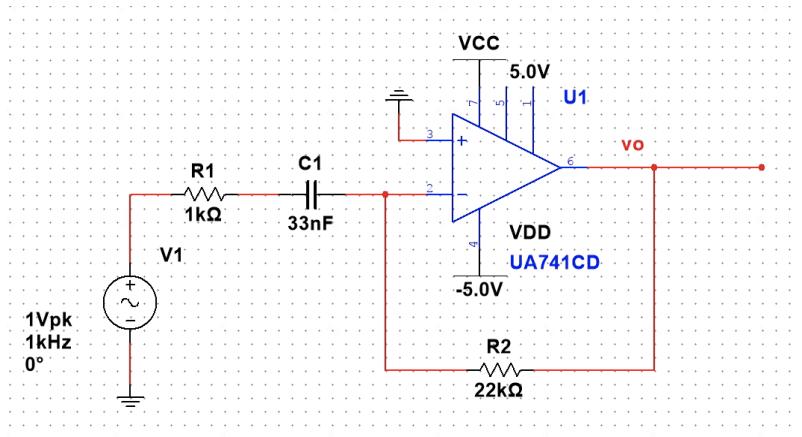


Bode

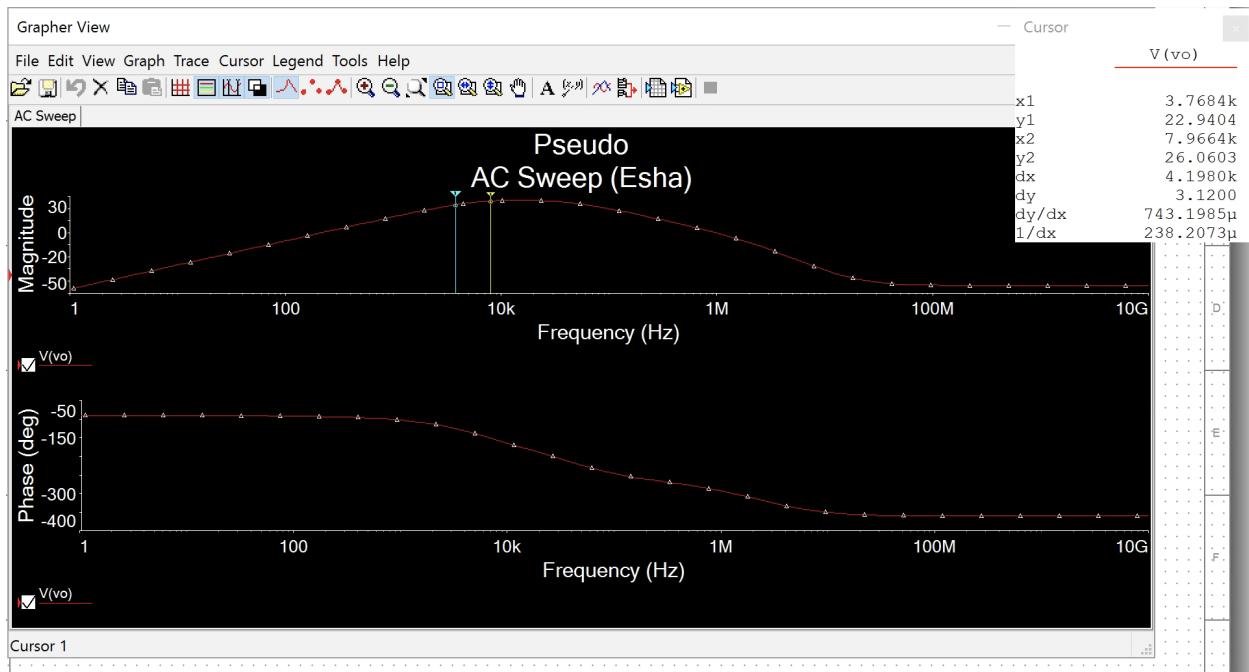

Sin Transient

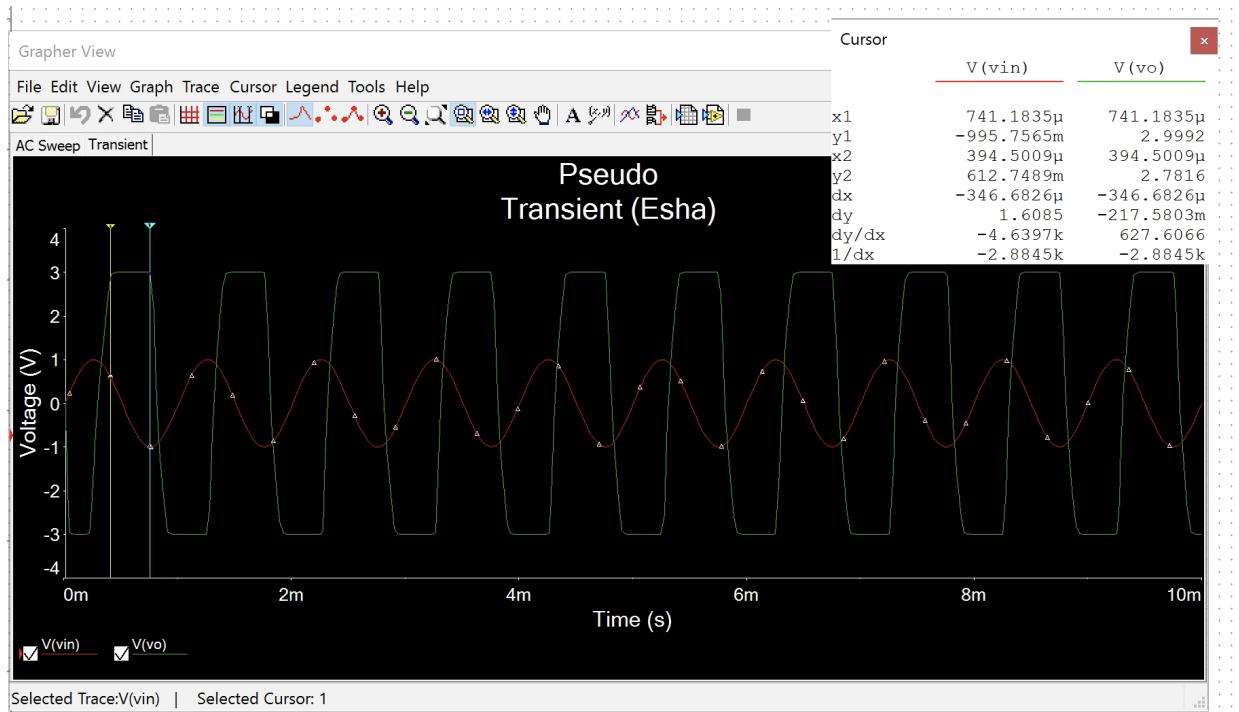


Triangle Transient

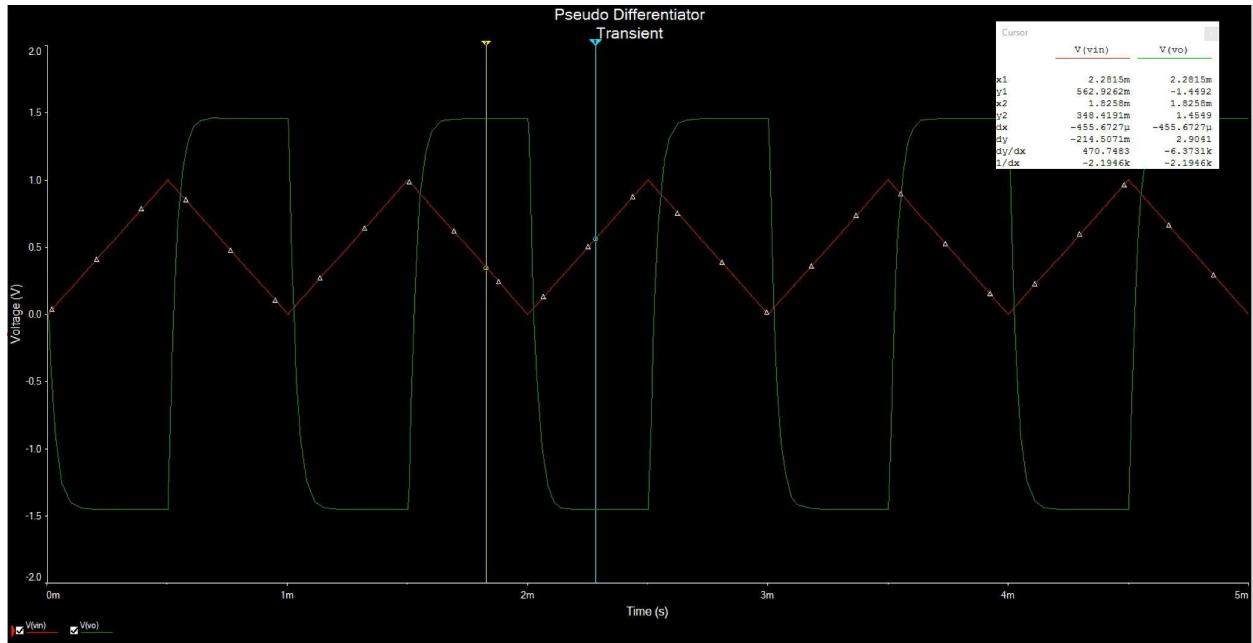


Finite GBW Limitations

Schematic

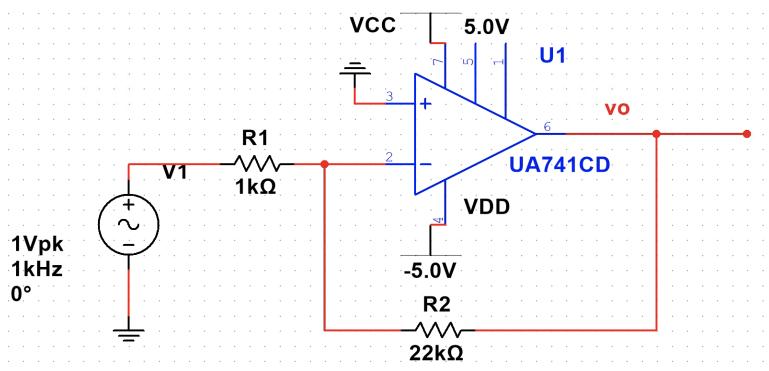


Bode

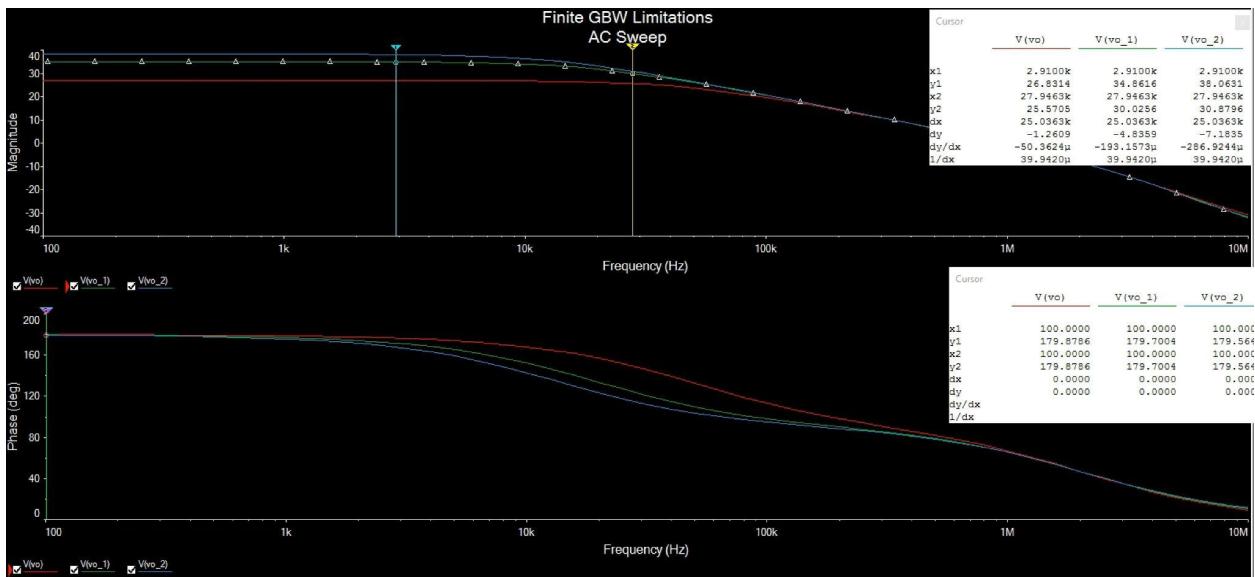


Slew Rate Limitations


Schematic

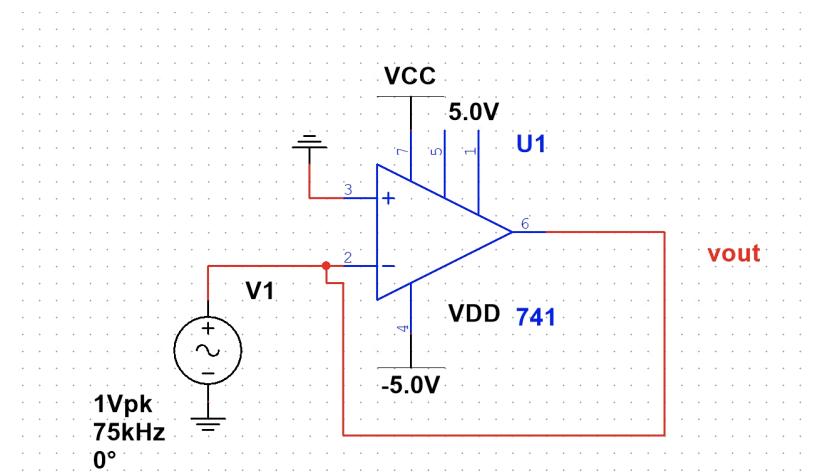


Bode

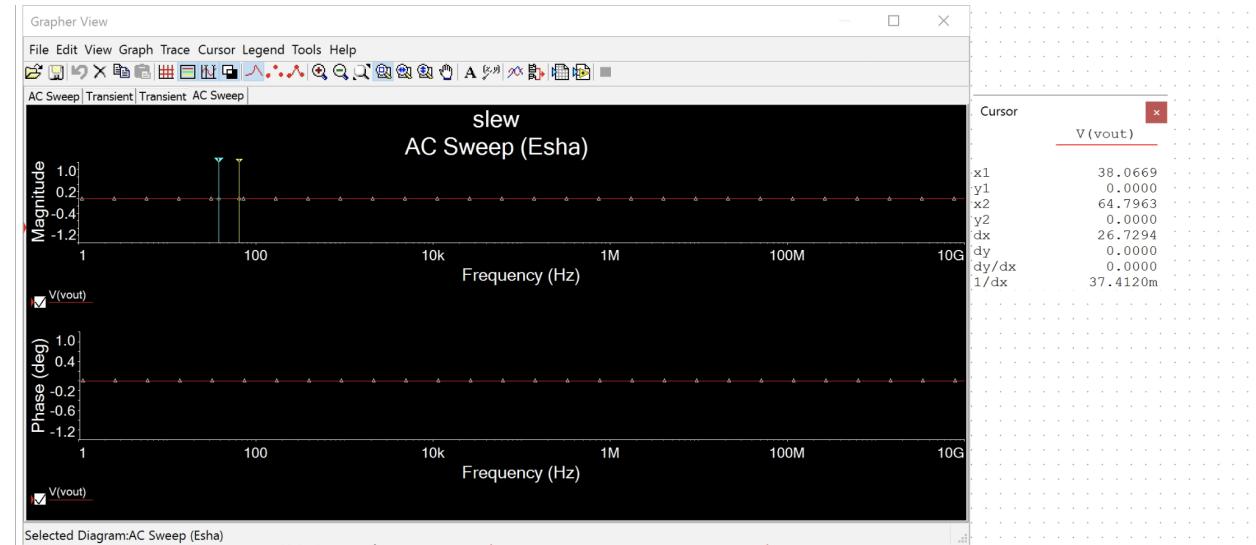


Sin Transient 75K 1V

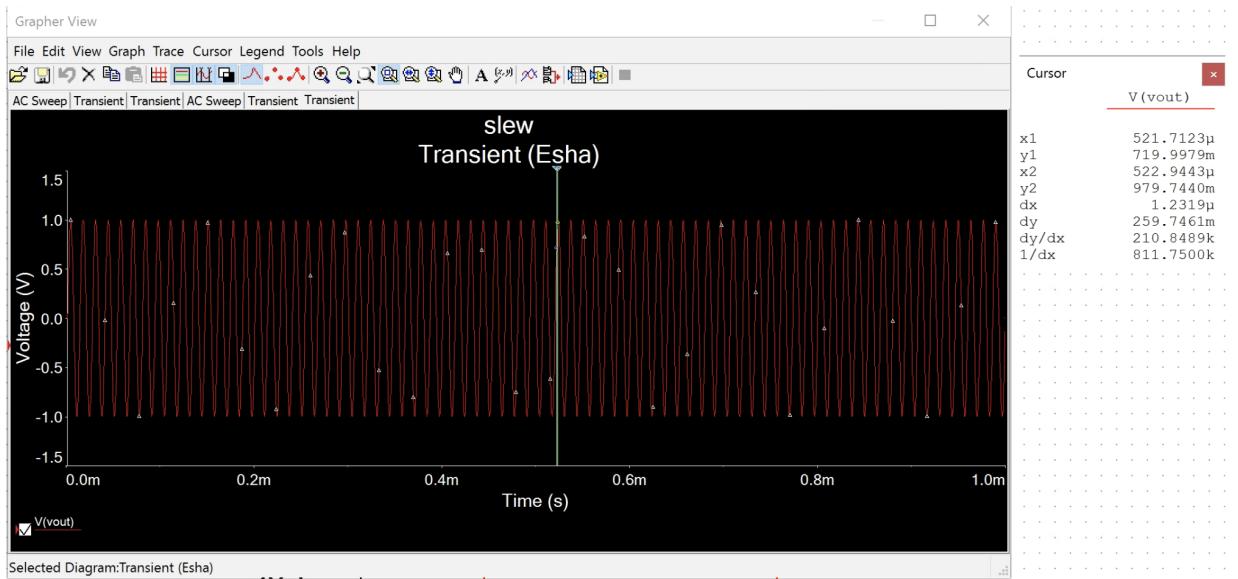


Fourier 75K 1V

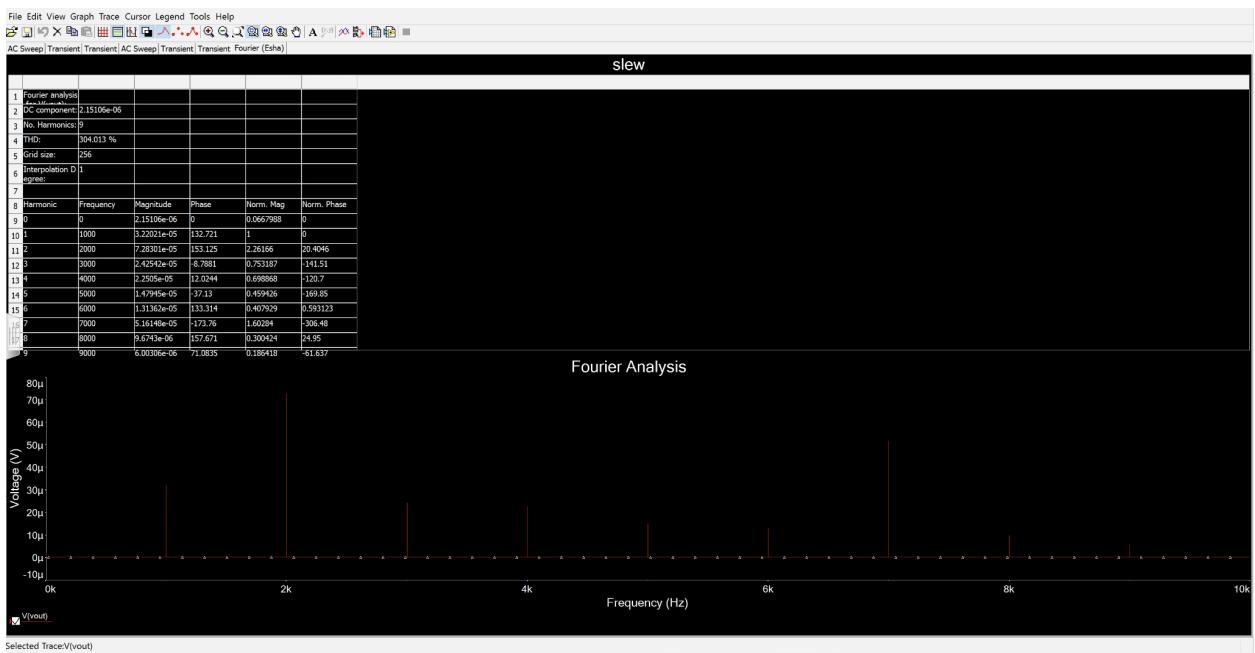


Sin Transient 75K 2V

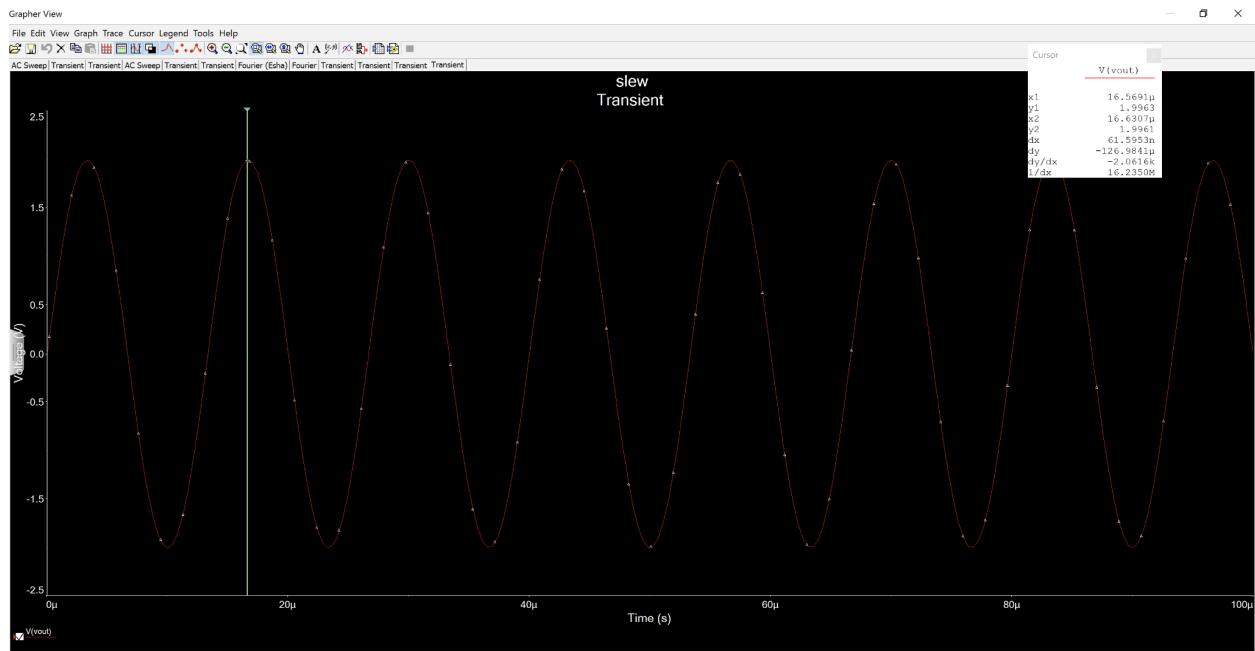

Fourier 75K 2V

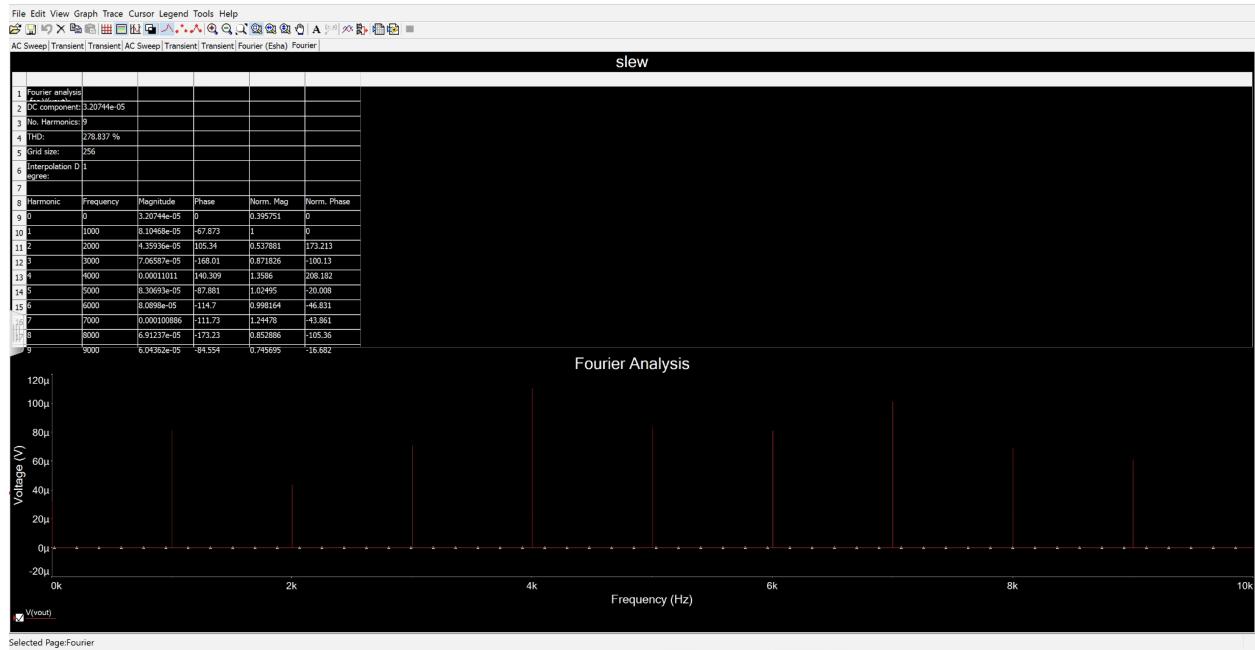

Sin Transient 150K 1V

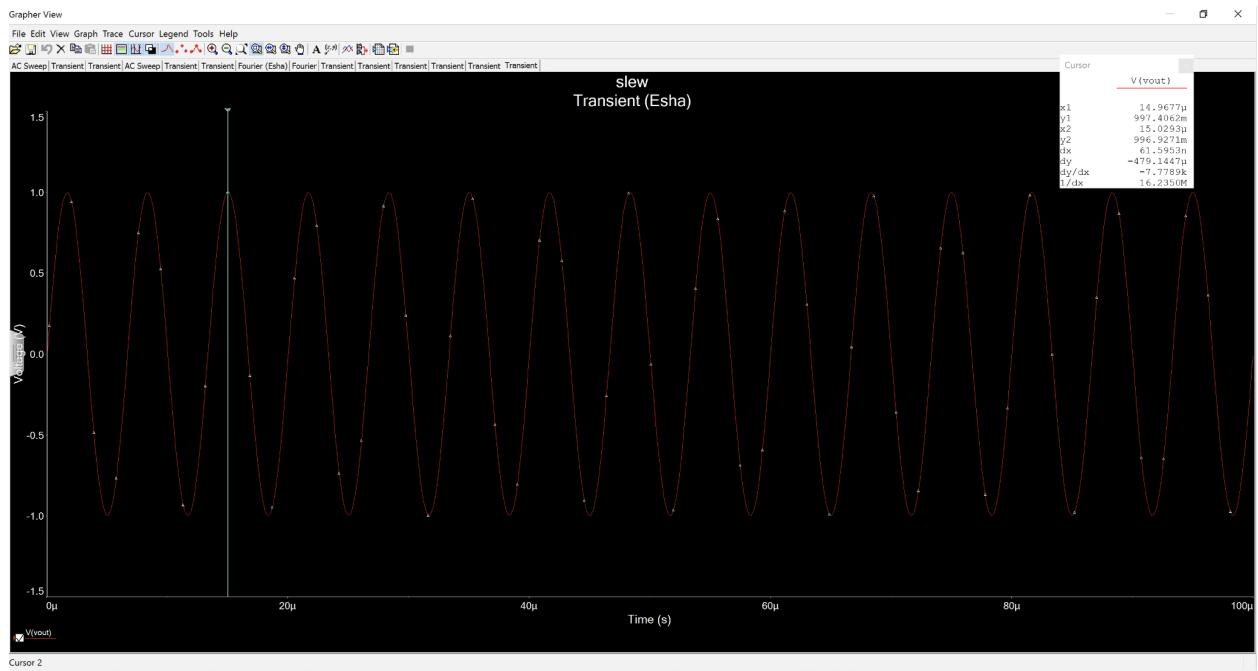

Fourier 150K 1V

