

# Lab 3: Operational Amplifiers Part 1

ECEN 325 - 511

TA: Zhiyong Zhang

Date Performed: September 28, 2021

Due Date: October 5, 2021

Purpose

The purpose of this lab was to be able to understand the fundamentals of amplifiers. There was the hands-on experience of making inverting and noninverting amplifiers, using the op-amps available.

### Calculations


1. Read the datasheet for the UA741 opamp and write down the typical values of the following parameters:

Supply Voltage	5V to 15 V -5V to -15 V
Input Offset Voltage	1mV
Voltage Gain	106dB
Power Consumption	50mW
Output Resistance	75Ω
Bandwidth	1MHz
Input Resistance	2MΩ
Input Offset Current	20nA
Slew Rate	0.5V/μs

2. Derive voltage gains

Circuit A:

**Circuit A :**

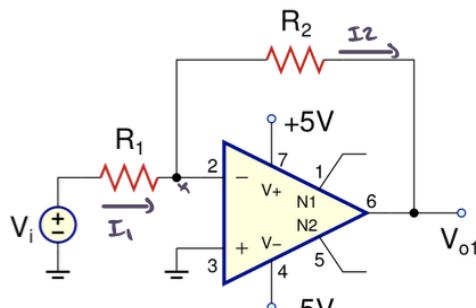


$$V_x = 0 \quad \text{and} \quad I_1 = I_2$$

$$\frac{V_i - V_x}{R_1} = \frac{V_x - V_{o1}}{R_2}$$

$$\frac{V_{o1}}{V_i} = -\frac{R_2}{R_1}$$

Circuit B:

Circuit B:

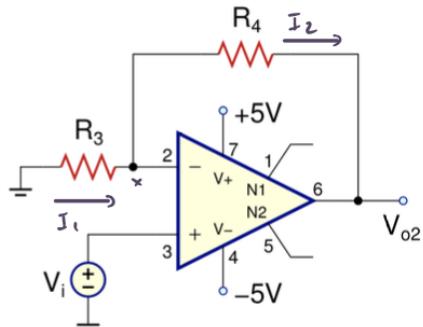

$$V_x = V_i$$

$$\text{node 1: } \frac{V_i}{R_3} + \frac{V_i + V_{o2}}{R_{f2}} = 0$$

$$V_i \left( \frac{1}{R_3 + R_{f2}} \right) - V_{o2} / R_{f2} = 0 \Rightarrow$$


$$V_i \left( \frac{1}{R_3 + R_{f2}} \right) = \frac{V_{o2}}{R_{f2}}$$

$$= \frac{V_{o2}}{V_i} = \frac{R_4}{R_3 + R_4}$$

$$\boxed{\frac{V_{o2}}{V_i} = 1 + \frac{R_4}{R_3}}$$

Circuit C:

Circuit C:

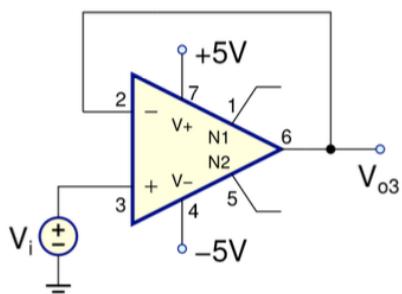

$$V_x = V_i$$

$$V_{o3} = V_i$$

$$\boxed{\frac{V_{o3}}{V_i} = 1}$$

3. If  $R_1 = R_3 = 10k\Omega$ , find  $R_2$  and  $R_4$  such that  $V_{o1}/V_i = -3$  and  $V_{o2}/V_i = 6$ .


$$3) \quad \frac{V_{o1}}{V_i} = -\frac{R_2}{R_1} = -3 = \frac{-R_2}{10k} \quad = \quad \boxed{R_2 = 30k\Omega}$$

$$\frac{V_{o2}}{V_i} = 1 + \frac{R_4}{R_3} = 6 = 1 + \frac{R_4}{10k} = \boxed{R_4 = 50k\Omega}$$


Simulations (on Multisim)

## Circuit A


### 1. Schematic

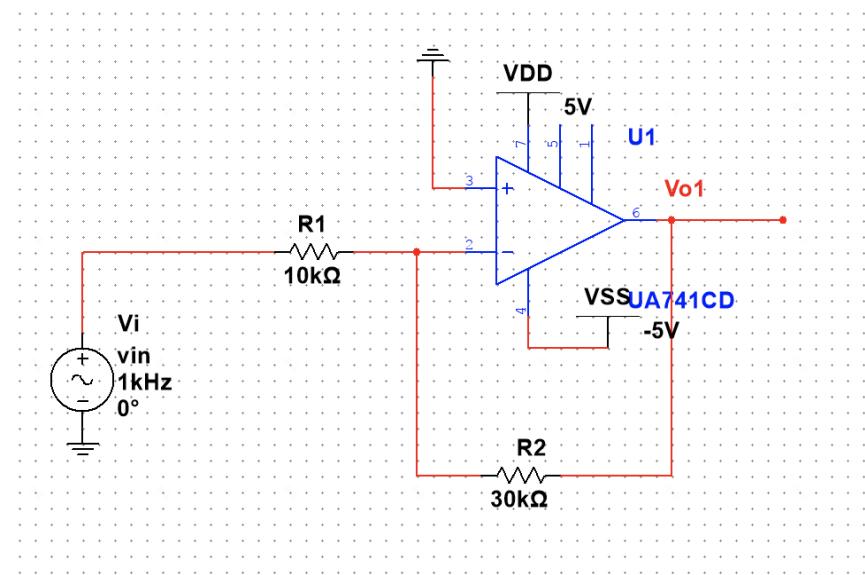


### 2. AC Sweep

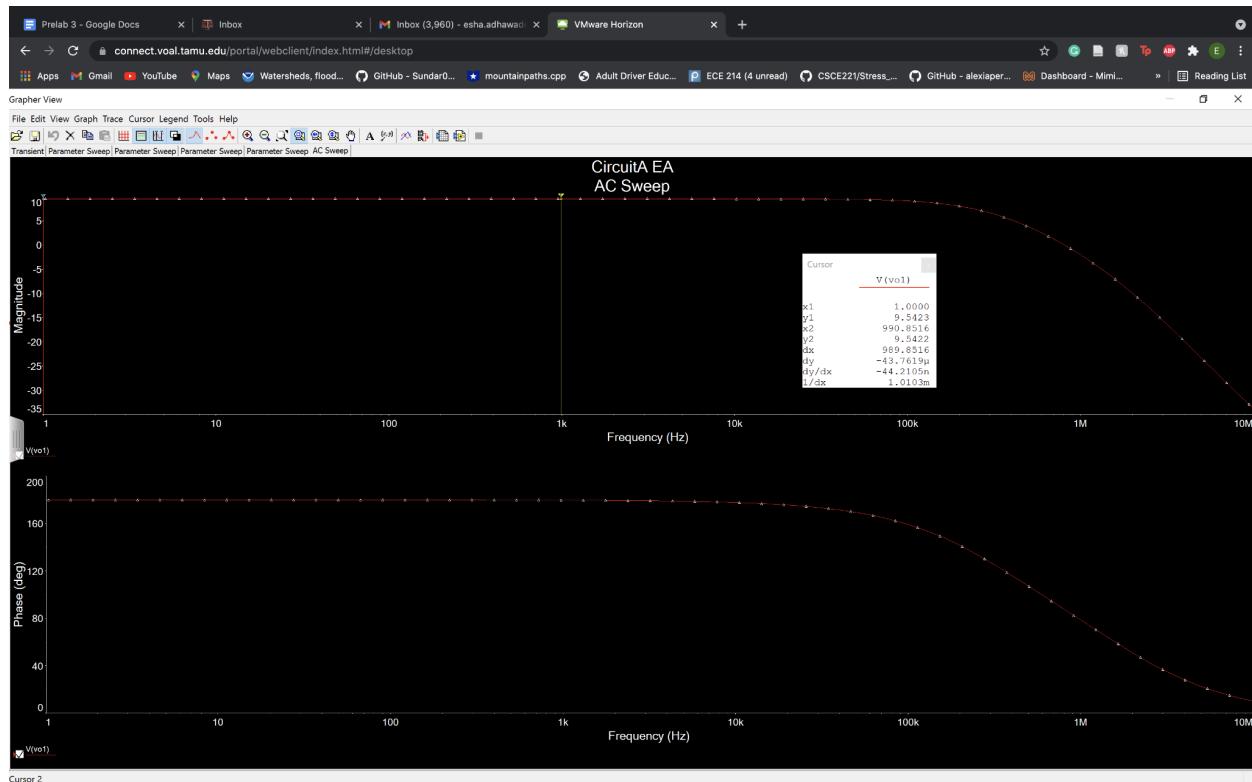


### 3. Transient

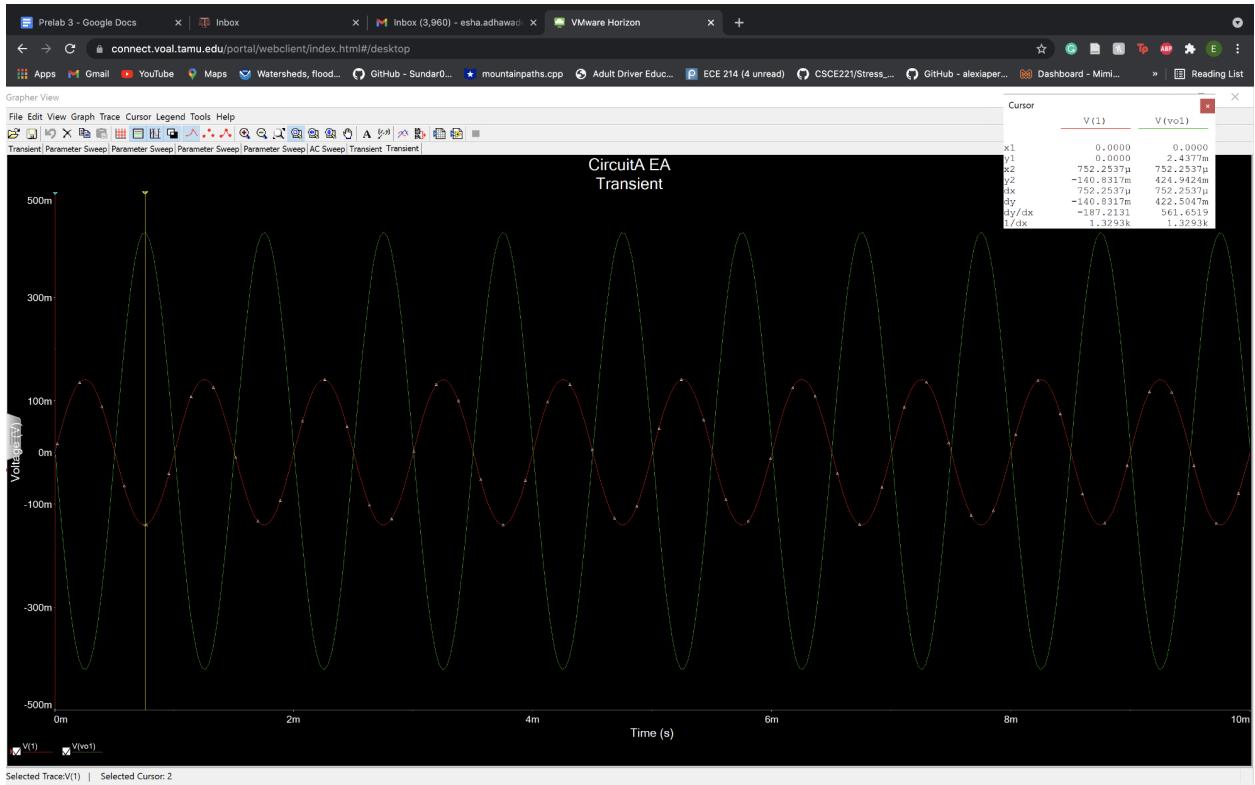

#### 4. Circuit Parameter Sweep

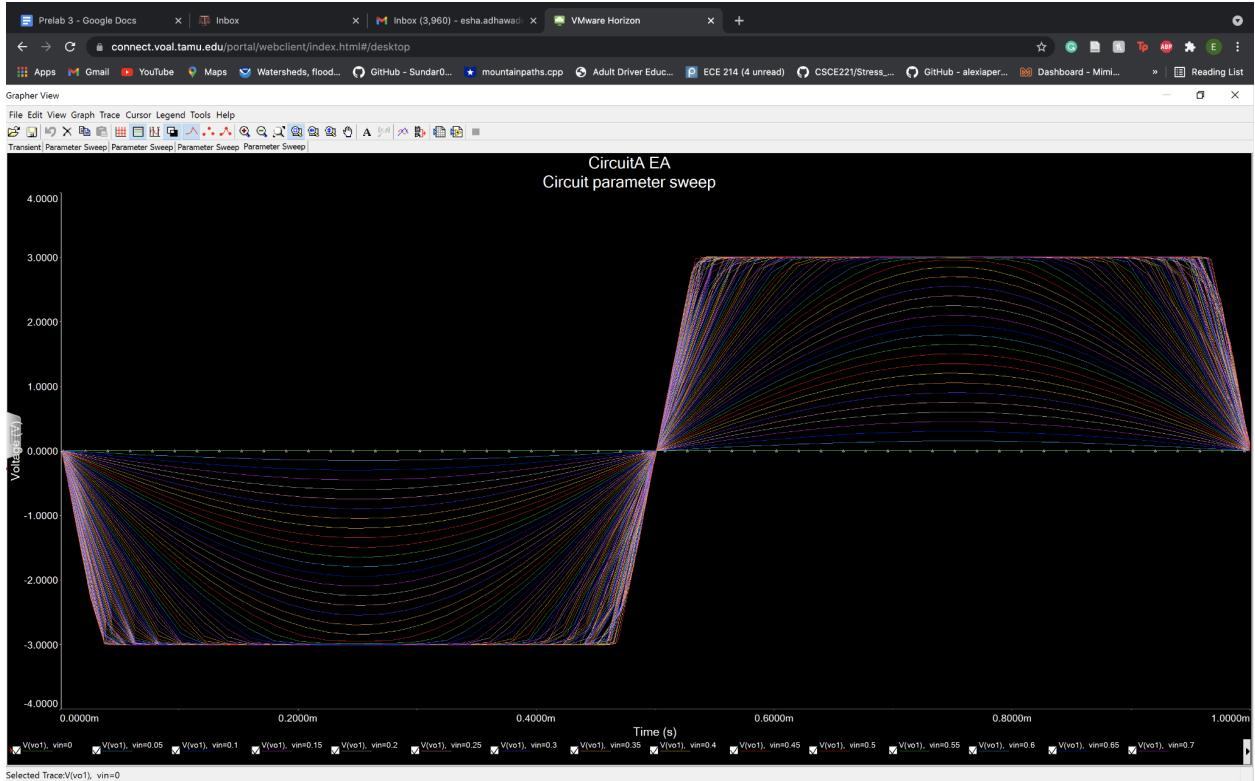


#### 5. Fourier Simulation

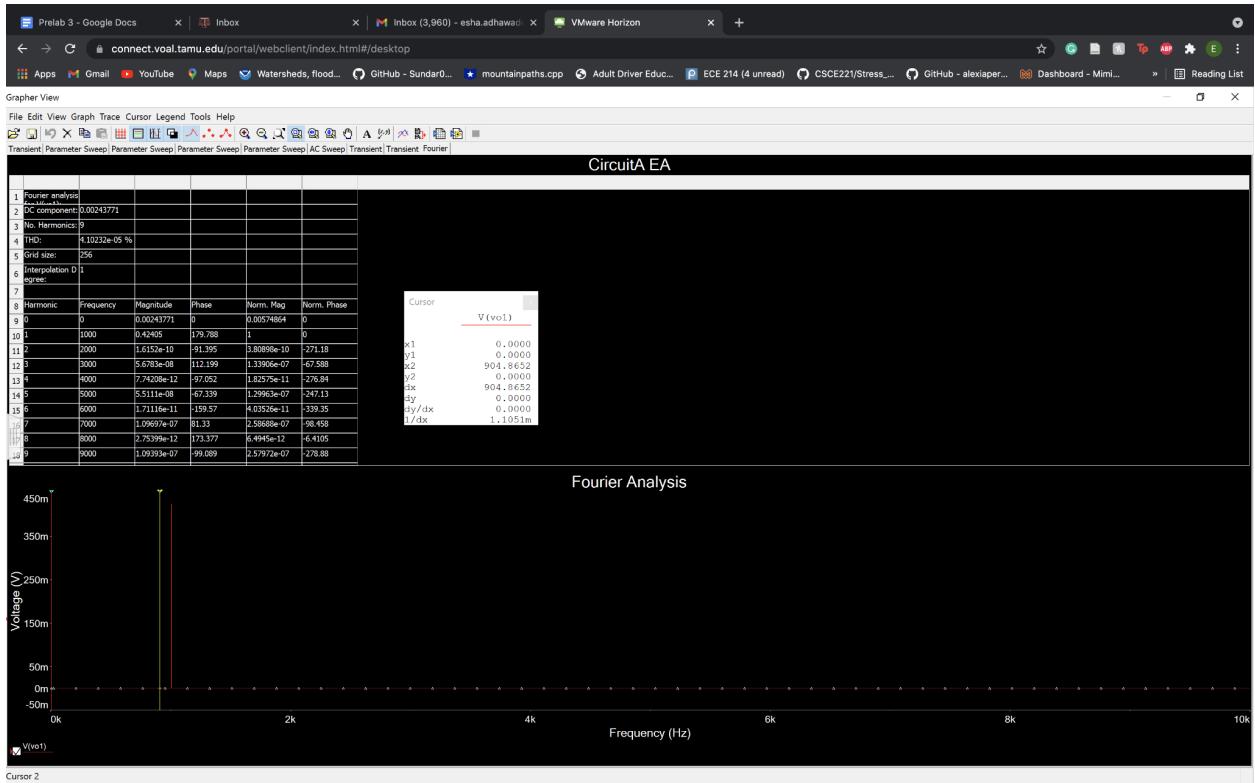


## Circuit B


### 1. Schematic

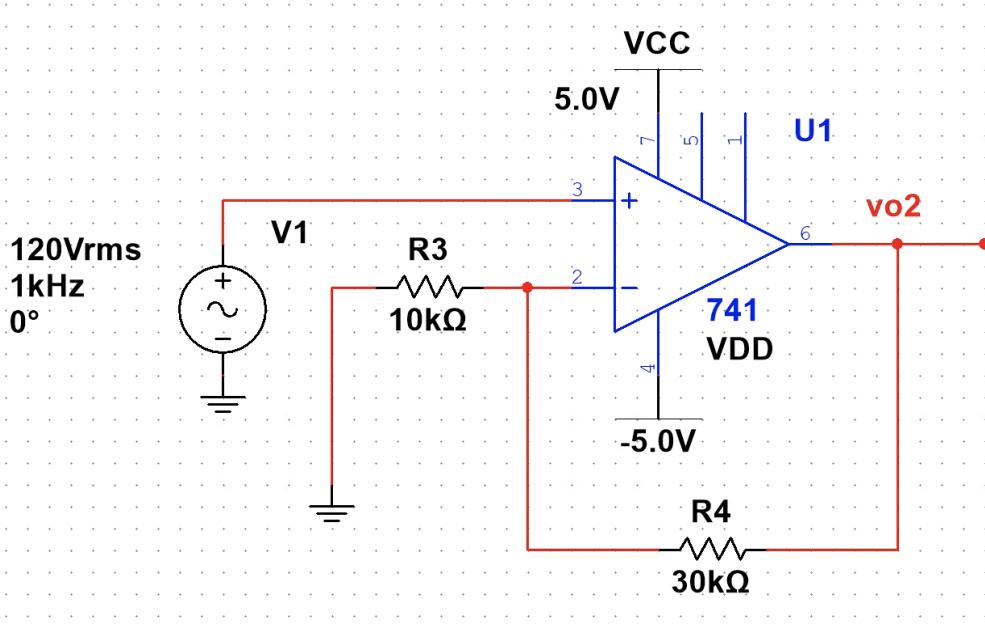


### 2. AC Sweep

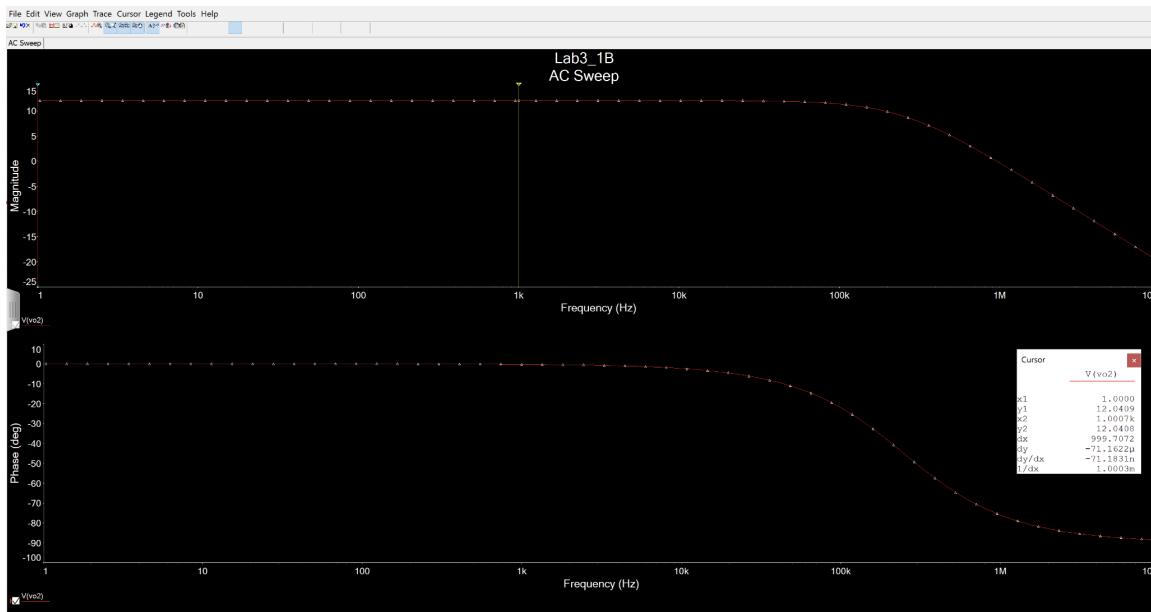


### 3. Transient

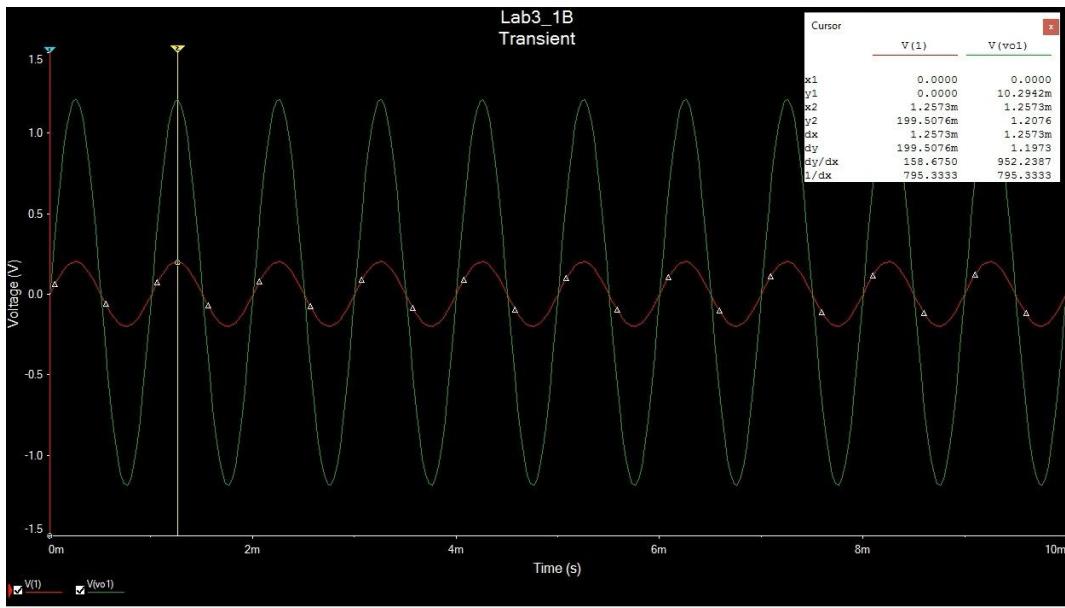

### 4. Circuit Parameter Sweep

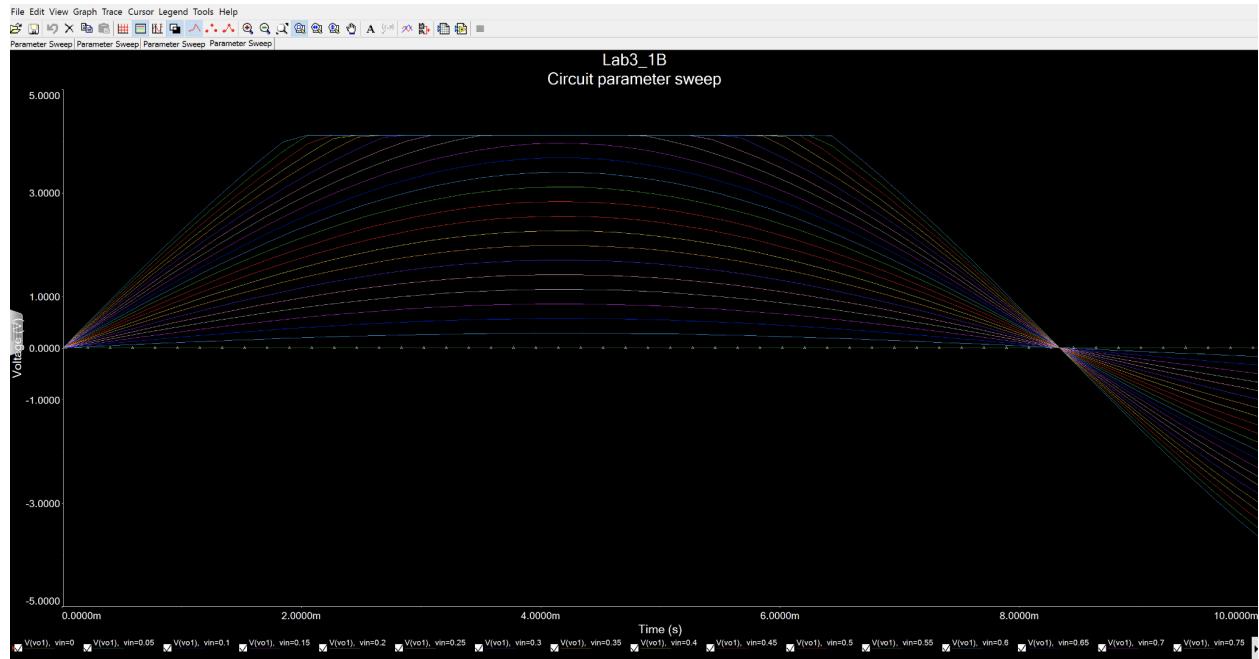


## 5. Fourier Simulation

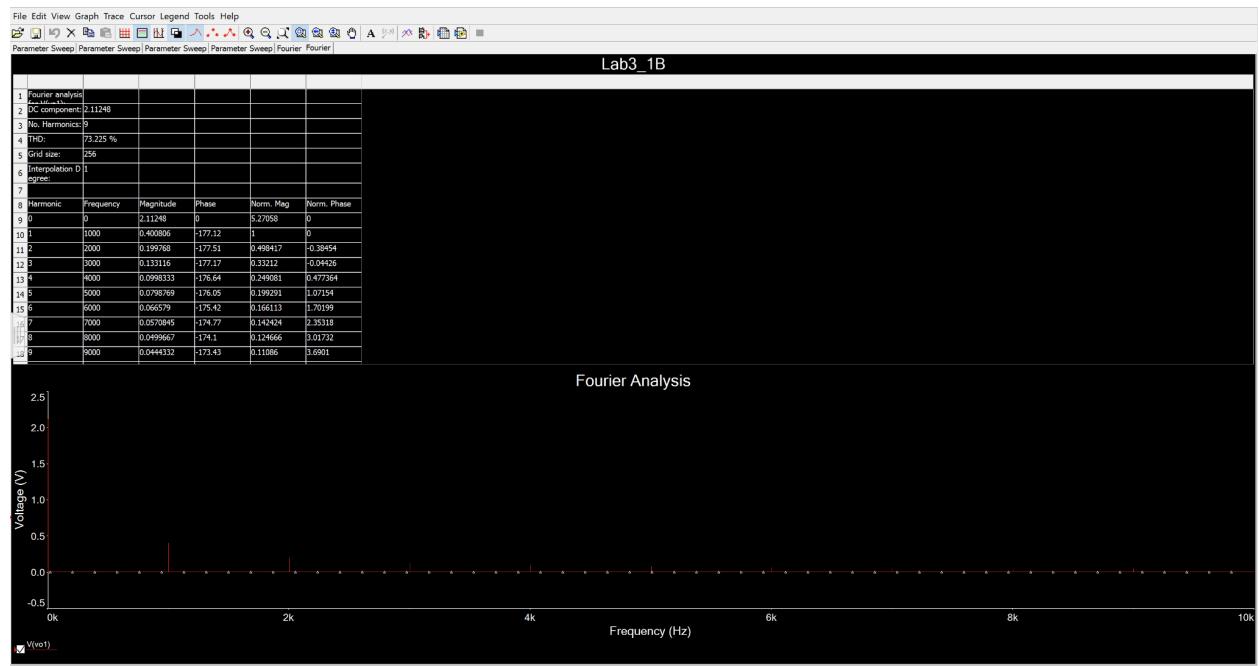


## Circuit C


## 1. Schematic

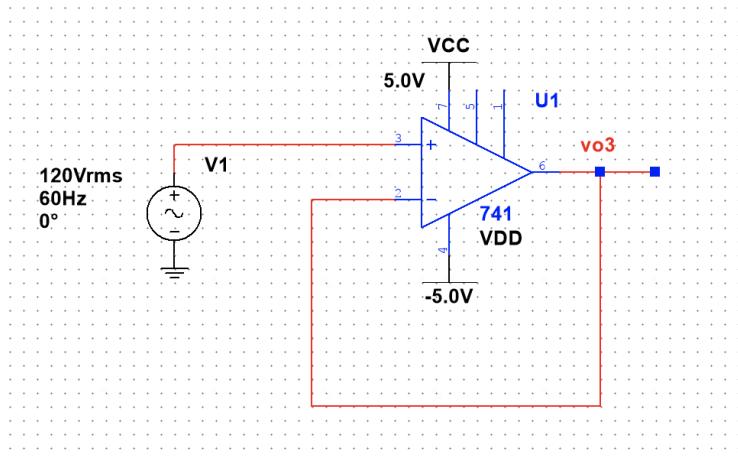


## 2. AC Sweep

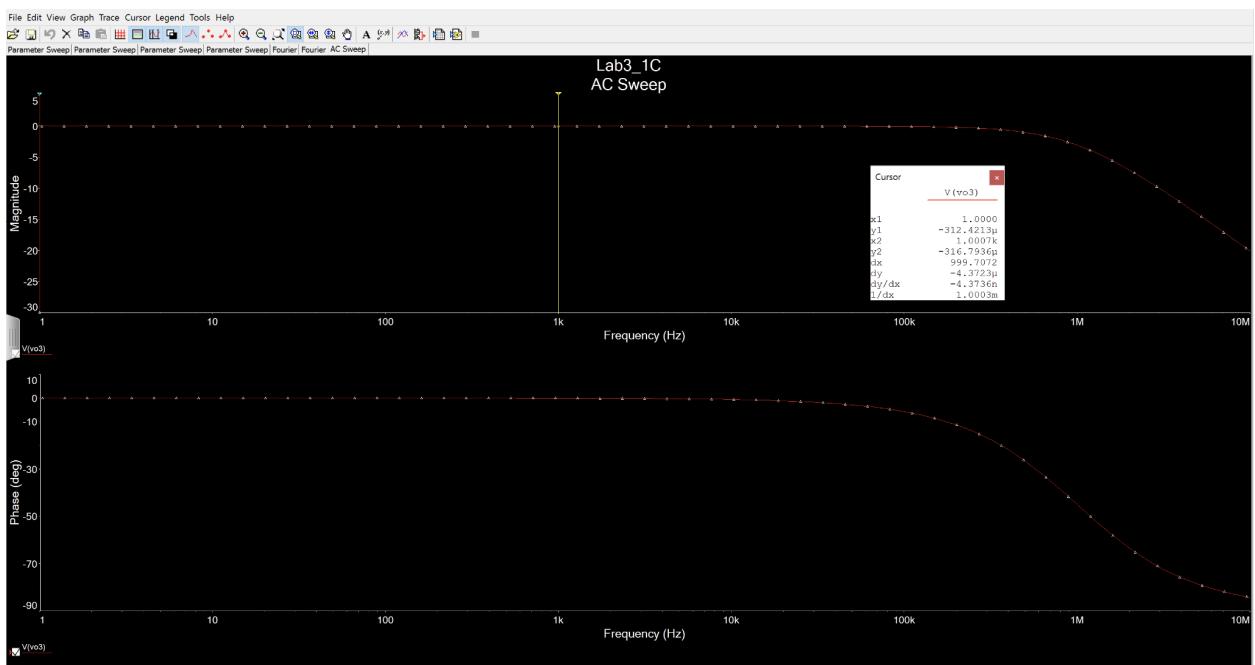


## 3. Transient

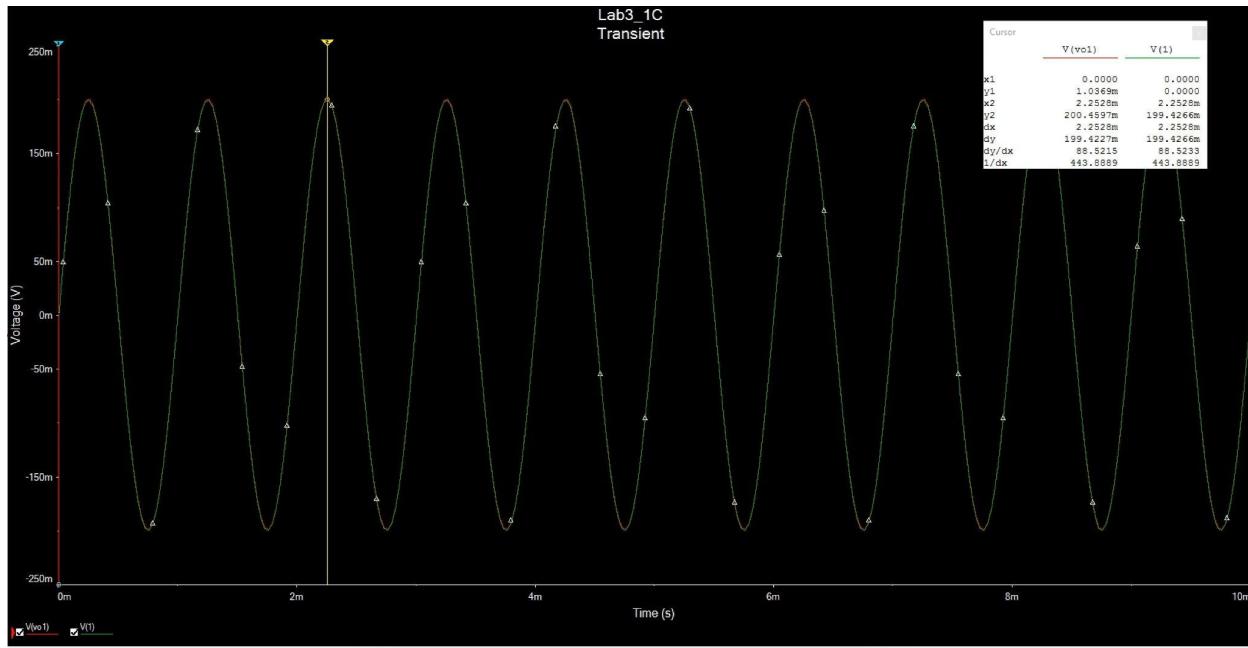

#### 4. Circuit Parameter Sweep

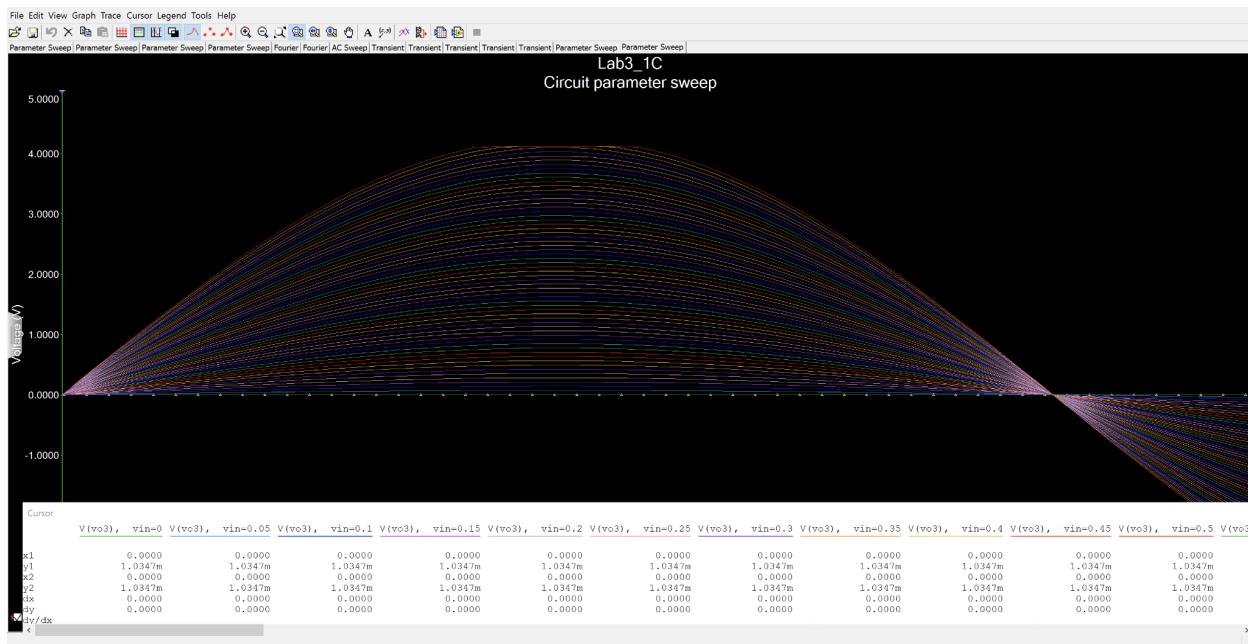

#### 5. Fourier Simulation

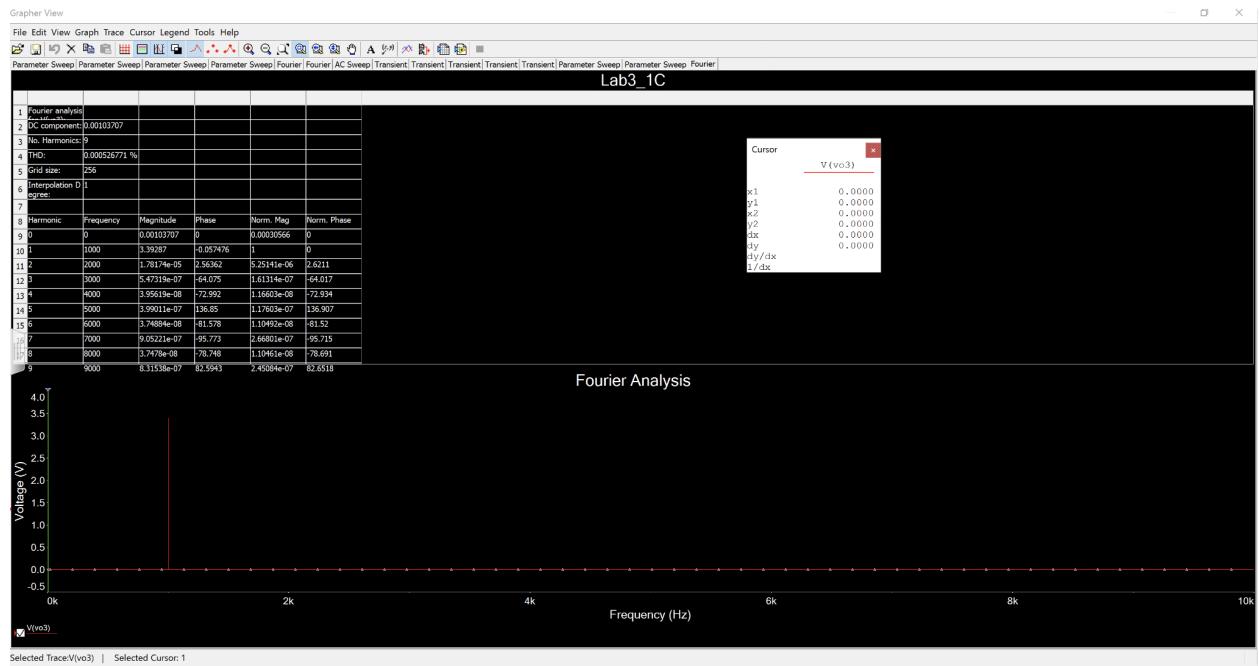

## Measured Waveforms

### Input Offset Current Measurement

In the data tables section...

### DC Offset Voltage Measurement

In the data tables section...


## Inverting and Non-inverting Configurations

## Circuit A

### Time Domain Plot




### Bode Plot

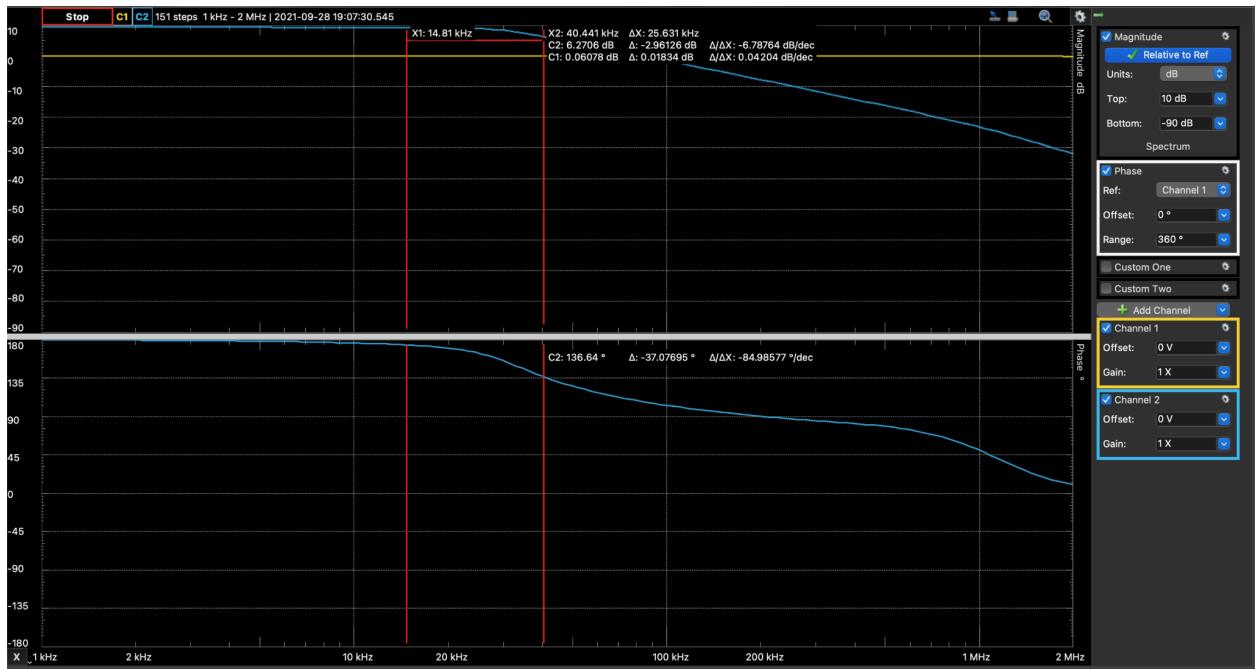


**Max: 1.23 V**

## Total Harmonic Distortion

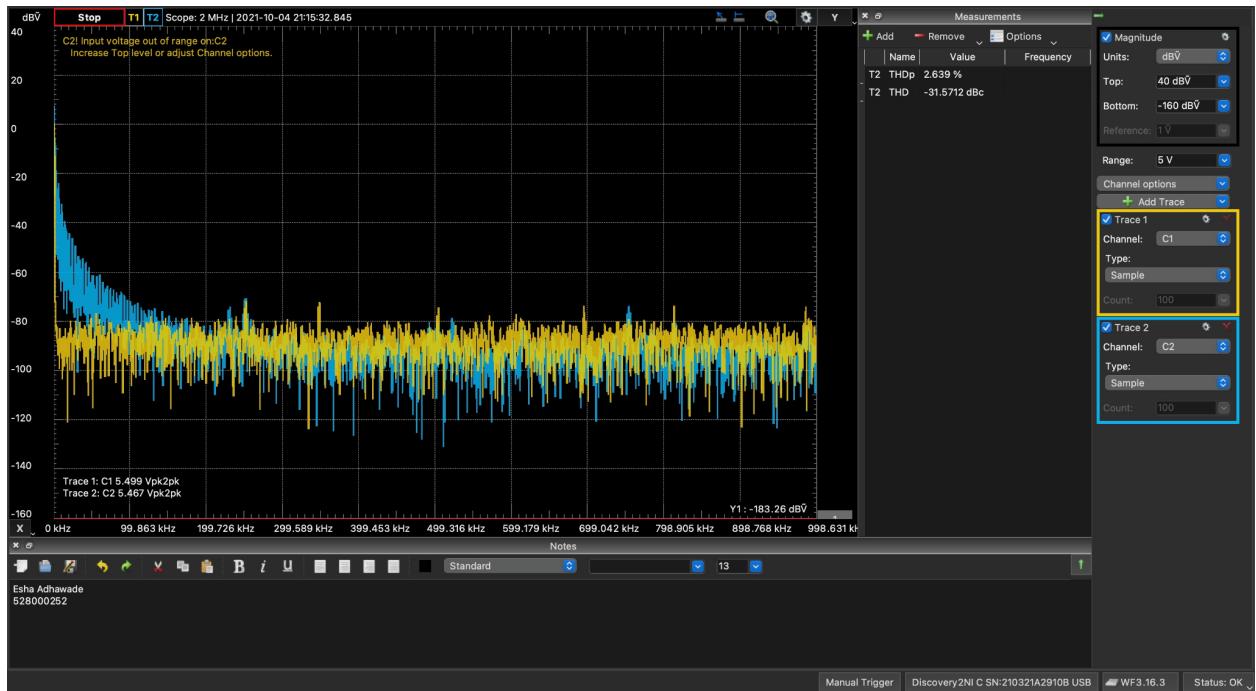


## Circuit B

### Time Domain Plot

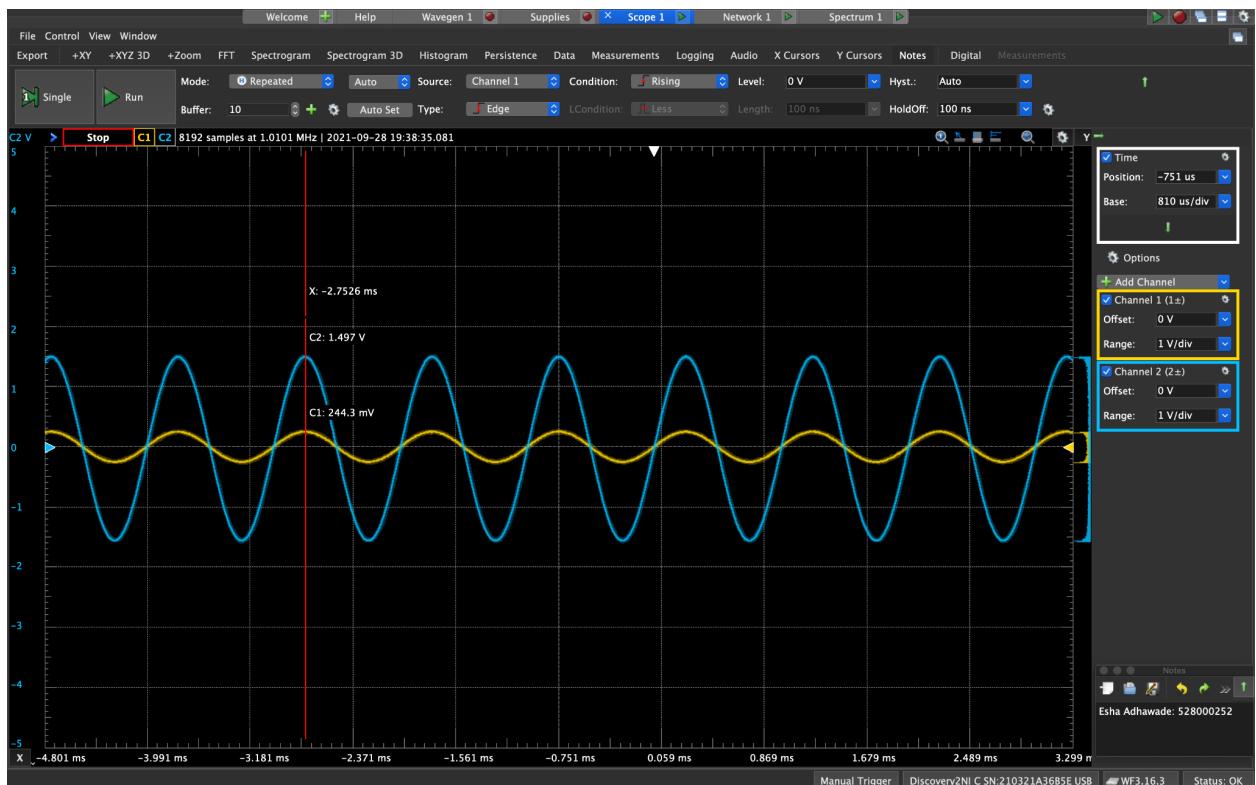


### Bode Plot

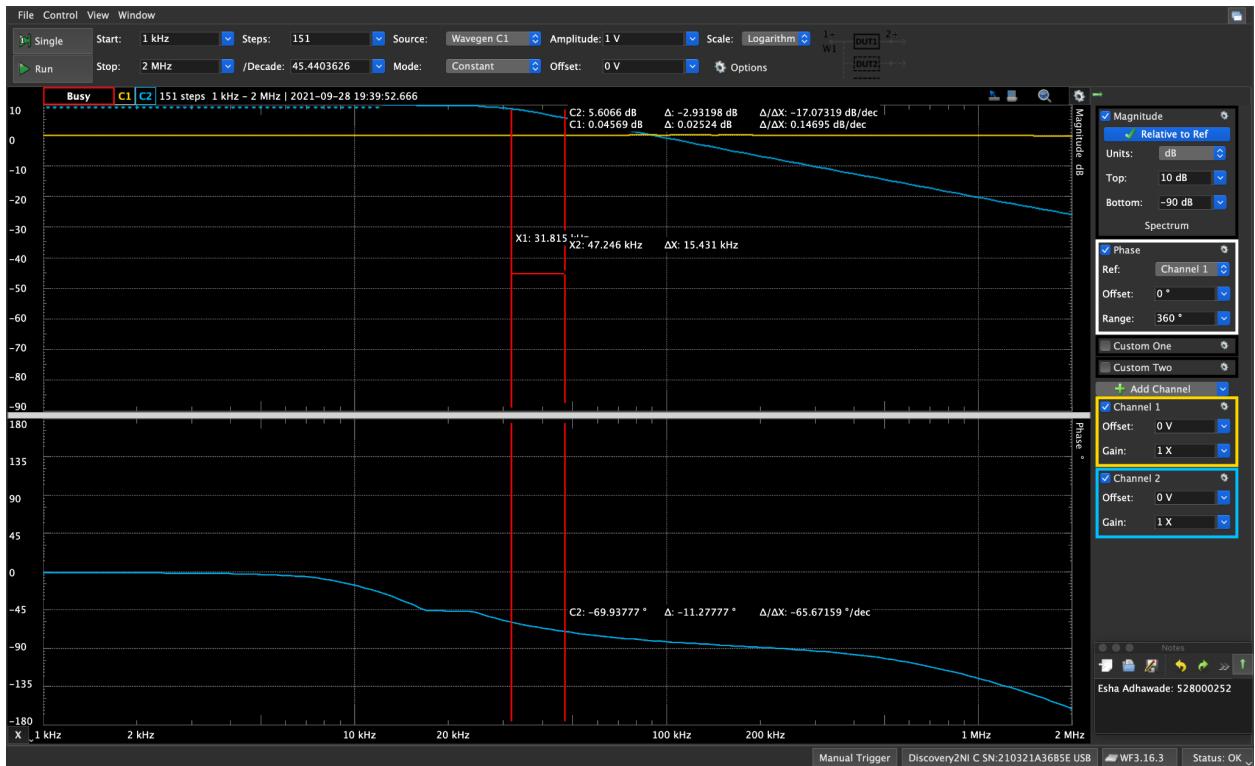

**Max: 0.61 V**

### Total Harmonic Distortion

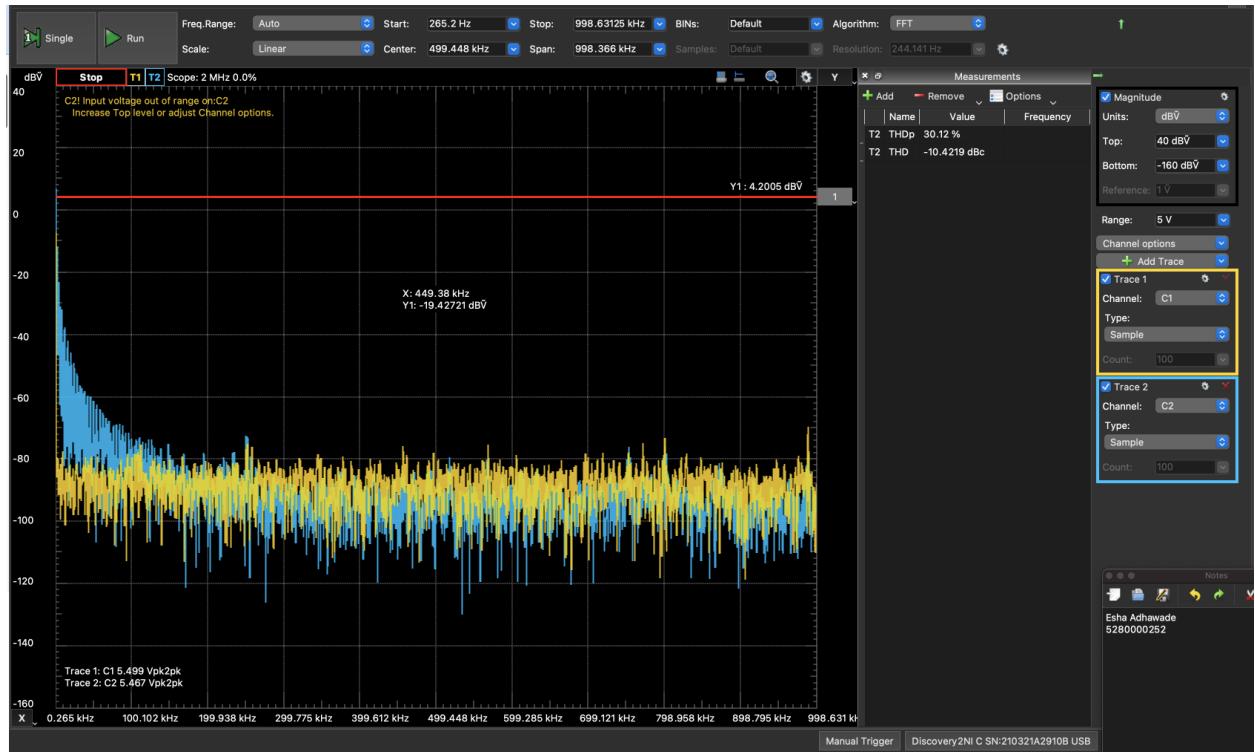


### Circuit C

## Time Domain Plot




## Bode Plot

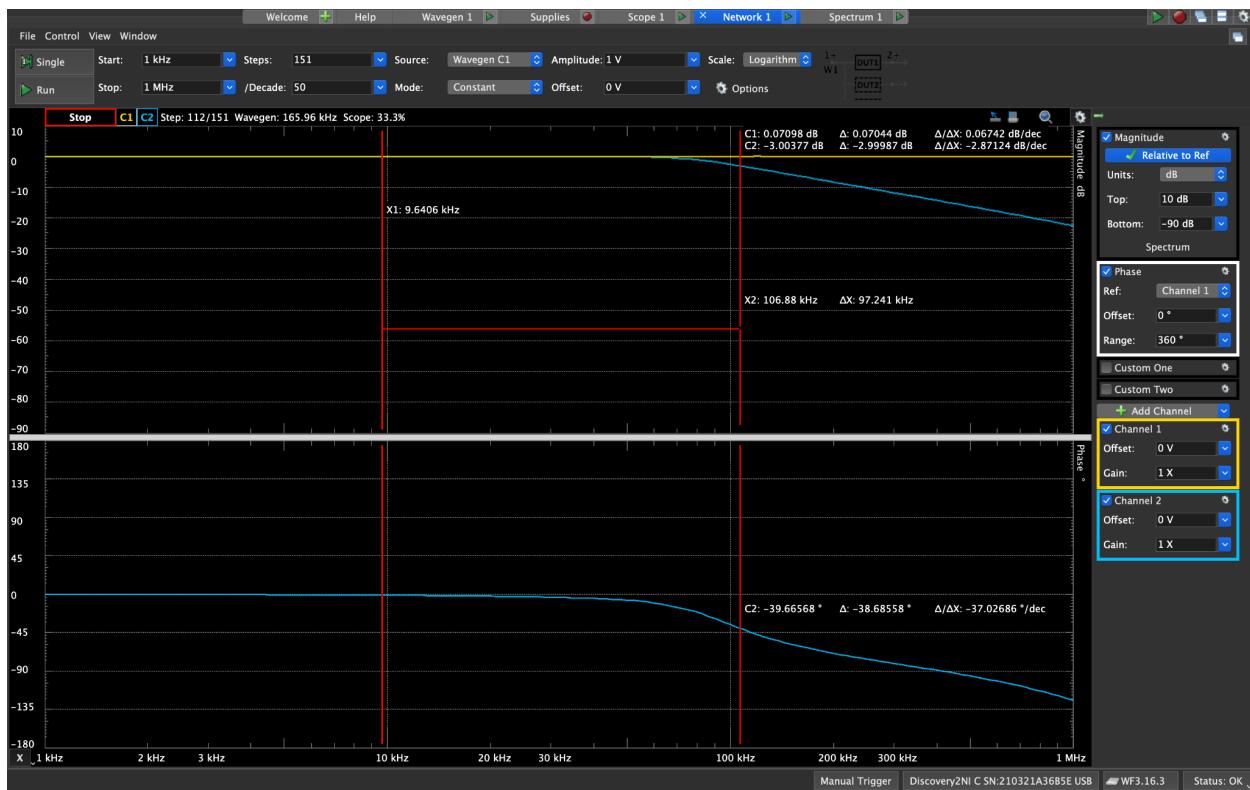

**Max: 3.15 V**

## Total Harmonic Distortion

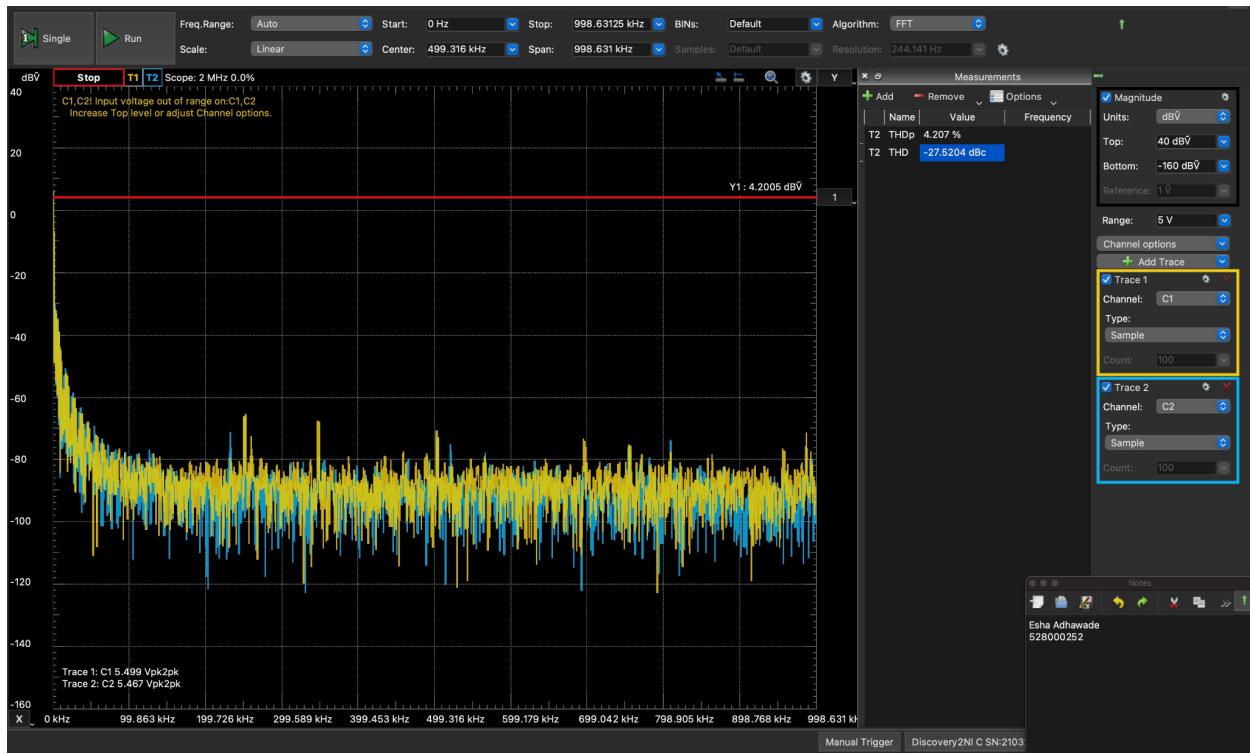

## Data Tables

### Input Offset Current Measurement

$$I_1 = V_1 / R = 0.00154 \text{ V} / 100\text{k}\Omega = 1.54 \times 10^{-8}$$

$$I_2 = V_2 / R = 0.00439 \text{ V} / 100\text{k}\Omega = 4.39 \times 10^{-8}$$

$$\text{Input Offset Current: } (4.39 \times 10^{-8}) - (1.54 \times 10^{-8}) = 2.85 \times 10^{-8} \text{ A}$$

### DC Offset Voltage Measurement

$$V_{i,\text{off}} = V_{o,\text{off}} / \text{Gain} = -0.00239 / 6 = -0.000398 \text{ V}$$

### Inverting and Non-inverting Configurations

	Vin	Vout	Voltage Gain
<b>Calculation Circuit A</b>	N/A	N/A	-3
<b>Calculation Circuit B</b>	N/A	N/A	6
<b>Calculation Circuit</b>	N/A	N/A	1

C			
<b>Simulation Circuit A</b>	-0.14083 V	0.42494 V	-3.0174
<b>Simulation Circuit B</b>	0.19951 V	1.2076 V	6.05283
<b>Simulation Circuit C</b>	0.199426 V	0.200459 V	1.0052
<b>Measurements Circuit A</b>	-1.0006 V	3.012 V	-3.0102
<b>Measurements Circuit B</b>	.2443 V	1.497 V	6.1277
<b>Measurements Circuit C</b>	0.1973 V	0.1984 V	1.0056

### Discussion

For lab 3, students learned about the different parameter values that can be utilized by operational amplifiers. Most of the values between the simulations and measurements, we were somewhat consistent for the circuits. If there were any minor differences, that's probably because of component differences, old breadboards, or loose wires.