

Esha Adhawade

Lab 2: Cadence Custom Layout: Design Rules, Extraction & Verification

ECEN 454 - 503

September 25, 2022


Introduction

The purpose of this lab is to create all layouts and extraction/ verifications for inverter, NAND, and XOR gates.


Result

Inverter


Schematic

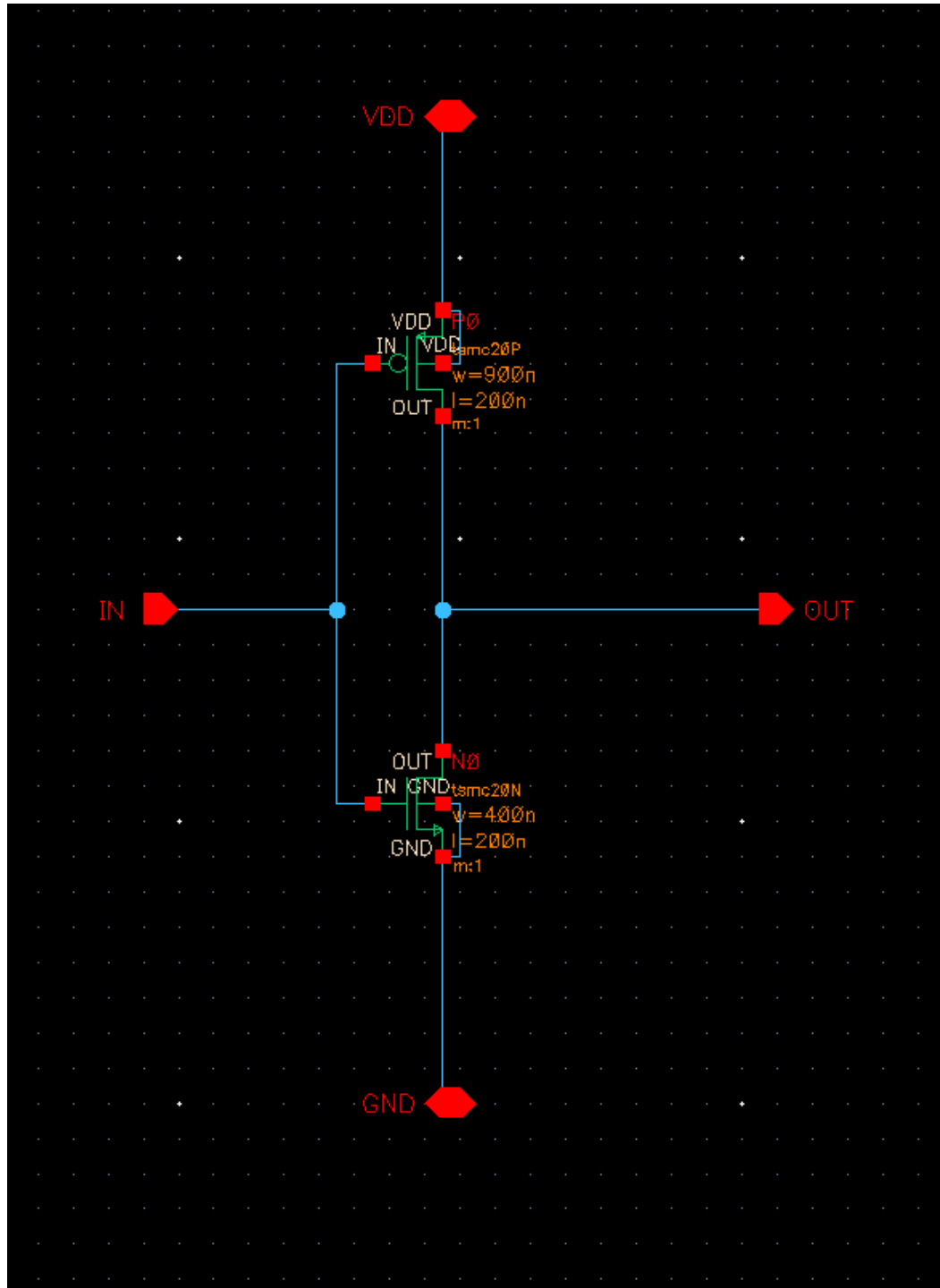


Symbol

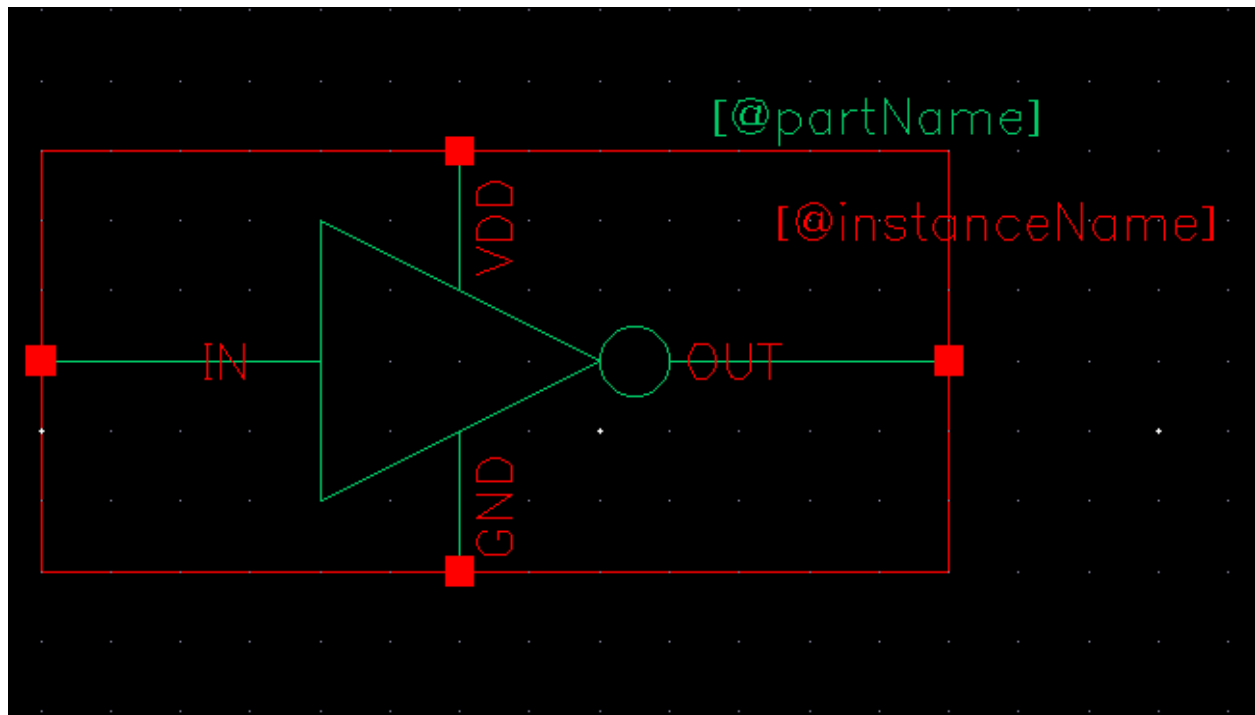


Layout

 

DRC - match

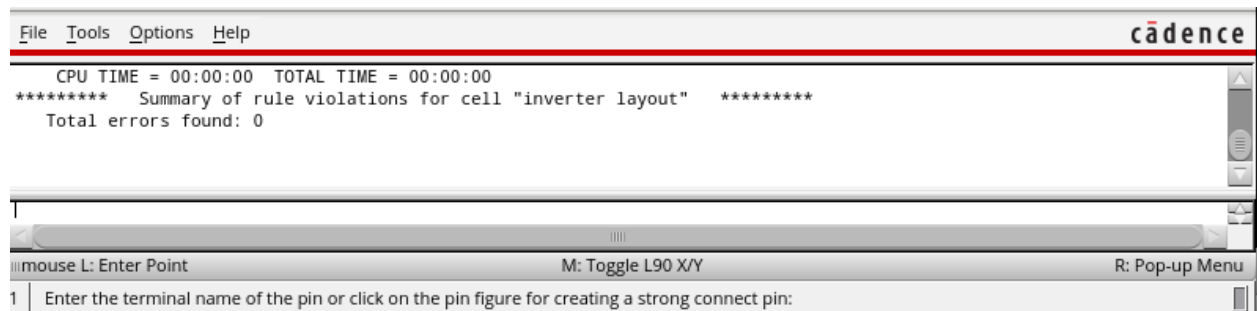

DRC

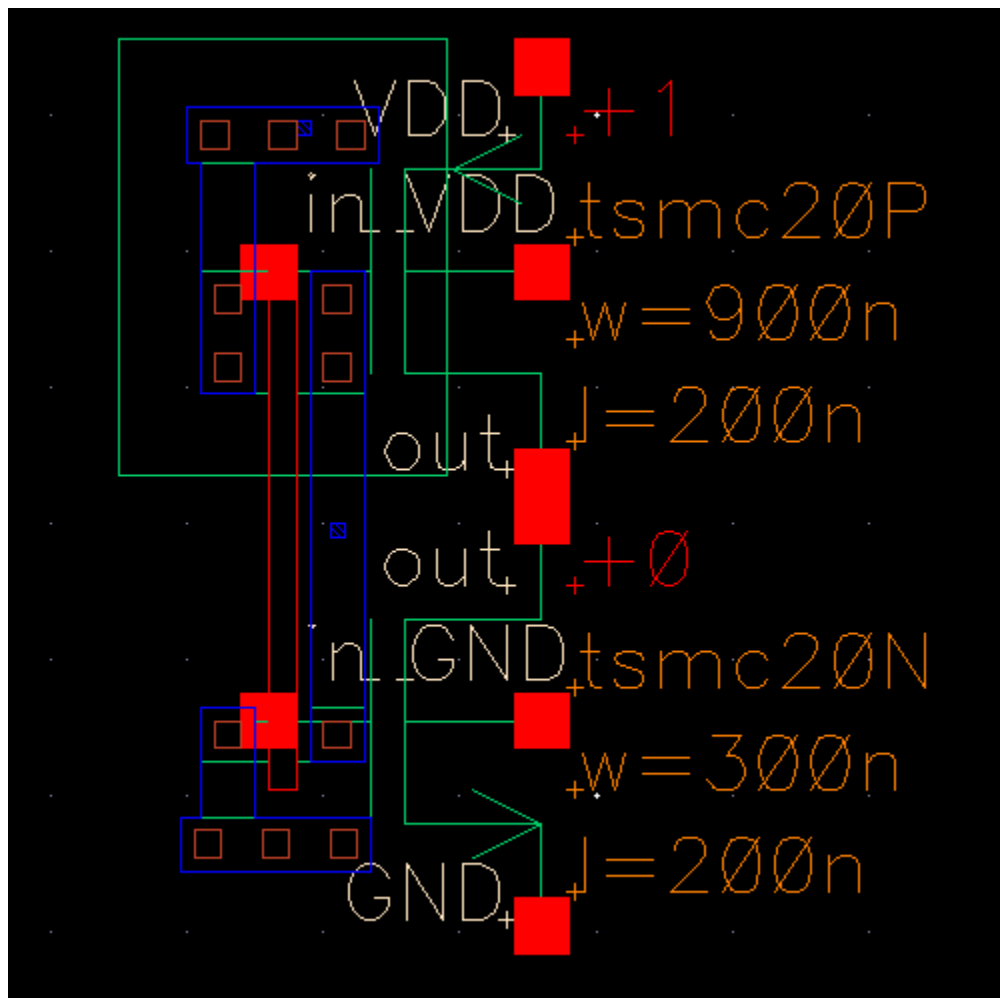

LVS (The net-lists match.)

```
RIPKOS: LVS version 6.1.8-64b 08/04/2020 19:19 (cpgsrv11) $
Command line: /opt/cadence/IC618/tools.lns86/dt11/bin/64bit/LVS -dlr /home/ugrads/e/esha.adhawaide/ecen454_503/LVS -l -s -t /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/layout /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/layout/netlist
count
4      nets
4      terminals
1      pmos
1      nmos

Net-list summary for /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/schematic/netlist
count
4      nets
4      terminals
1      pmos
1      nmos

Terminal correspondence points
NO      N1      GND
N2      N3      IN
N1      N2      OUT
N3      NO      VDD

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nnet pnet mosd pmosd

The net-lists match.

              layout schematic
un-matched    0      0
rewired       0      0
size errors   0      0
pruned        0      0
active        2      2
total         2      2

              nets
un-matched    0      0
merged        0      0
pruned        0      0
active        4      4
total         4      4


              terminals
un-matched    0      0
matched but   0      0
different type
total         4      4

Probe files from /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/schematic
devbad.out:
netbad.out:
mergenet.out:
termbad.out:
prunenet.out:
prunedev.out:
audit.out:


Probe files from /home/ugrads/e/esha.adhawaide/ecen454_503/LVS/layout
devbad.out:
netbad.out:
mergenet.out:
termbad.out:
prunenet.out:
prunedev.out:
audit.out:
```

NAND


Schematic

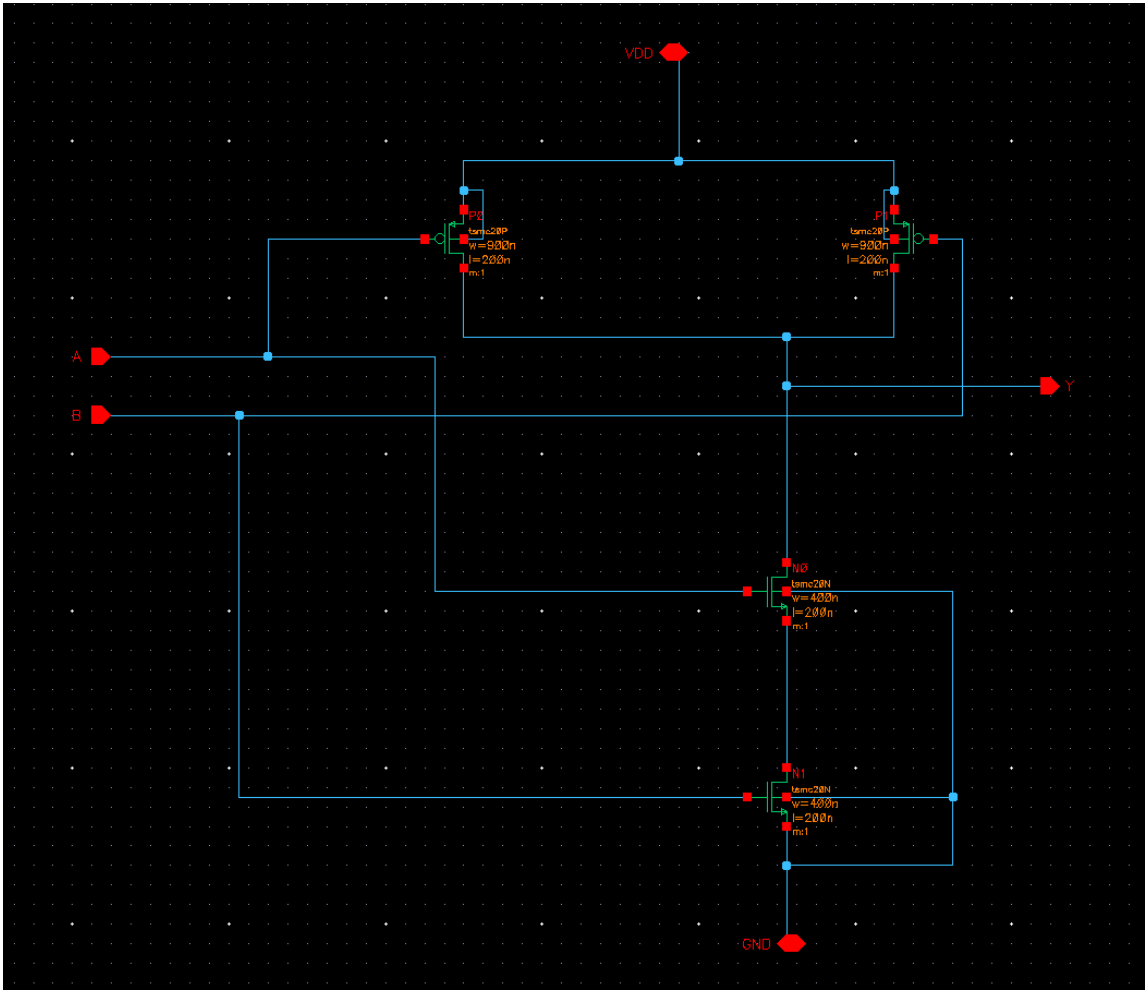


Symbol

 


Layout

 

DRC - match

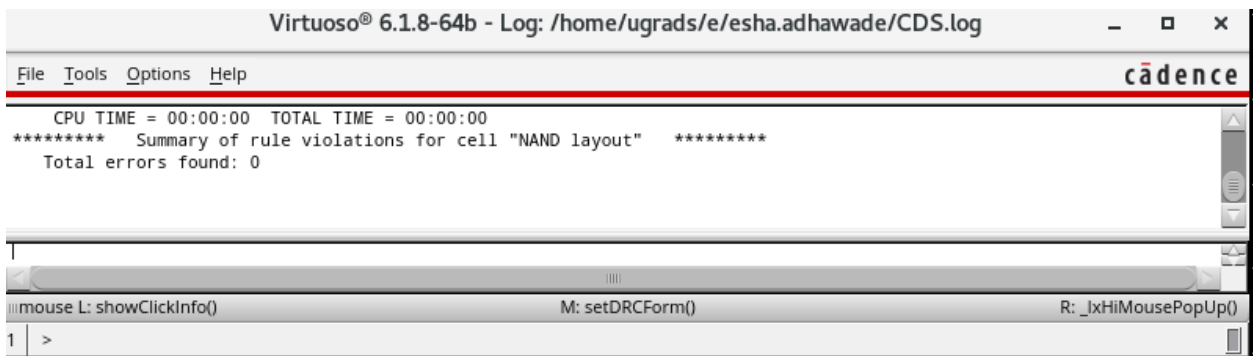

DRC

 

LVS (The net-lists match)

```

[CP]KCD5: LVS version 6.1.8-64b 08/04/2020 19:19 (cpgsrv11) $
Command line: /opt/coe/cadence/IC618/tools.lnx86/dfl1/bin/64bit/LVS -dir /home/ugrads/e/esha.adhawade/ecen454_503/LVS -l -s -t /home/ugrads/e/esha.adhawade/ecen454_503/LVS/layout /home/ugrads/e/esha.adhawade/ecen454_503/LVS/schematic
Like matching is enabled.
Net mapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/e/esha.adhawade/ecen454_503/LVS/layout/netlist
count
6      nets
5      terminals
2      pmos
2      nmos

Net-list summary for /home/ugrads/e/esha.adhawade/ecen454_503/LVS/schematic/netlist
count
6      nets
5      terminals
2      pmos
2      nmos

Terminal correspondence points
N4    N5    A
N3    N2    B
N2    N3    GND
N5    N0    VDD
N1    N1    Y

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.

          layout  schematic
un-matched      0      0
rewired          0      0
size errors     0      0
pruned          0      0
active          4      4
total           4      4

          nets
un-matched      0      0
merged          0      0
pruned          0      0
active          6      6
total           6      6

          terminals
un-matched      0      0
matched but
different type   0      0
total           5      5


Probe files from /home/ugrads/e/esha.adhawade/ecen454_503/LVS/schematic
devbad.out:
netbad.out:
mergenet.out:
termbad.out:
prunenet.out:
prunedev.out:
audit.out:

Probe files from /home/ugrads/e/esha.adhawade/ecen454_503/LVS/layout
devbad.out:
netbad.out:
mergenet.out:
termbad.out:
prunenet.out:
prunedev.out:

```



XOR

Schematic

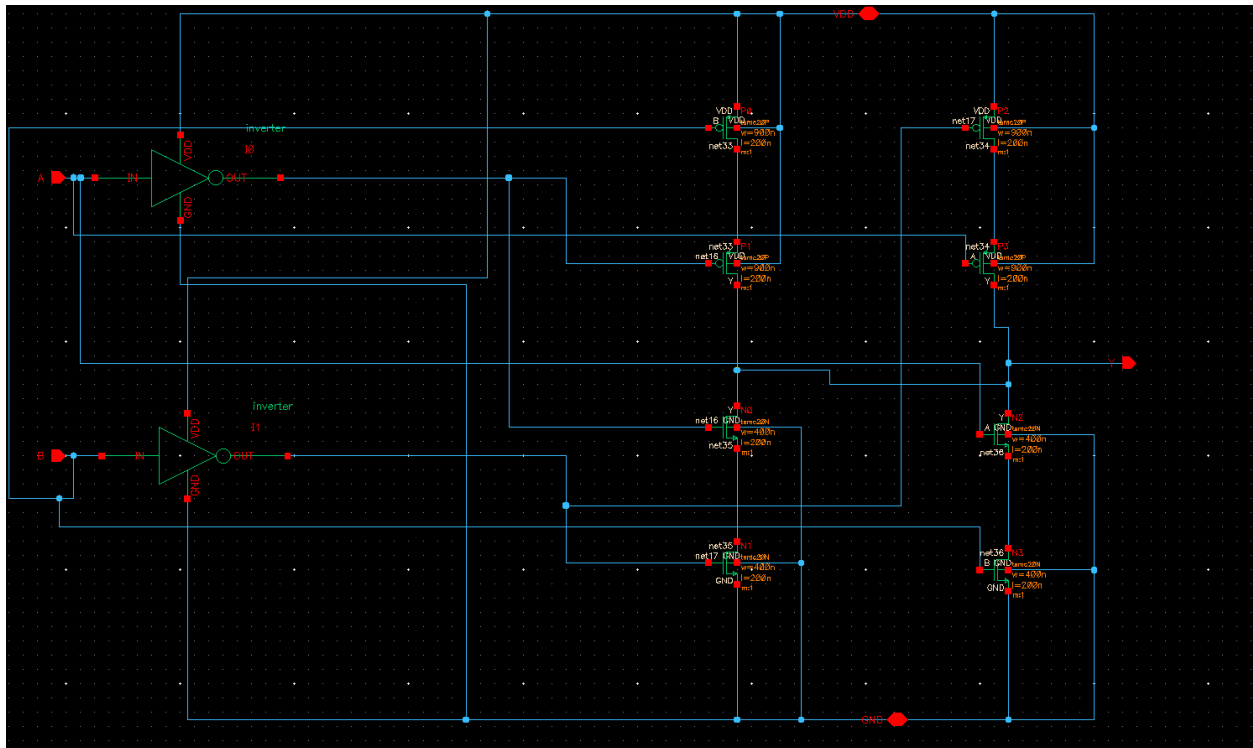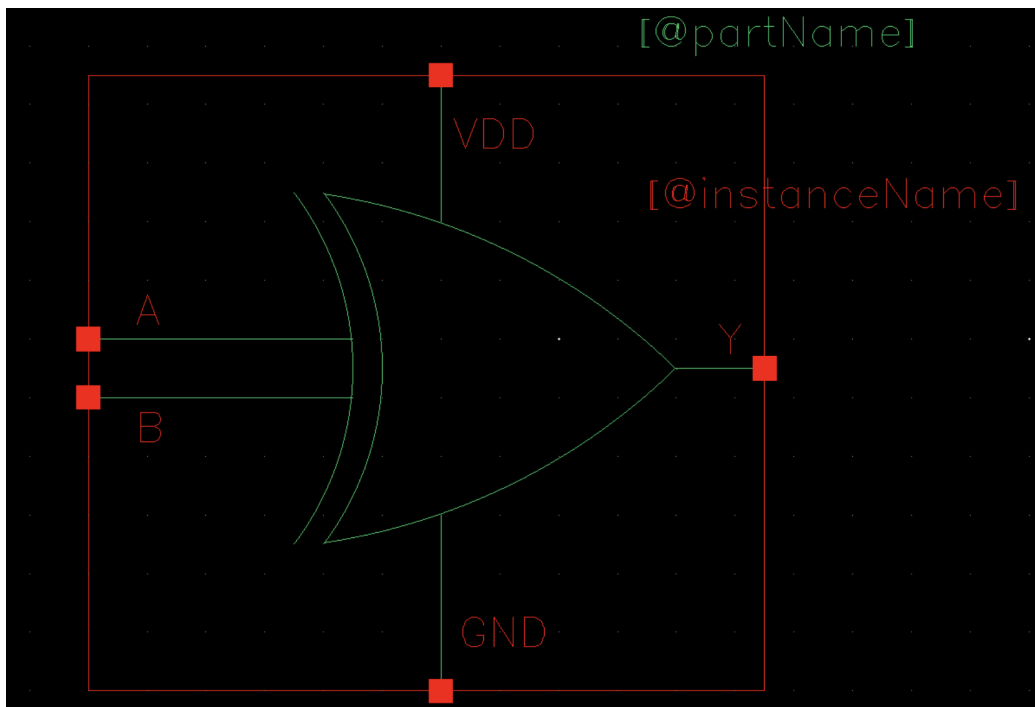


The wire labeling didn't work out so I just directly connect the inputs (A, B, _A (inverse), _B(inverse)) to corresponding terminals in order to pass check and save.

Symbol



Layout

 

DRC - match

CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "xor layout" *****
Total errors found: 0

vvv

DRC



LVS (The net-lists match)

Terminal correspondence points

N3	N1	A
N2	N3	B
N1	N2	GND
N5	N0	VDD
N4	N4	out

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:

```
cap nfet pfet nmos4 pmos4
```

The net-lists match.

	layout	schematic
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	4	4
total	4	4

	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	6	6
total	6	6

	terminals	
un-matched	0	0
matched but		
different type	1	1
total	5	5