

Lab 2: Second-Order Circuits

ECEN 325 - 511

TA: Zhiyong Zhang

Date Performed: September 21, 2021


Due Date: September 28, 2021

Purpose

The purpose of this lab was to be able to explore the frequency response for second-order circuits. This lab gave students experience with circuit design and analysis techniques, through simulations and measurements.

Calculations

part 1 → find transfer functions

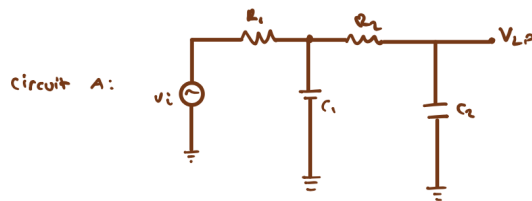

$$\frac{V - V_i}{R_1} + \frac{V}{Z_{C_1}} + \frac{V - V_{LP}}{R_2} = 0$$

$$\begin{aligned} V \left(\frac{1}{R_1} + C_1 s + \frac{1}{R_2} \right) &= \frac{V_i}{R_1} + \frac{V_{LP}}{R_2} \\ &= V (R_1 + R_2 + C_1 s R_1 R_2) = R_2 V_i + V_{LP} R_1 \\ &= \frac{R_2 V_i + V_{LP} R_1}{R_1 + R_2 + C_1 s R_1 R_2} \end{aligned}$$

and , $\frac{V_{LP}}{Z_{C_2}} + \frac{V_{LP} - V}{R_2} = 0$

$$s C_2 V_{LP} + \frac{V_{LP}}{R_2} = V \Rightarrow (s C_2 R_2 + 1) V_{LP} = V$$


$$= V_{LP} (s C_2 R_2 + 1) = \frac{R_2 V_i + V_{LP} R_1}{R_1 + R_2 + C_1 s R_1 R_2}$$

$$\begin{aligned} &= V_{LP} (R_1 + R_2 + C_1 s R_1 R_2 + R_1 R_2 C_2 s + s R_2^2 C_2 + R_1 R_2^2 C_1 C_2 s^2) \\ &= R_2 V_i + V_{LP} R_1 \end{aligned}$$

$$= V_{LP} (R_2 + C_1 s R_1 R_2 + R_1 R_2 C_2 s + s R_2^2 C_2 + R_1 R_2^2 C_1 C_2 s^2) = R_2 V_i$$

$$\boxed{\frac{V_{LP}}{V_i} = \frac{1}{R_1 + C_1 s R_1 R_2 + C_2 R_1 s + s R_2^2 C_2 + R_1 R_2 C_1 C_2 s^2}}$$

Circuit B:

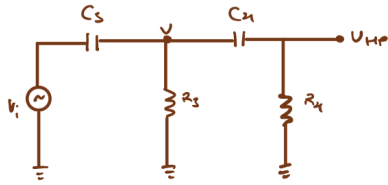

$$\frac{V_o - V_i}{2C_3} + \frac{V}{R_3} + \frac{V - V_{HP}}{R_4 C_4} = 0$$

$$V \left(\frac{1}{1/sC_3} + \frac{1}{R_3} + \frac{1}{1/sC_4} \right) = sC_3 V_i + sC_4 V_{HP}$$

$$V \left(sC_3 + \frac{1}{R_3} + sC_4 \right) = sC_3 V_i + sC_4 V_{HP}$$

$$V (sC_3 R_3 + 1 + R_3 sC_4) = R_3 sC_3 V_i + R_3 sC_4 V_{HP}$$

$$V = \frac{R_3 s (sC_3 V_i + R_3 sC_4 V_{HP})}{(sC_3 R_3 + 1 + R_3 sC_4)}$$

and , $\frac{V_{HP}}{R_4} + \frac{V - V_o}{1/sC_4} = 0$

$$\frac{V_{HP}}{R_4} + V_{HP} \left(\frac{1}{R_4} + sC_4 \right) = sC_4 V$$


$$V_{HP} (1 + R_4 sC_4) = sC_4 R_4 V$$

$$V_{HP} (1 + R_4 sC_4) = sR_4 C_4 \left(\frac{R_3 s (sC_3 V_i + sR_3 C_4 V_{HP})}{sC_3 R_3 + 1 + R_3 sC_4} \right)$$

$$V_{HP} (1 + R_4 s C_4) (s C_3 R_3 + 1 + R_3 s C_4) = s^2 (R_3 R_4 C_3 C_4 V_i + R_3 R_4 C_4^2 V_{HP})$$

$$\hookrightarrow s(C_3 R_3 + 1 + R_3 s C_4 + s^2 R_3 C_3 R_4 C_4 + C_4 R_4 + s^2 R_3 R_4 C_4^2)$$
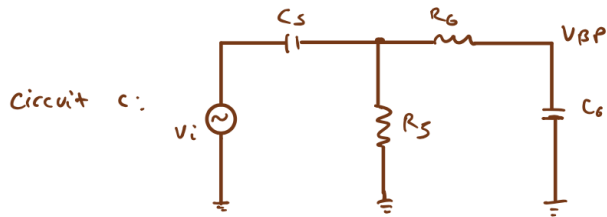
$$\frac{V_{HP}}{V_i} = \frac{s^2 R_3 R_4 C_3 C_4}{1 + s(C_3 R_4 + C_3 R_3 + R_4 C_4) + s^2 R_3 R_4 C_3 C_4}$$



$$\frac{V - V_i}{2C_5} + \frac{V}{R_5} + \frac{V - V_{HP}}{R_6} = 0$$

$$V \left(sC_5 + \frac{1}{R_5} + \frac{1}{R_6} \right) = V_i sC_5 + \frac{V_{HP}}{R_6}$$

$$V \left(\frac{sC_5 R_5 R_6 + R_6 + R_5}{R_5 R_6} \right) = \frac{R_6 V_i sC_5 + V_{HP} R_5}{R_6}$$

$$V (sC_5 R_5 R_6 + R_6 + R_5) = R_5 R_6 sC_5 V_i + V_{HP} R_5$$

$$V = \frac{R_5 R_6 sC_5 V_i + V_{HP} R_5}{sC_5 R_5 R_6 + R_6 + R_5}$$

$$\text{and, } \frac{V_{HP}}{2C_6} + \frac{V_{HP} - V}{R_6} = 0$$

$$= V_{HP} (sC_6 + \frac{1}{R_6}) = \frac{V}{R_6}$$

$$= V_{HP} (sC_6 R_6 + 1) = V$$

$$= V_{HP} (sC_6 R_6 + 1) = \frac{sR_5 R_6 C_5 V_i + V_{HP} R_5}{sC_5 R_5 R_6 + R_6 + R_5}$$

$$V_{HP} (1 + sC_6 R_6) (sC_5 R_5 R_6 + R_6 + R_5) = sR_5 R_6 C_5 V_i + V_{HP} R_5$$

$$V_{HP} (1 + sC_5 R_5 + s^2 C_6 C_5 R_5 R_6 + sC_6 R_6 + sC_6 R_5) = sR_5 C_5 V_i$$

$$\frac{V_{HP}}{V_i} = \frac{sR_5 C_5}{1 + s(C_5 R_5 + C_6 R_6 + C_6 R_5) + s^2 C_6 C_5 R_5 R_6}$$

part 2 → find values for resistors and capacitors

$$\text{circuit A: } H_{LP} = \frac{1}{1 + \frac{s}{2\pi f_1}} \cdot \frac{1}{1 + \frac{s}{2\pi f_2}} = \frac{1}{1 + s\left(\frac{1}{2\pi f_1} + \frac{1}{2\pi f_2}\right) + s^2\left(\frac{1}{4\pi^2 f_1 f_2}\right)}$$

lets say $C_1 = 47nF$ and $C_2 = 1nF$

$$\text{then } \frac{1}{2\pi f_1} + \frac{1}{2\pi f_2} = C_1 R_1 + C_2 R_2 + R_1 C_2$$

$$\begin{aligned} \frac{f_1 + f_2}{2\pi f_1 f_2} &= R_1 (C_1 + C_2) + C_2 R_2 \\ &= \frac{11000}{2\pi 1000000} = R_1 [47 \times 10^{-9}] + 1 \times 10^{-9} R_2 \end{aligned}$$

$$R_2 = \frac{1.75 \times 10^{-4}}{1 \times 10^{-9}} - \frac{(47 \times 10^{-9}) R_1}{1 \times 10^{-9}} \quad R_2 = 1.75 \times 10^5 - 47 R_1$$

$$\frac{1}{4\pi^2 f_1 f_2} = R_1 R_2 C_1 C_2 \rightarrow 2.533 \times 10^{-4} = (1.75 \times 10^5 - 47 R_1) 47 \times 10^{-9} R_1$$

$$5.39 \times 10^{-2} = 1.75 \times 10^5 R_1 - 47 R_1^2$$

$$47 R_1^2 - 1.75 \times 10^5 R_1 + 5.39 \times 10^{-2} = 0$$

$$R_1 = 3723 \Omega, \quad R_2 = 171277 \Omega, \quad C_1 = 47 \text{ nF}, \quad C_2 = 1 \text{ nF}$$

Circuit B: $H_{HP}(s) = \frac{s}{s + 2\pi f_3} \cdot \frac{s}{s + 2\pi f_4} = \frac{s^2 / 4\pi^2 f_3 f_4}{1 + \frac{2\pi(f_3 + f_4)}{4\pi^2 f_3 f_4} s + \frac{s^2}{4\pi^2 f_3 f_4}}$

$$C_4 R_4 + C_4 R_3 + R_3 C_3 = \frac{f_3 + f_4}{2\pi(f_3 f_4)} \quad \text{let } C_3 = 10 \text{ nF and } C_4 = 1 \text{ nF}$$

then, $1 \times 10^{-9} R_4 + 1 \times 10^{-9} R_3 + 10 \times 10^{-6} R_3 = 3.5 \times 10^{-4}$
 $\sim 1 \times 10^{-9} R_4 + 10 \times 10^{-6} R_3 = 3.5 \times 10^{-4}$
 $\sim 1 \times 10^{-3} R_4 + R_3 = 35$

$$\text{so, } \frac{1}{4\pi^2 f_3 f_4} = R_3 R_4 C_3 C_4$$

$$= \frac{1}{4\pi^2 \cdot 10^7} = R_4 (35 - 1 \times 10^{-3} R_4) 1 \times 10^{-14}$$

$$R_3 = 24.77 \Omega \quad R_4 = 10223.7 \Omega \quad C_3 = 10 \text{ nF} \quad C_4 = 1 \text{ nF}$$

circuit c:
$$\frac{S}{s+2\pi f_s} \cdot \frac{1}{1+\frac{s}{2\pi f_6}} = \frac{\frac{s/2\pi f_s}{2\pi f_s + 1}}{1 + \frac{s/2\pi f_6}{1 + \left(\frac{1}{2\pi f_s} + \frac{1}{2\pi f_6}\right)^2 + s^2 \left(\frac{1}{4\pi^2 f_s f_6}\right)}}$$

$$C_s R_s + C_6 R_6 + C_6 R_s = \frac{1}{2\pi} \left(\frac{1}{f_s} + \frac{1}{f_6} \right)$$

$$R_s (C_6 + C_s) + C_6 R_6 = \frac{1}{2\pi} \left(\frac{1}{1k} + \frac{1}{100k} \right)$$

let $C_s = 1\mu F$ and $C_6 = 1nF$

$$C_s R_s + C_6 R_6 = \frac{1}{2\pi} \left(\frac{1010000}{1000000000} \right)$$

$$1 \times 10^{-6} R_s + 1 \times 10^{-9} R_6 = 1.607 \times 10^{-5}$$

$$R_6 = 1607 + 1 \times 10^{-3} R_s$$

so, $\frac{1}{4\pi^2 f_s f_6} = C_s C_s R_s R_6$

$$= \frac{2.535 \times 10^{-11}}{1 \times 10^{-15}} = (16.07 + 1 \times 10^{-3} R_6)$$

$$25330 = (16.07 + 1 \times 10^{-3} R_6) R_s$$

$R_s = 16.07\Omega$	$R_6 = 1576\Omega$	$C_s = 1\mu F$	$C_6 = 1nF$
---------------------	--------------------	----------------	-------------



part 3 \Rightarrow plots

circuit A: $f_1 = 1kHz$ $f_2 = 10kHz$

$$H_{LP} = \frac{1}{1 + \frac{s}{2600\pi}} \cdot \frac{1}{1 + \frac{s}{20000\pi}}$$

$$\lim_{s \rightarrow 0} (H_{LP}) = 1$$

$$\lim_{s \rightarrow \infty} = 0$$

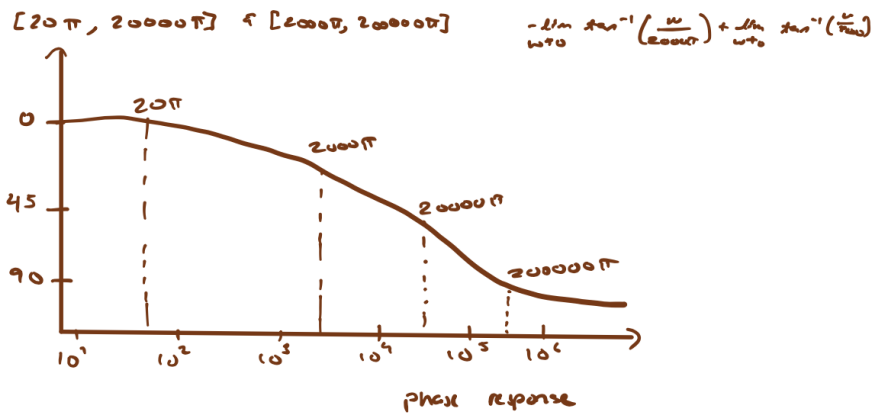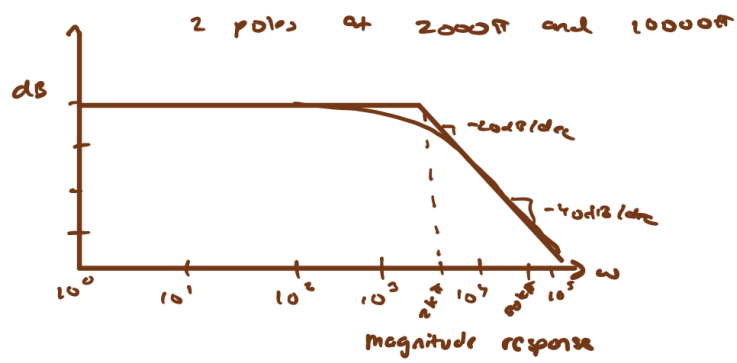


Circuit 8:

$$H_{HP} = \frac{s}{s + 2\pi f_3} \cdot \frac{s}{s + 2\pi f_4} \quad \text{since } f_3 = 1 \text{ kHz} \quad f_4 = 10 \text{ kHz} \quad = \frac{s}{s + 2000\pi} \cdot \frac{s}{s + 20000\pi}$$

there's two poles at 2000π , 20000π and 2 zeros at 0


$$\lim_{s \rightarrow 0} |H_{HP}| = 10 \log(s)^2 + 10 \log(s)^2 - 10 \log_{10}(2000\pi)^2 - 10 \log_{10}(20000\pi)^2$$

$$= -75.96 - 95.46 = -171.92$$

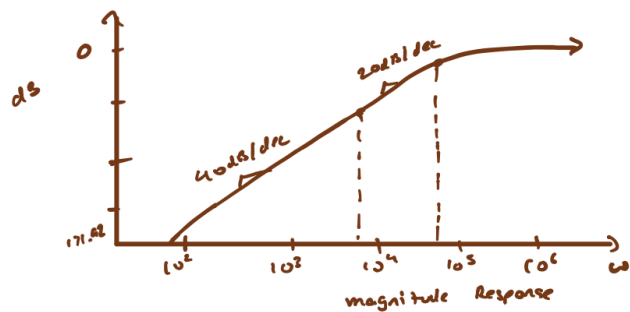

$$\lim_{\omega \rightarrow 0} \text{phase } |H_{HP}| = \tan^{-1}\left(\frac{s}{0}\right) + \tan^{-1}\left(\frac{s}{0}\right) - \tan^{-1}\left(\frac{s}{2000\pi}\right) - \tan^{-1}\left(\frac{s}{20000\pi}\right)$$

$$= 90 + 90 = 180^\circ$$

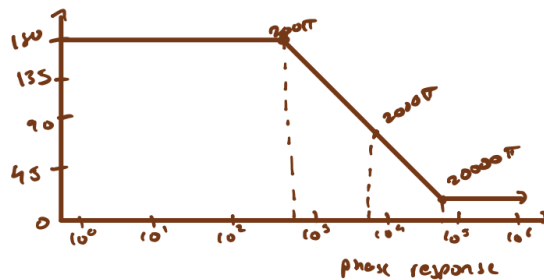


circuit (i): $\frac{s}{s + 2\pi f_3} \cdot \frac{1}{1 + \frac{s}{2\pi f_6}} = \frac{s}{s + 2000\pi} + \frac{1}{1 + \frac{s}{2000\pi}}$

$f_3 = 1\text{kHz}$
 $f_6 = 100\text{kHz}$


there's 0's on 0 and poles on 2000π and 2000π

$$\lim_{\omega \rightarrow 0} |H_{sp}| = 10 \log_{10}(1^2) - 10 \log_{10}(2000\pi)^2 - 20 \log_{10}(2000\pi)^2 = -24.92 \text{ dB}$$

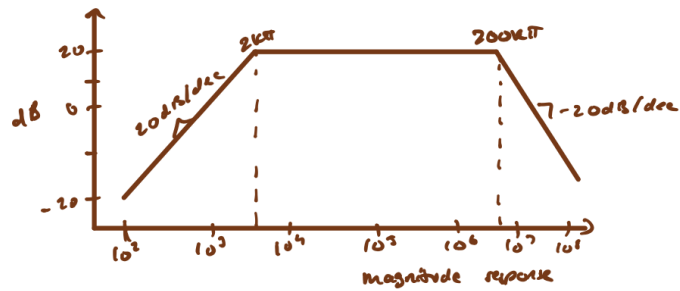

$$\lim_{\omega \rightarrow 0} \text{phase } |H_{sp}| = \tan^{-1}\left(\frac{1}{0}\right) - \tan^{-1}\left(\frac{1}{2000\pi}\right) - \tan^{-1}\left(\frac{1}{2000\pi}\right) = 90^\circ$$

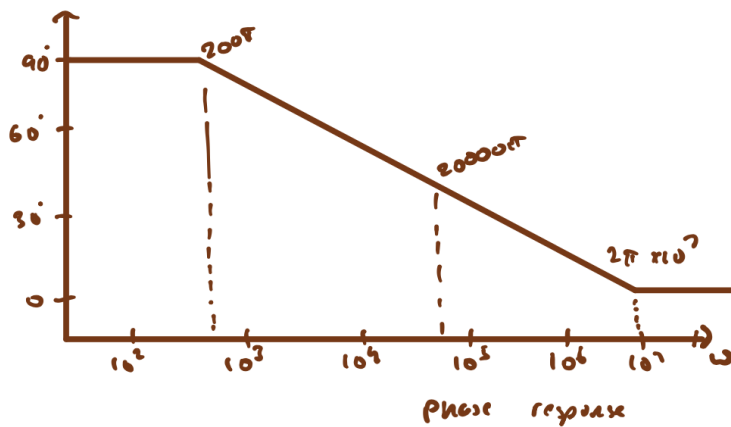$[200\pi, 20000\pi] \quad [20000\pi, 200000\pi]$



part 9 \rightarrow find V_o

circuit A: Here $V_i = 0.5 \sin(2\pi 10000t)$
 $V_i = 0.5 \angle 0^\circ$

$$\text{Now } H_{LP} = \frac{1}{1 + \frac{j\omega}{2000\pi}} - \frac{1}{1 + \frac{j\omega}{20000\pi}}$$

$$H_{LP}(2\pi 10000) = \frac{1}{\left(1 + j \frac{20000\pi}{2000\pi}\right)} \cdot \frac{1}{1 + j \frac{20000\pi}{20000\pi}}$$

$$= \frac{1}{1+j10} \cdot \frac{1}{1+j} = -0.024 - 0.026j$$

$$= 0.035 \angle -132.376$$

So,

$$V_{LP} = H_{LP} \cdot 0.5 \angle 0$$

$$= 0.0176 \angle -132.376$$

$$V_{LP} = 0.0176 \sin(2\pi 10000t - 132.376)$$

Circuit B: $H_{HP} = \frac{s}{s + 2\pi f_3} \cdot \frac{s}{s + 2\pi f_4}$

$$f_3 = 10 \text{ kHz}$$

$$f_4 = 10 \text{ kHz}$$

$$= \frac{s}{s + 2\pi 10000} \cdot \frac{s}{s + 2\pi 10000} = \frac{j\omega}{j\omega + 20000\pi} \cdot \frac{j\omega}{j\omega + 20000\pi}$$

$$H_{HP}(10000) = \frac{2\pi 10000\pi j}{20000\pi + 20000\pi} + \frac{20000\pi j}{20000\pi + 20000\pi}$$

$$= \frac{10j}{10\pi j} \cdot \frac{j}{1+j} = 0.70 \angle 129.28$$

$$V_{HP} = H_{HP} \cdot 0.5 \angle 0 = 0.70 \angle 129.28 \cdot 0.5 \angle 0 = 0.35 \angle 129.28$$

$$V_{HP} = 0.35 \sin(2\pi 10000t + 129.28)$$

circuit c: $V_{BP} = \frac{s}{s + 2\pi f_c} \cdot \frac{1}{1 + \frac{s}{2\pi f_c}}$ $f_s = 1\text{kHz}$
 $f_c = 100\text{kHz}$
where $\omega = 2\pi \cdot 100000$

$$= \frac{j\omega}{j\omega + 20000\pi} \cdot \frac{1}{1 + \frac{j\omega}{20000\pi}}$$

$$H_{BP}(100000) = \frac{j20000\pi}{j200000\pi + 20000\pi} \cdot \frac{1}{1 + \frac{200000\pi j}{2000000\pi}} = \frac{10j}{10j + 1} \cdot \frac{1}{1 + j/100}$$

$$= \frac{10j}{10j + 1} \cdot \frac{100}{100j + 1} = 0.995 \angle 5.13^\circ$$

$$V_{BP} = H_{BP} V_i$$


$$= 0.995 \angle 5.13^\circ \cdot 0.5 \angle 0^\circ = 0.497 \angle 5.13^\circ$$

$$V_{BP} = 0.497 \sin(2\pi 100000t + 5.13^\circ)$$


Simulations (on Multisim)

Lowpass Circuit


Schematic

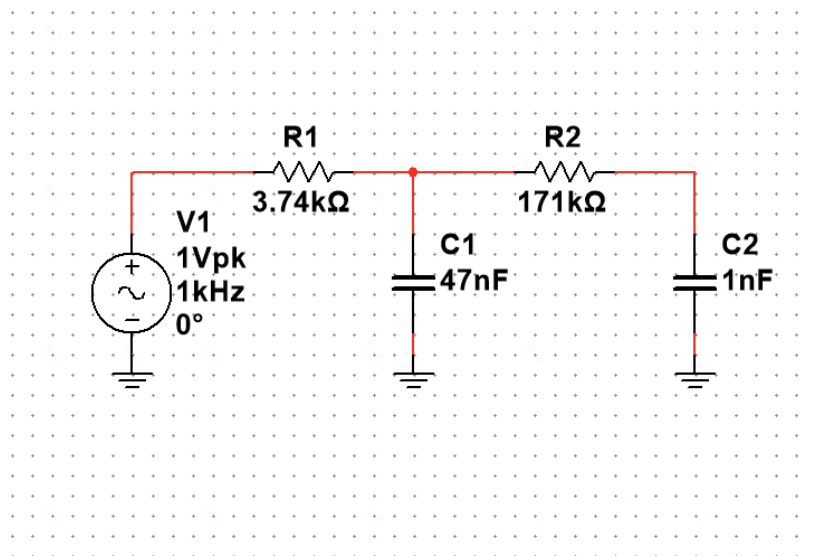

Transient

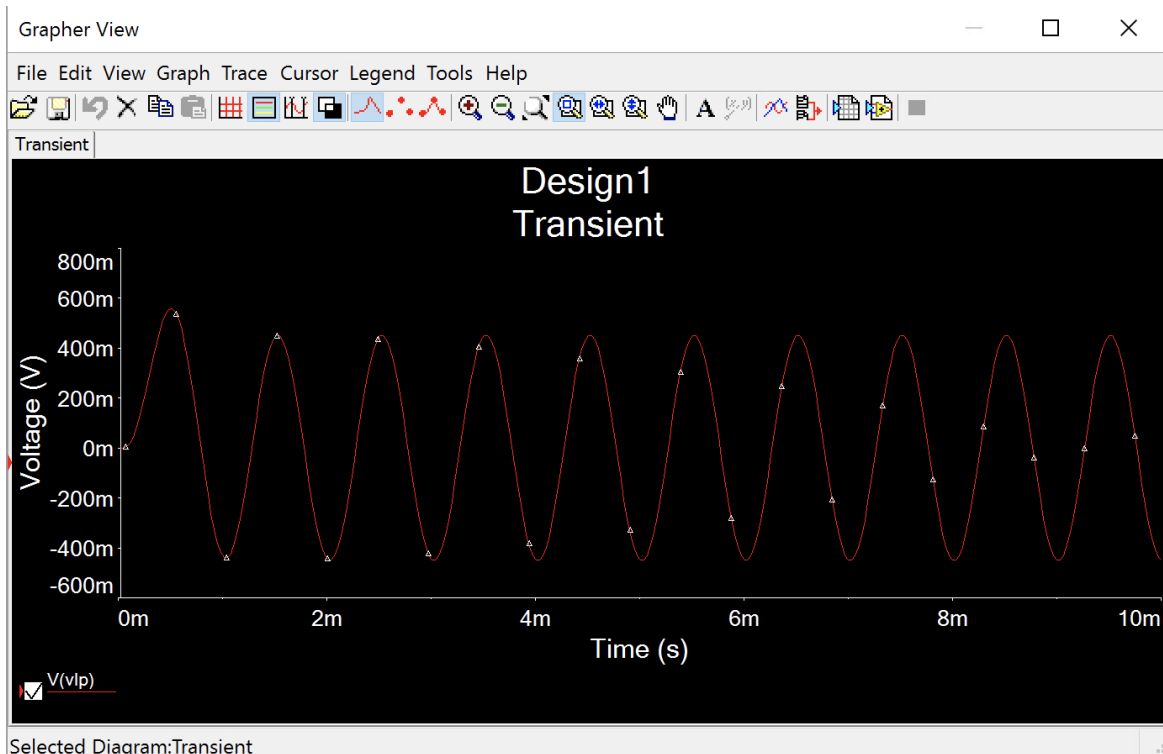


AC Sweep

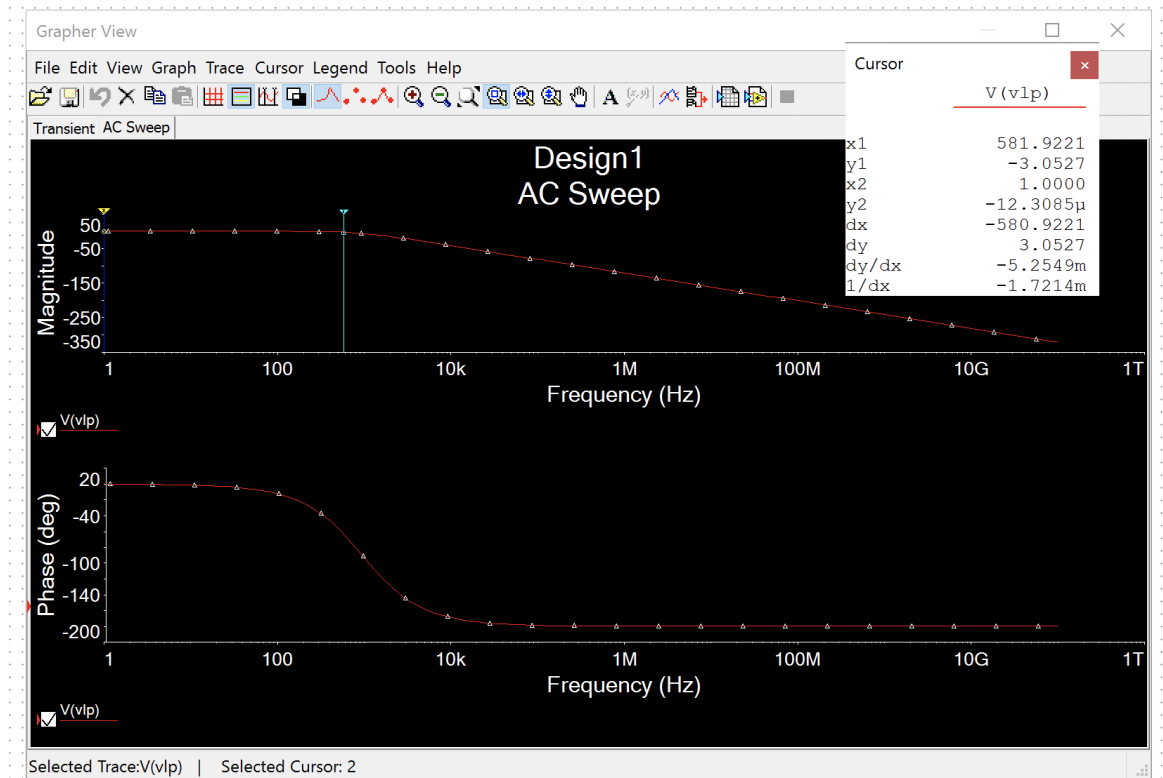


Highpass Circuit


Schematics

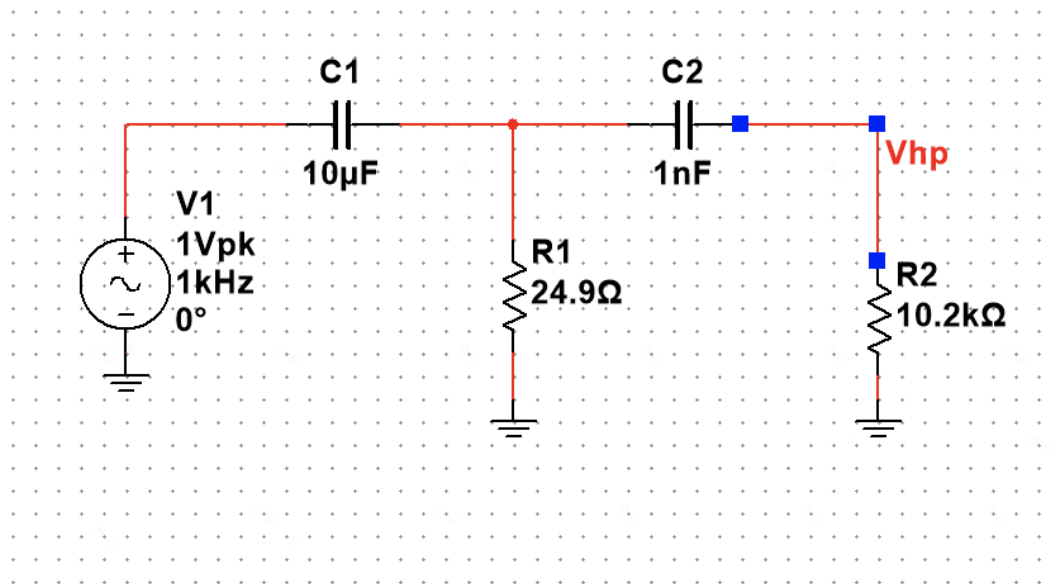

Transient

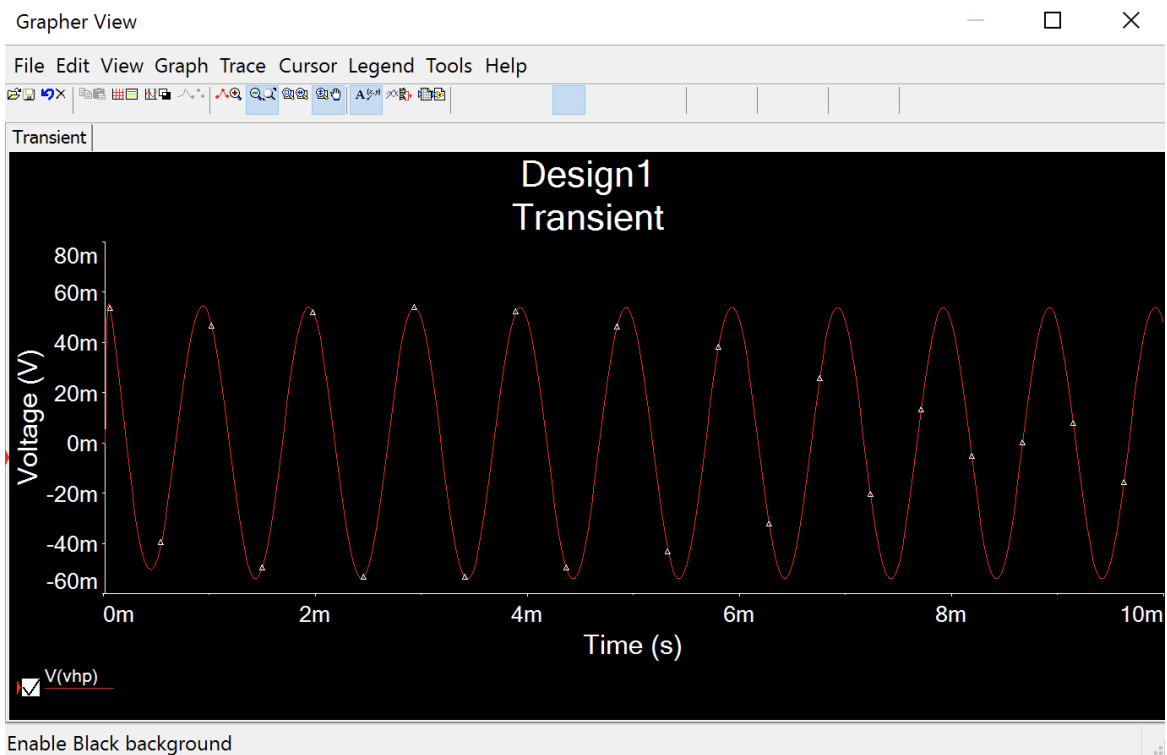


AC Sweep

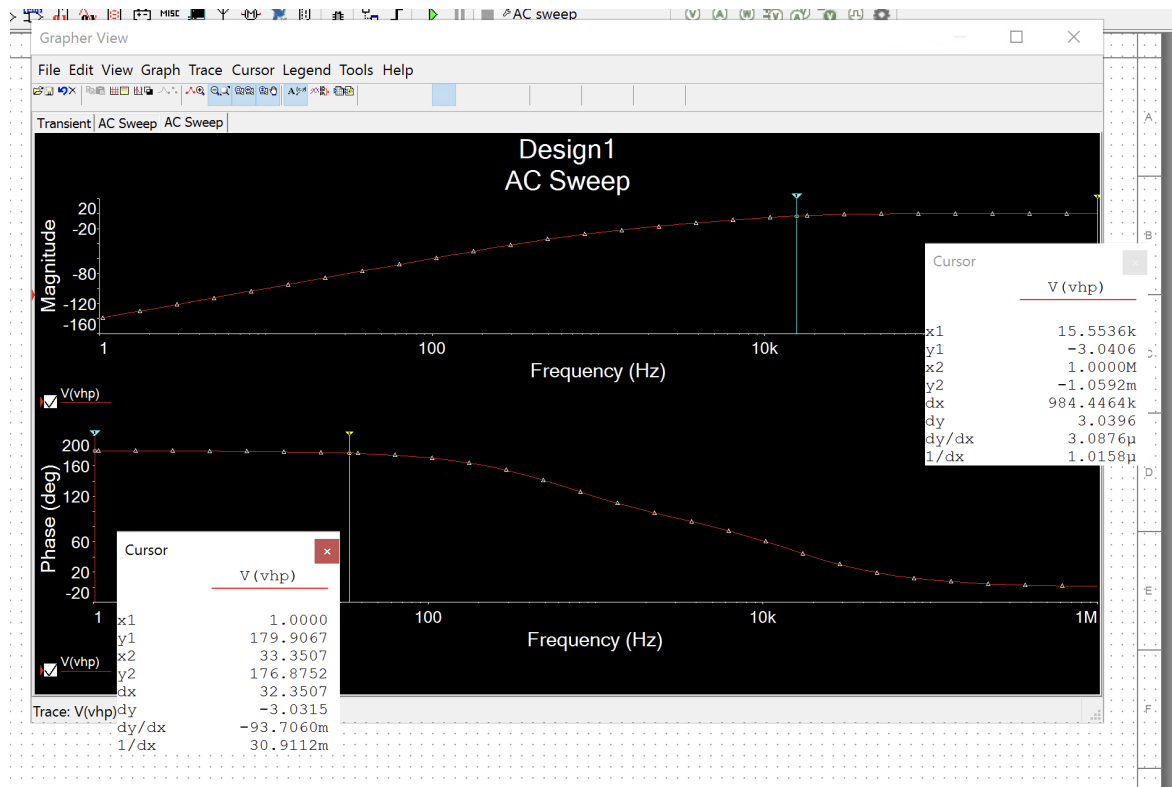


Bandpass Circuit


Schematic

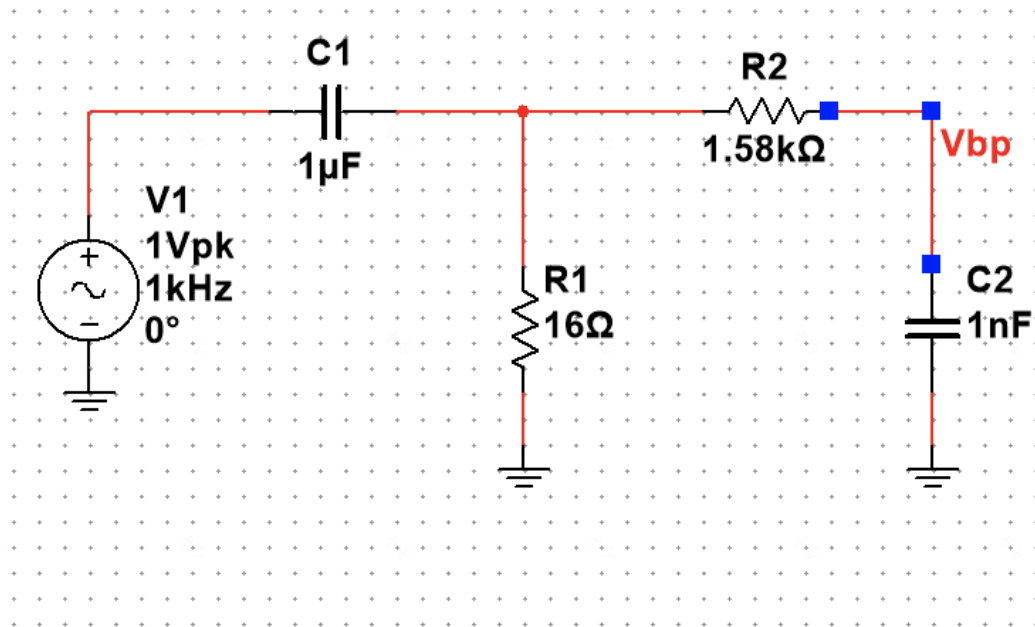

Transient

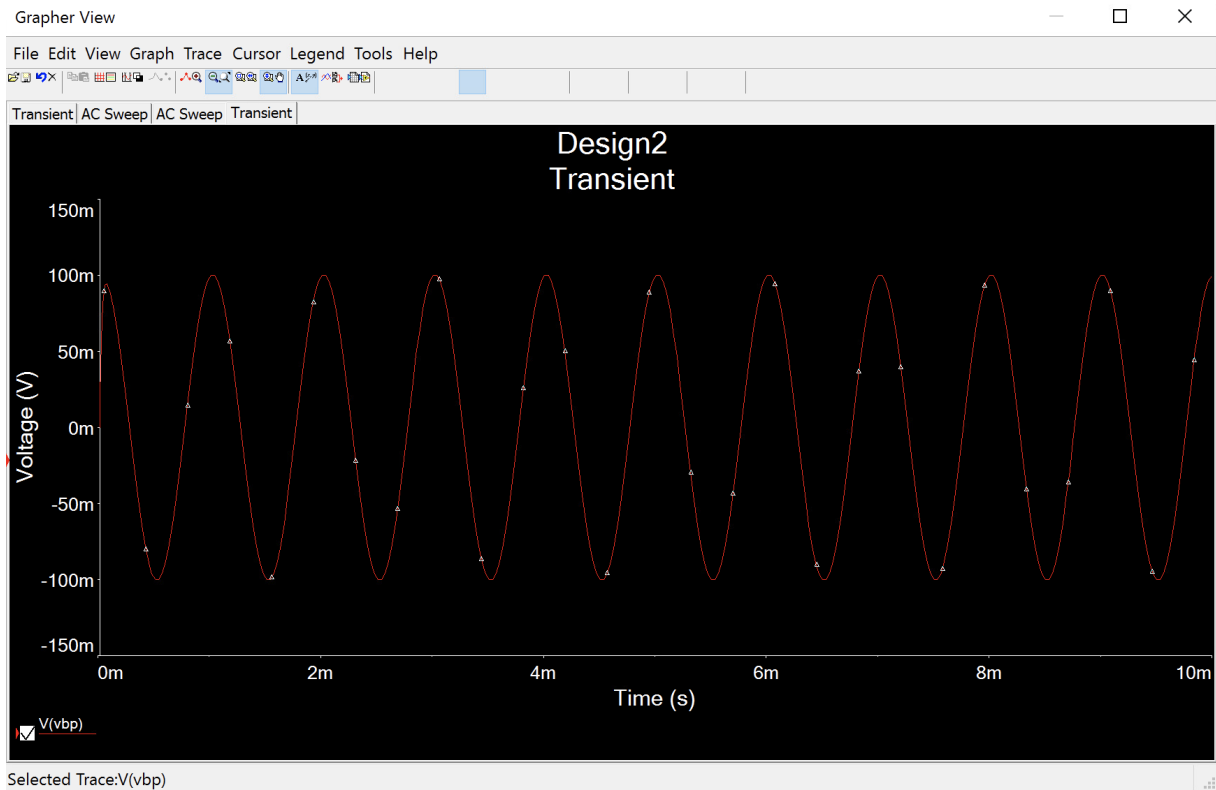


AC Sweep

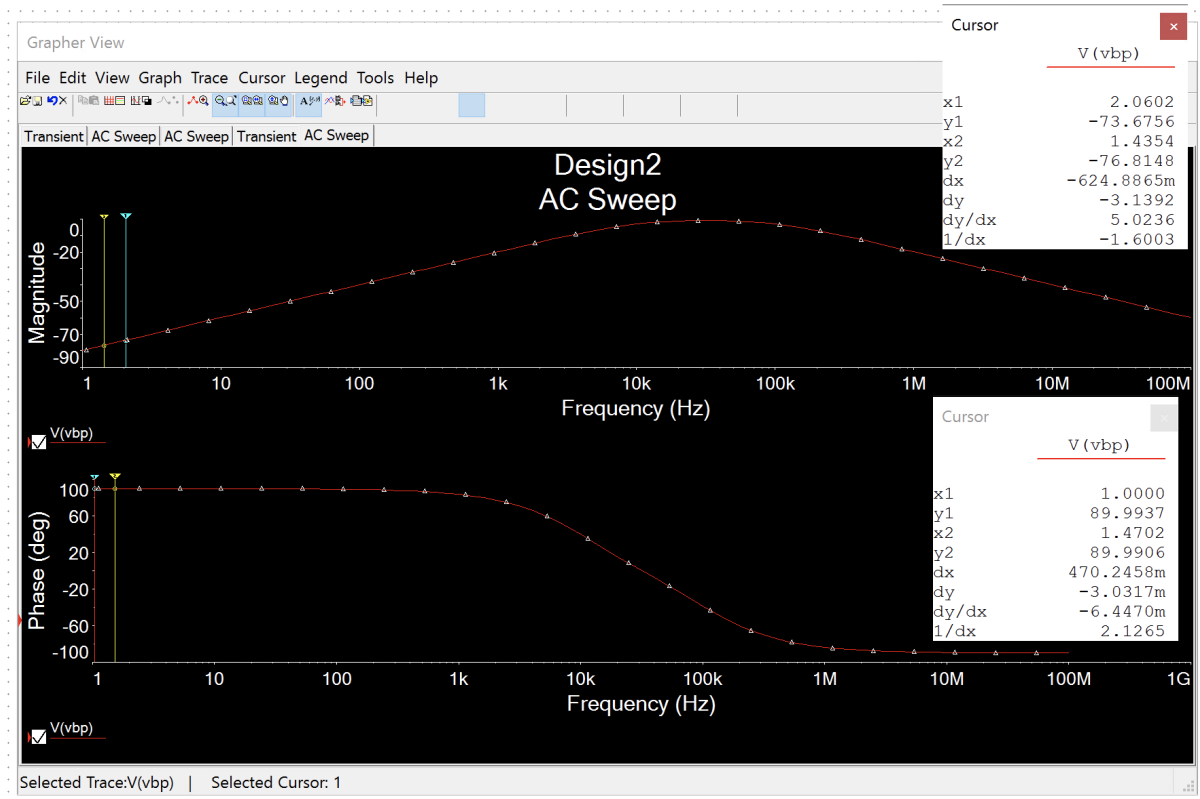


Measured Waveforms

Circuit A-low pass

Bode Plot

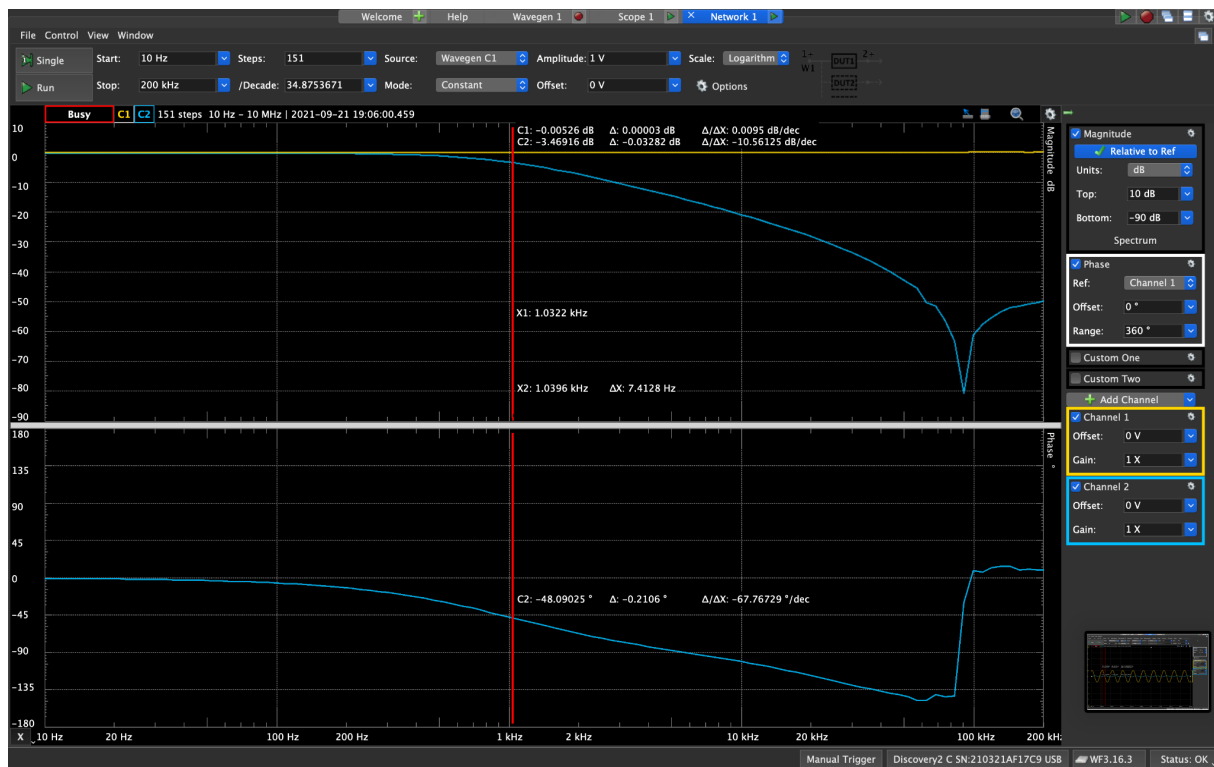


Time Domain Plot

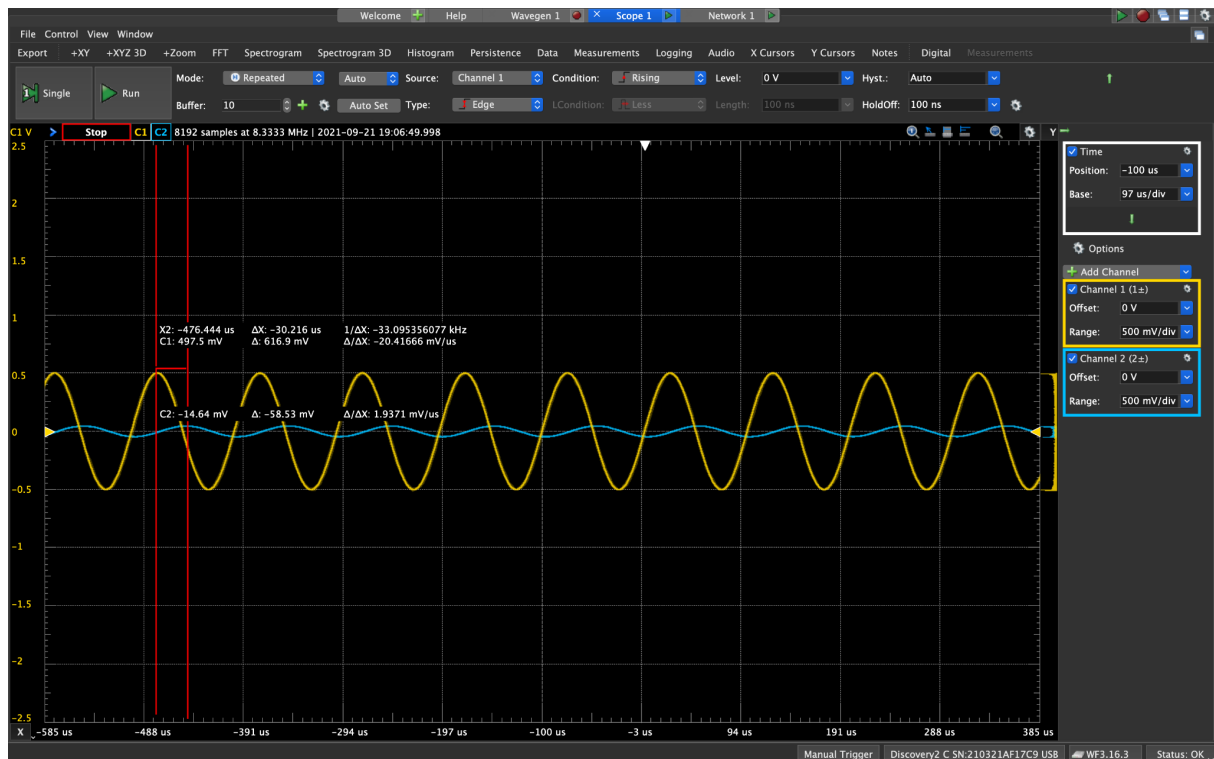


Circuit B- high pass

Bode Plot

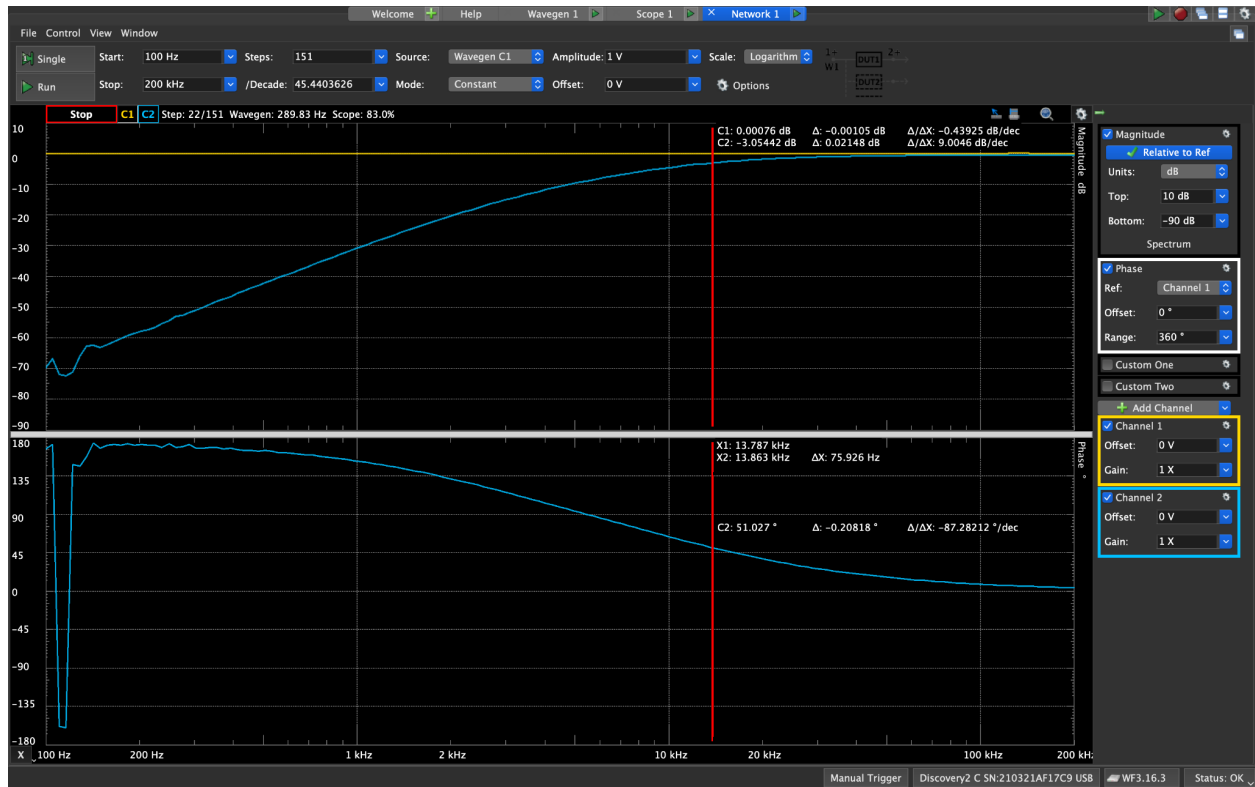


Time Domain Plot

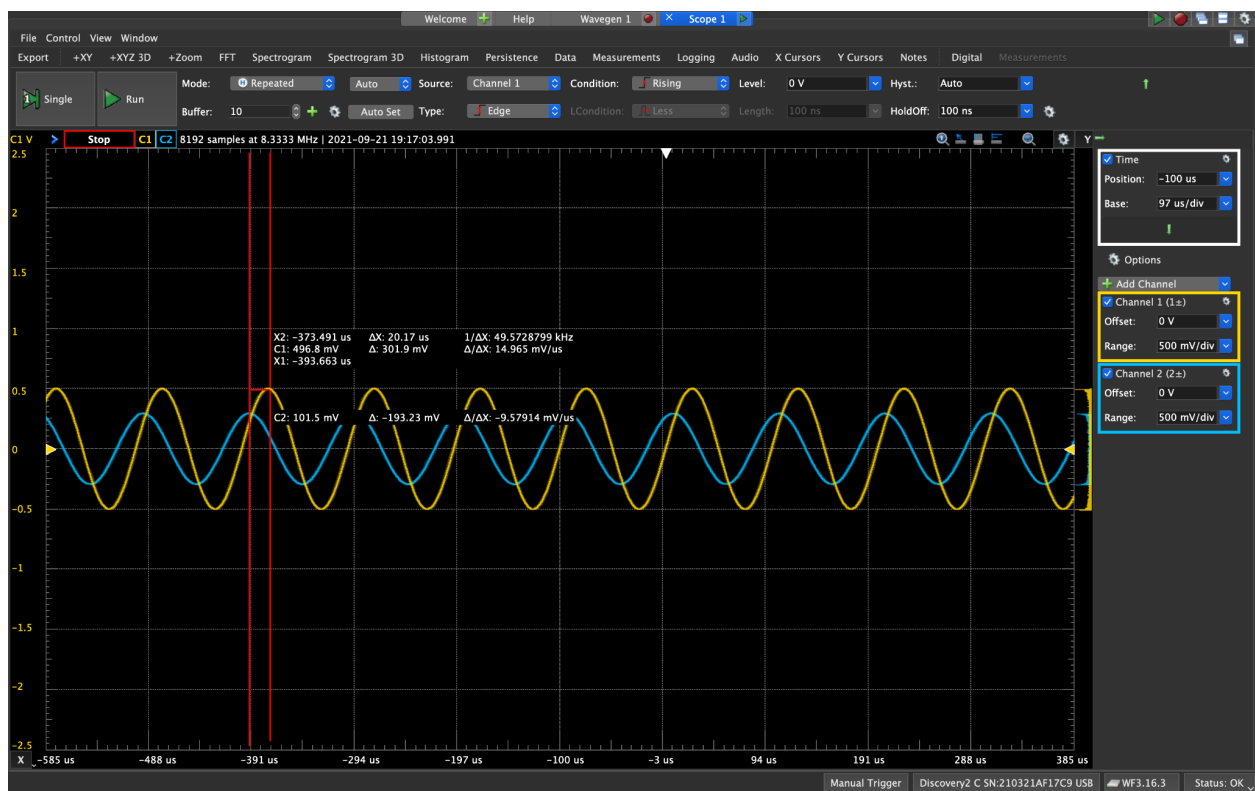


Circuit C-bandpass filter

Bode Plot

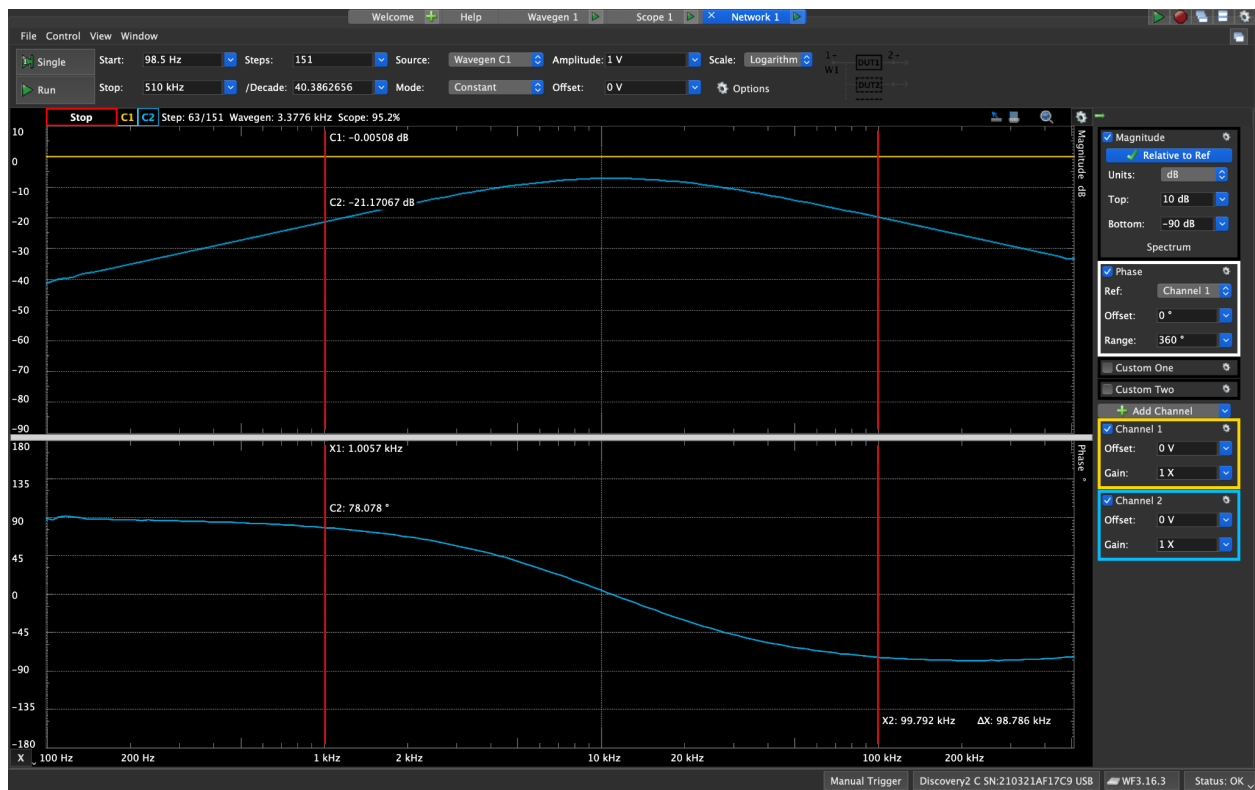

Time Domain Plot

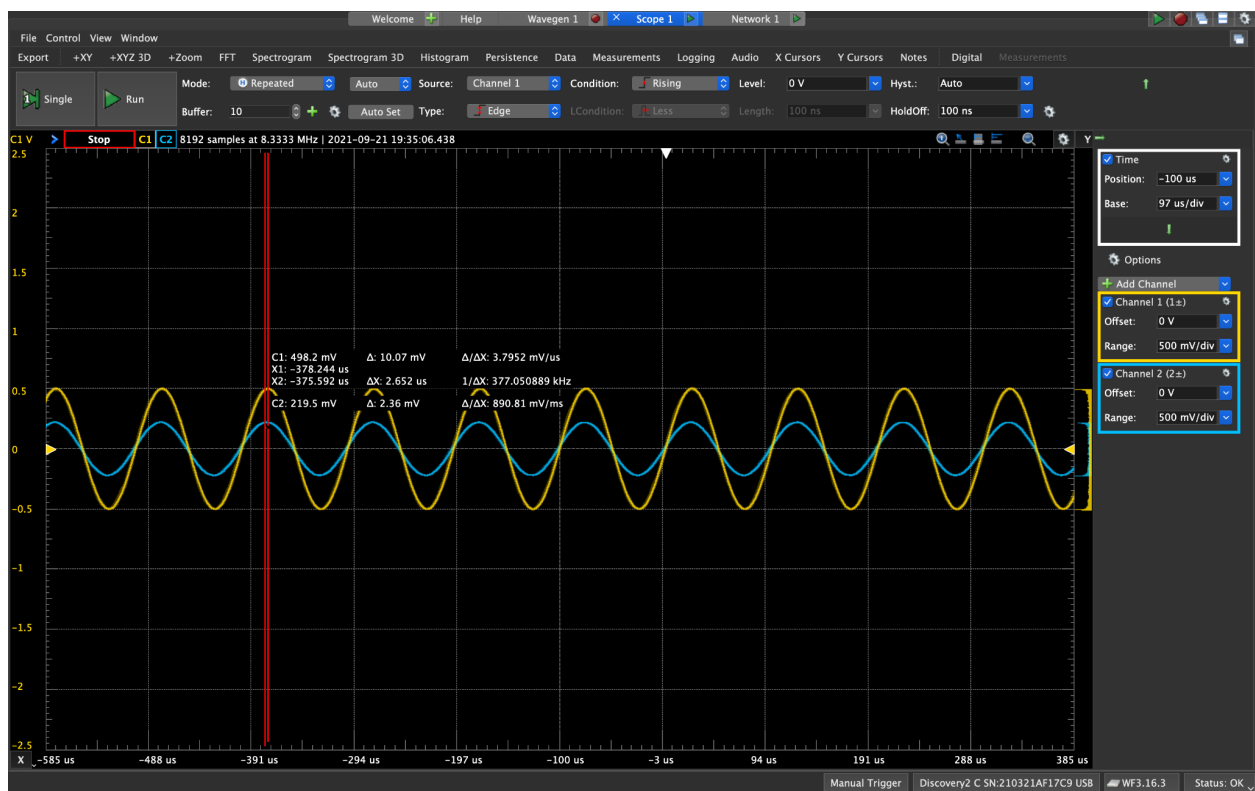

Data Tables

	Time Difference	$\angle H$	H
Calculation Circuit A	N/A	-132.37°	0.176V
Calculation Circuit B	N/A	129.28°	123mV
Calculation Circuit C	N/A	5.14°	0.497V
Simulation Circuit A	-10.08	-36.288°	394.1mV
Simulation Circuit B	15.81	56.916°	269.3mV
Simulation Circuit C	0	0°	497mV
Measurements Circuit A	-30.216	-108.778°	-14.64mV
Measurements Circuit B	20.17	72.612°	101.5mV
Measurements Circuit C	2.65	9.54°	219.5mV

Discussion

The values I got for my simulations were slightly different from my measurements, but this could be because of the breadboard, or the sensitivity of the Analog Discovery. For some, I had to make a series for the resistors or use resistors that were closest to the calculated values because of limited materials. When it came to calculating the component values, I utilized the transfer function, but the resistance values were either too small or too large to actually use a resistor of the exact resistance value, hence why the calculated component values may be different from the measurement values.