

## Pre-Lab 7: Characterization and DC Biasing of the BJT


ECEN 325 - 511

TA: Zhiyong Zhang

Due Date: October 26, 2021

## Calculations

1) NPN

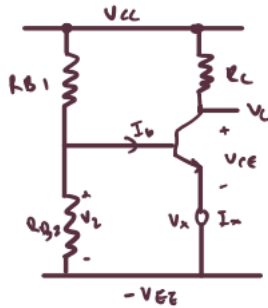

$$V_{CC} = 5V$$

$$V_C = 3.5V$$

$$I_C = 1mA$$

$$V_C = I_C R_C - V_{CC}$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 3.5}{1mA} = \underline{1.5k\Omega}$$

$$R_E = \frac{V_{RE}}{I_E} \rightarrow I_E = (1 + \beta) I_B = (1 + \beta) (I_C / \beta)$$

$$I_E = (101) \frac{1mA}{100} = \underline{1.01mA}$$

$$I_B = I_E - I_C = \underline{0.01mA}$$

$$V_C = V_{RE} + V_{RC} = \underline{3.5V}$$

$$V_{RC} = R_C (I_C) = 1.5k(1mA) = 1.5V$$

$$V_{RC} = 1.5V \rightarrow V_{RE} = \underline{2V}$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2V}{1.01mA}$$

$$R_E = \underline{1.98k\Omega} \approx 2k\Omega$$

$$I_{supply} = 2mA = I + I_C \quad I = 1mA$$


$$V_{B1} + V_{B2} = V_{CC} \rightarrow V_{B2} = 0.7 + V_{RE} = 2.7V$$

$$V_{B1} = 5 - 2.7 = 2.3V$$

$$V_{B1} = I R_{B1} = 2.3 = 1mA(R_{B1}) \rightarrow \underline{R_{B1} = 2.3k\Omega}$$

$$V_{B2} = (\beta + 1) I_B = (2.7)(0.99mA) = \underline{R_{B2} = 2.7k\Omega}$$

1) PNP

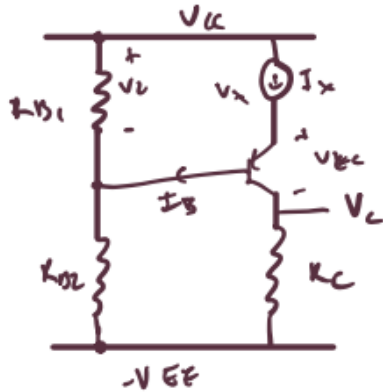

$$V_{EE} = 0V$$

$$V_C = 1.5V$$

$$I_C = 1mA$$

$$R_C = \frac{V_C - V_{EE}}{I_C} = \frac{1.5V}{1mA} = 1.5k\Omega$$

$$I_B = I_C / \beta = \frac{1mA}{100} = 0.01mA$$

$$I_E = I_B + I_C = \underline{1.01mA}$$

$$V_{RE} = V_{CC} - V_{RC} - V_C = 5 - 1.5 - 1.5 = 2V$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2V}{1.01mA} = 1.98k\Omega = 2k\Omega$$


$$V_{R1} + V_{R2} = V_{CC} \rightarrow V_{R2} = 5 - 2.7 = 2.3V$$

$$I_{supply} = I + I_E = 2mA \quad I = 2mA - 1.01mA = 0.99mA$$

$$R_{B2} = \frac{V_{R2}}{I} = \frac{2.3V}{0.99mA} = \underline{2.32k\Omega}$$

$$R_{B1} = \frac{V_{R1}}{I + I_{B1}} = \frac{2.7V}{1mA} = \underline{2.7k\Omega}$$

2) NPN

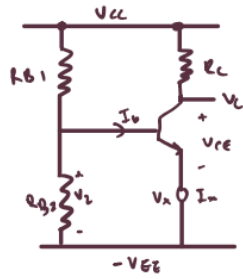


$$I_C = 2 \text{ mA}$$

$$V_C = 3.5 \text{ V}$$

$$V_{CE} \geq 1 \text{ V}$$

$$V_X \geq 1.5 \text{ V}, \quad V_{CC} = 5, \quad V_{EE} = 0$$
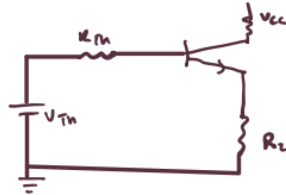
$$\beta = 100, \quad V_T = 25 \text{ mV}, \quad I_{\text{supply}} \leq 5 \text{ mA}$$



$$V_{TH} = V_{CC} \left( \frac{R_2}{R_{B1} + R_{B2}} \right)$$

$$R_{TH} = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}}$$

$$V_{CC} = I_C R_C + V_C \rightarrow R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 3.5}{2 \times 10^{-3}} = 0.75 \text{ k}\Omega = 750 \Omega$$

$$V_{TH} = V_{BE} + I_B R_{TH} + V_{CE} = 0.7 + 20 \times 10^{-6} (R_{TH}) + 1.5 = 2.2 \text{ V}$$

$$V_C \geq 1.5 \text{ V}$$

$$I_B = I_C / \beta = 2 / 100 = 20 \mu\text{A}$$

$$I_C \approx I_E = 2 \text{ mA}$$

$$V_{TH} = V_{CE} \left( \frac{R_2}{R_{B1} + R_{B2}} \right)$$

$$2.2 = 5 \left( \frac{R_2}{R_1 + R_2} \right)$$


$$2.2 (R_1 + R_2) = 5 R_2$$

$$R_1 = 1.27 R_2$$

$$R_{B2} = 1 \text{ k}\Omega \quad R_{B1} = 1.27 \text{ k}\Omega$$


$$R_1 = R_2 = R_3 = 500 \Omega$$

2) PNP

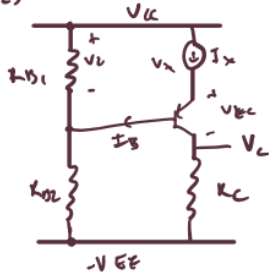

$$\begin{aligned} I_C &= 2 \text{ mA} \\ V_C &= 1.5 \text{ V} \\ V_{EC} &= 2 \text{ V} \\ V_{CE} &= 1 \text{ V} \\ V_{CC} &= 5 \text{ V} \\ V_{EE} &= 0 \text{ V} \end{aligned}$$
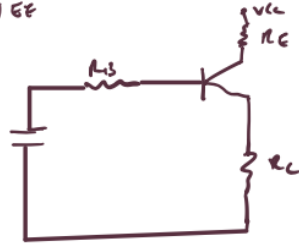
$$\begin{aligned} \beta &= 100 \\ V_T &= 25 \text{ mV} \end{aligned}$$



$$V_C = V_{CC} - V_{EC} - V_C = 5 - 1.5 - 1 = 2.5 \text{ V}$$

$$V_C = 2.5 \text{ V}$$

$$I_E = I_C = 2 \text{ mA}$$

$$R_E = \frac{V_C}{I_E} = \frac{2.5}{2 \times 10^{-3}} \quad R_E = 1.25 \text{ k}\Omega$$

$$R_C = \frac{V_C}{I_C} = \frac{1.5}{2 \times 10^{-3}} \quad R_C = 0.75 \text{ k}\Omega$$

$$V_C = V_C + 0.7 \rightarrow 2.5 + 0.7 \quad V_C = 3.2 \text{ V}$$

$$V_C = \left( \frac{R_1}{R_1 + R_2} \right) V_{CC} \rightarrow 3.2 = \left( \frac{R_1}{R_1 + R_2} \right) 5$$


$$R_1 = 1.77 R_2$$

$$\begin{aligned} R_2 &= 1 \text{ k}\Omega \\ R_1 &= 1.77 \text{ k}\Omega \end{aligned}$$


$$R_1 \approx R_2 + R_3 = 500 \Omega$$

## Simulations (on Multisim)


### *Schematic NPN*

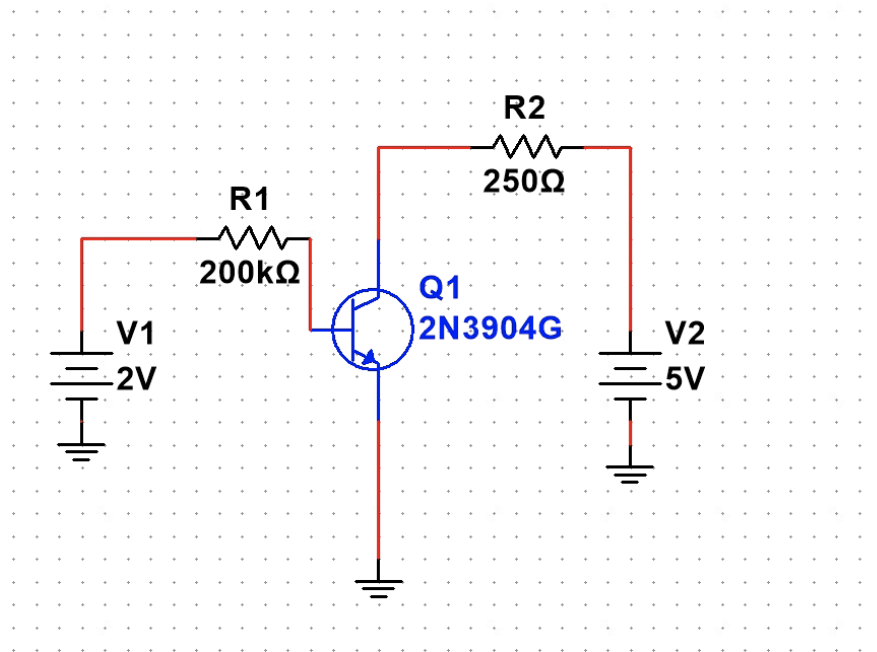


$I_C$  vs  $V_{BE}$

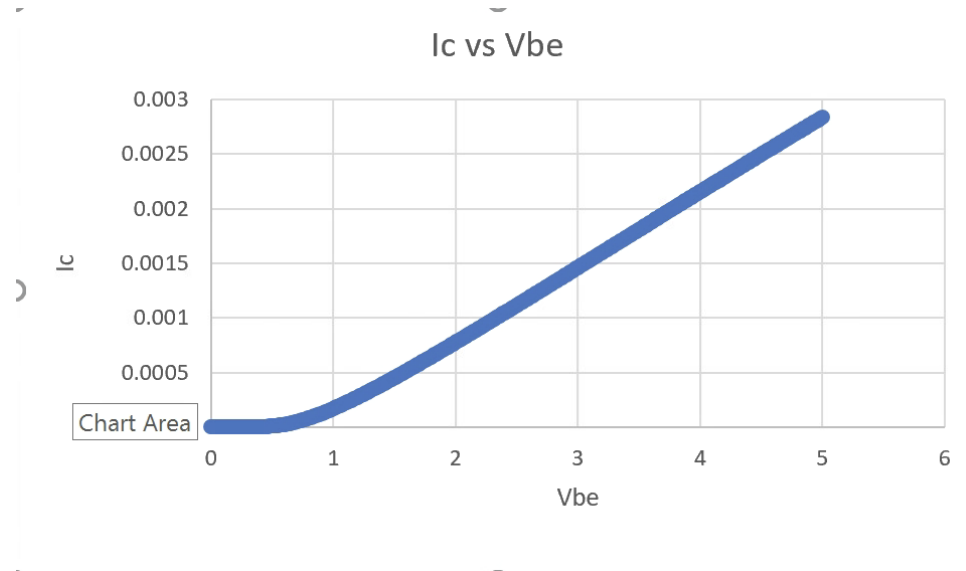


$I_c$  vs  $V_{CE}$

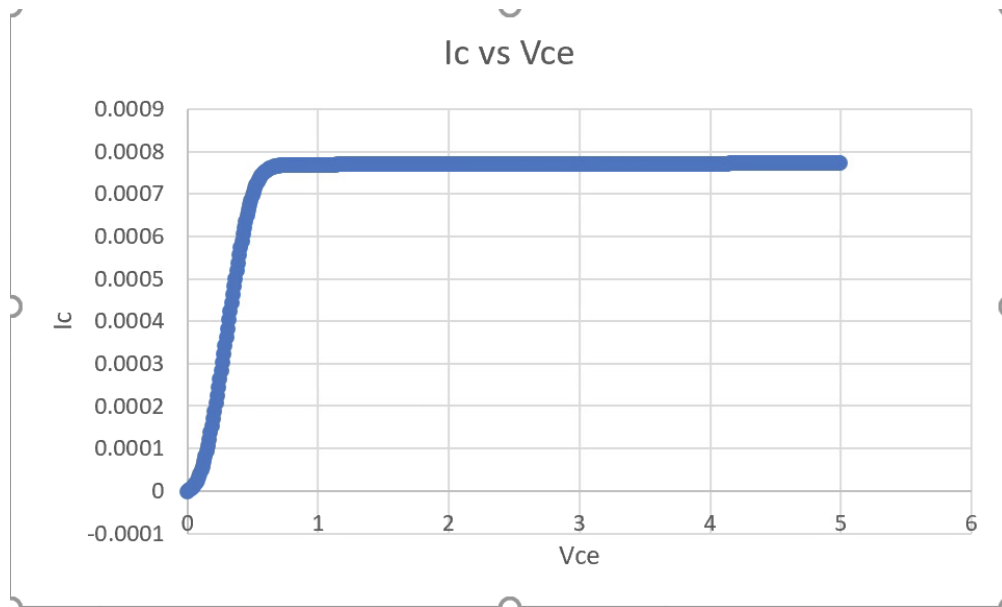


*Schematic PNP*

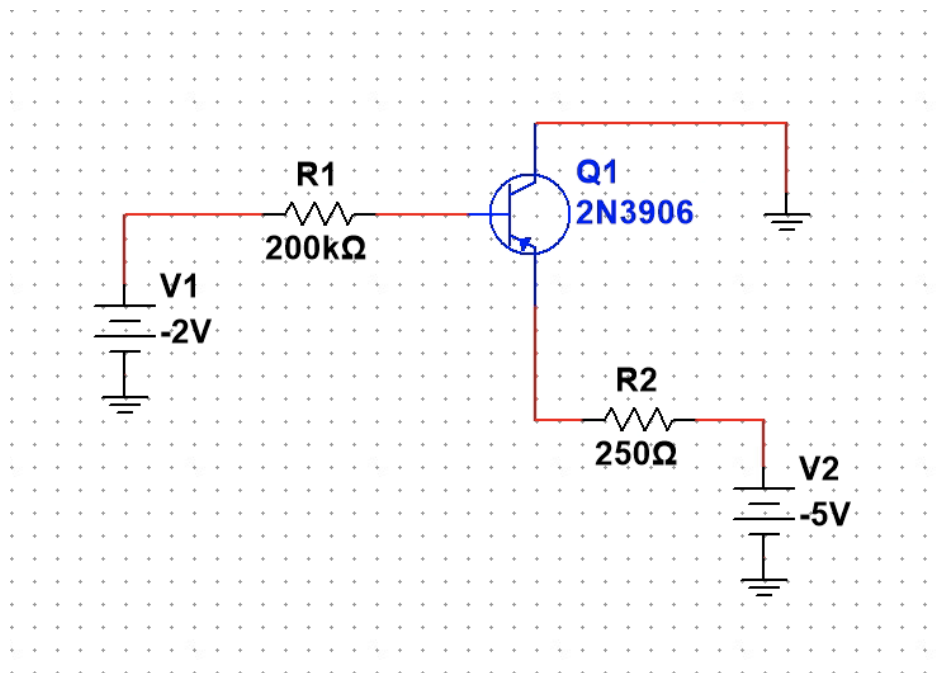

$I_c$  vs  $V_{EB}$

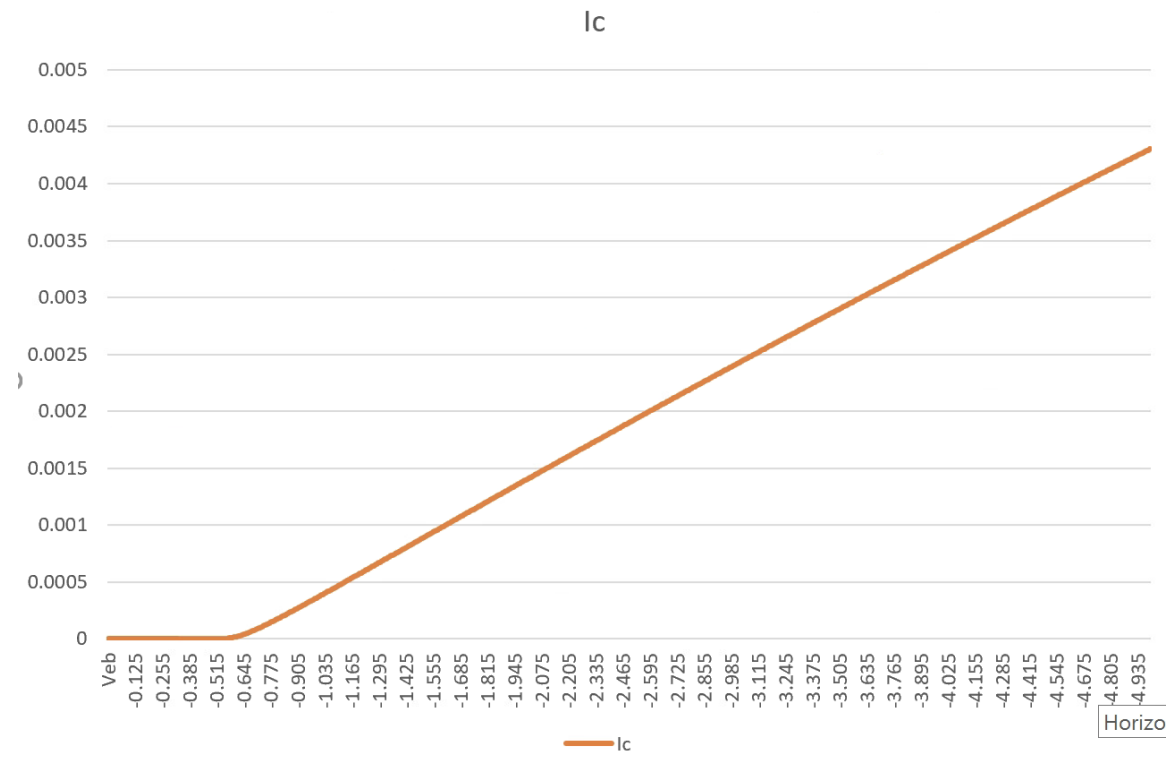


$I_c$  vs  $V_{EC}$

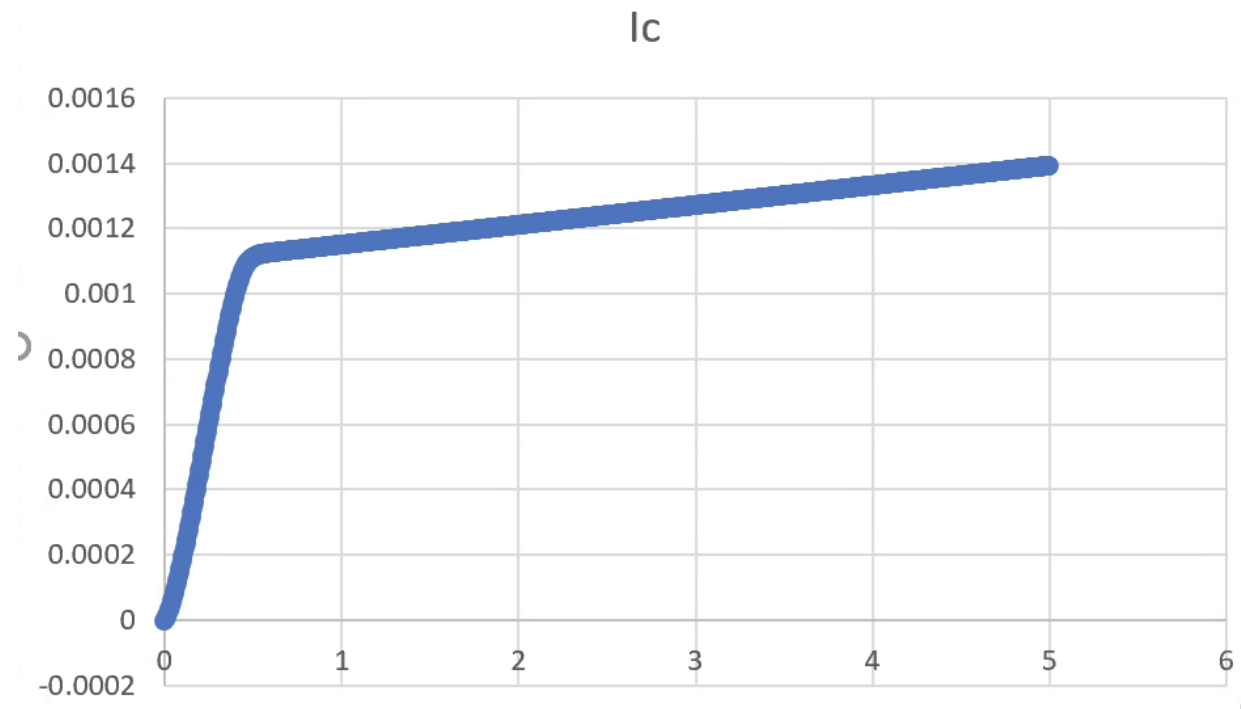





**Schematic 6a**

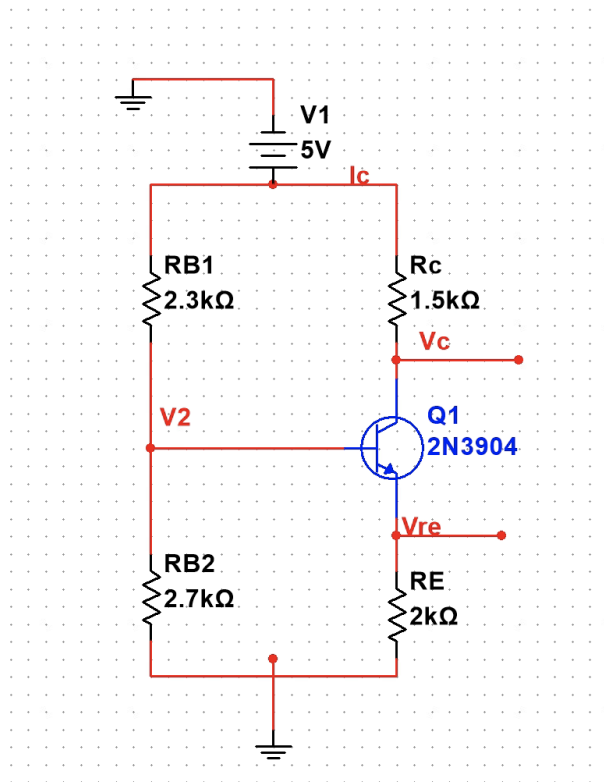


**DC operating point or interactive simulation for 6a**

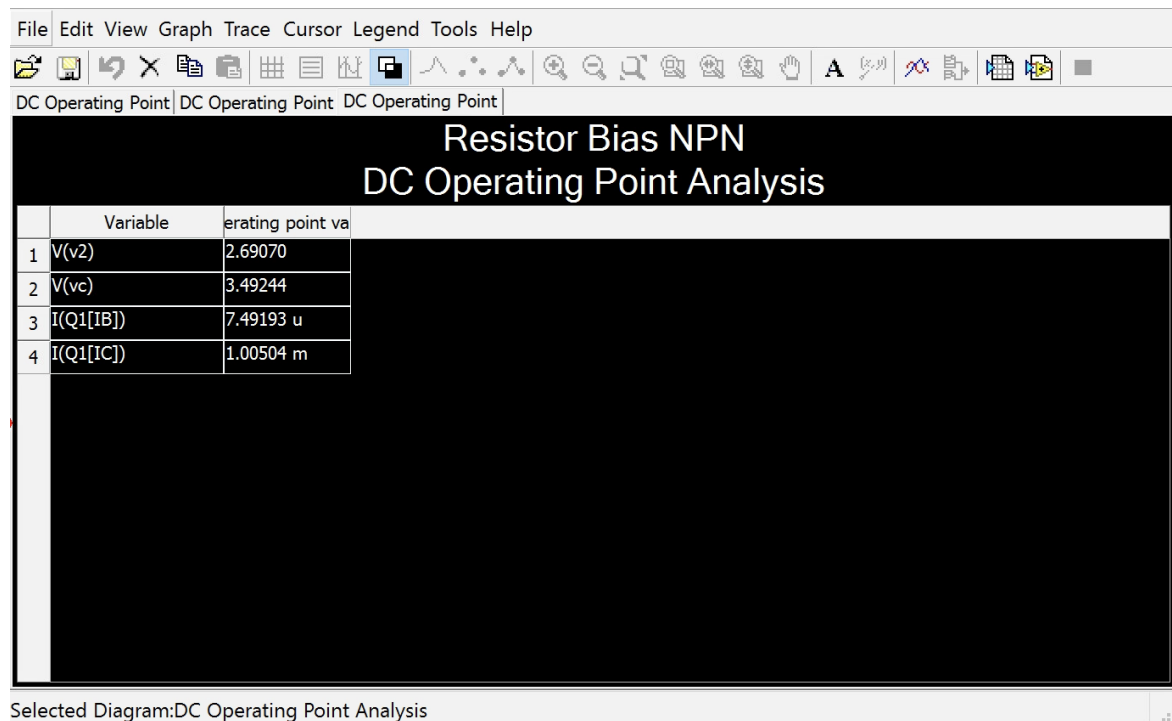


*Schematic 6b*

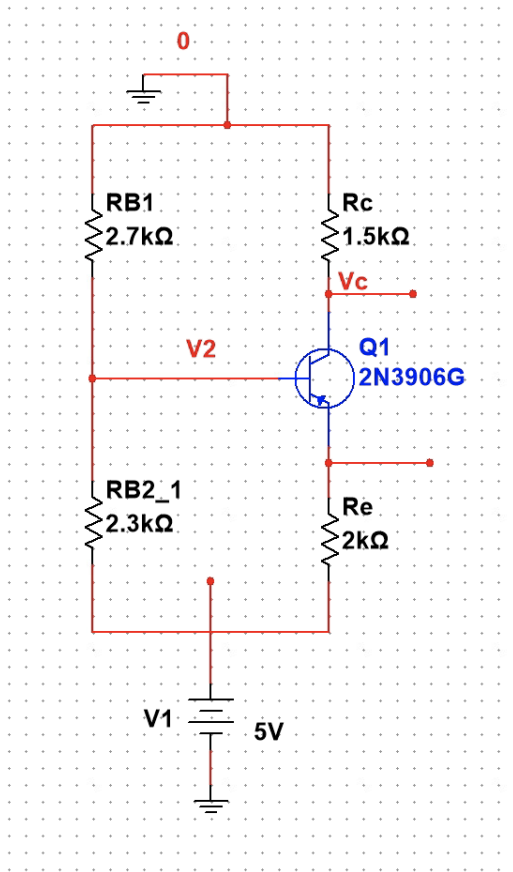


*DC operating point or interactive simulation for 6b*

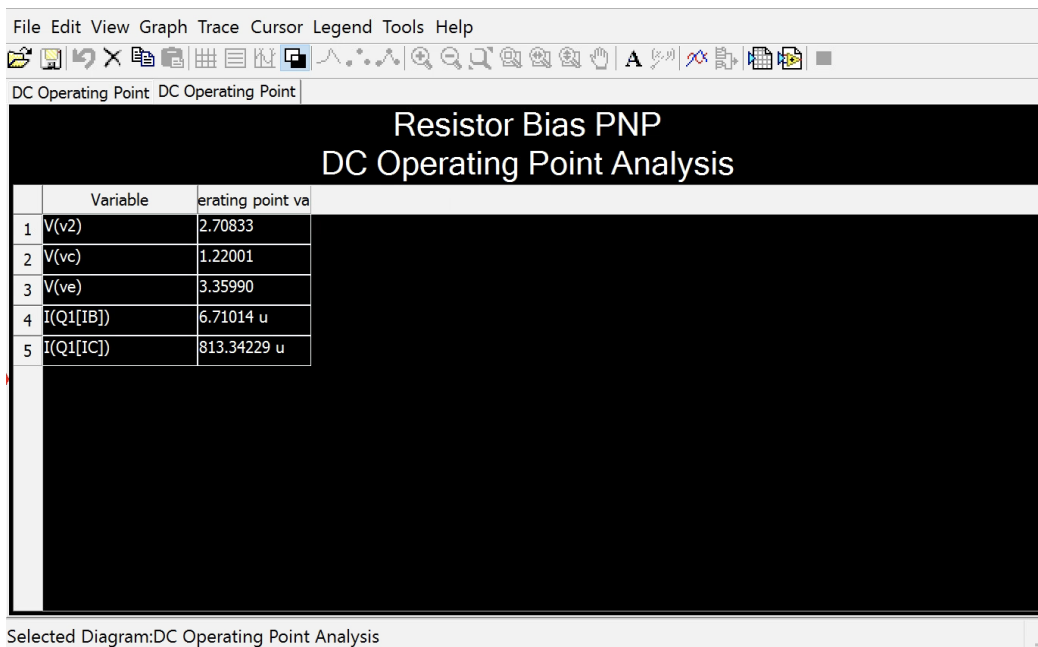


Schematic 7a

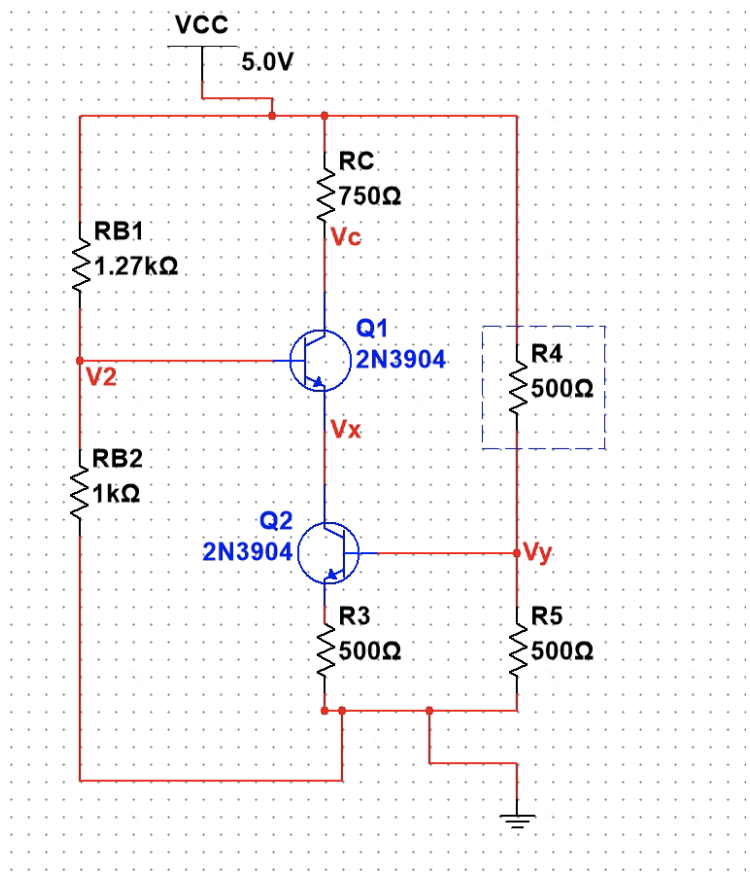

DC operating point or interactive simulation for 7a

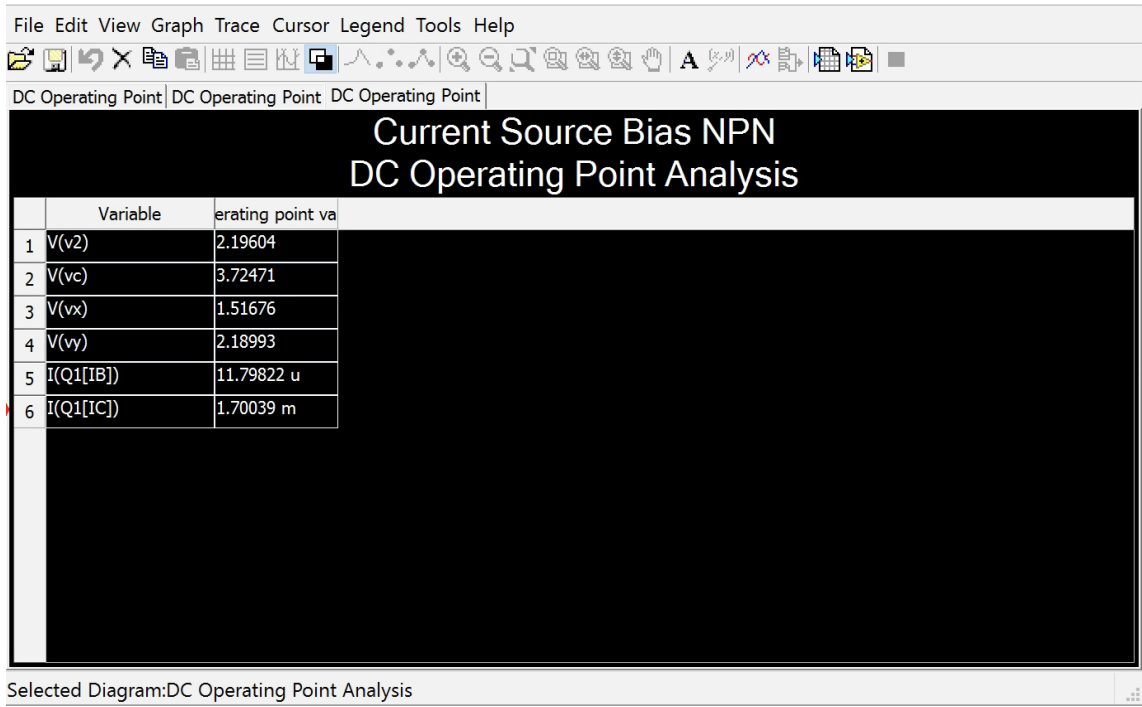

Schematic 8a

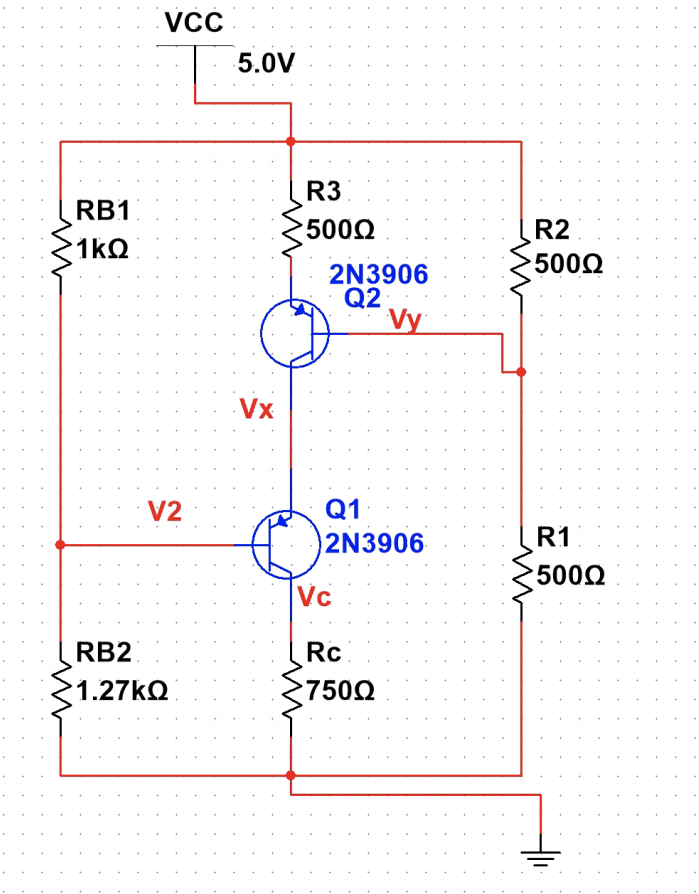

DC operating point or interactive simulation for 8a

