

Lab 6: Diodes

ECEN 325 - 511

TA: Zhiyong Zhang


Date Performed: October 19, 2021

Due Date: October 26, 2021

Purpose

The purpose of this lab was to learn about the basic properties of semiconductor diodes. These characteristics include switching behavior, and rectification properties are examined, which leads to the construction of a DC power supply.

Calculations

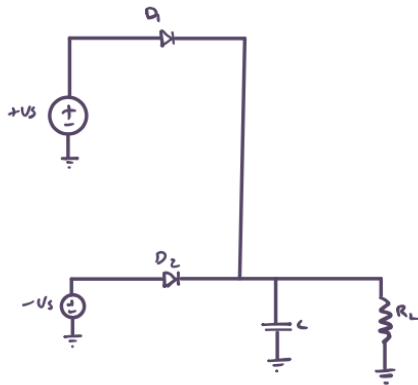

Output should be $3V (V_m)$
 $I_m = 3mA$
 10% of max ripple,
 $f = 250Hz$
 $V_d = 0.7V$

$$\text{Load Resistance} = \frac{V_m}{I_m} = \frac{3V}{0.003A} = \boxed{R_L = 1k\Omega}$$

$$V_r = 0.1 \times 3V = \underline{0.3V}$$

$$V_p = 3 + 0.3 = \underline{3.3V}$$

$$V_s = V_p + V_d = 3.3 + 0.7 = 4V$$

$$\boxed{V_s = 4V}$$


so $C = \frac{1}{2fV_r k}$ where $k = 0.1$

$$C = \frac{1}{2 \times 0.1 \times 1000 \times 250}$$


$$\boxed{C = 20\mu F}$$

Simulations (on Multisim)


Schematic

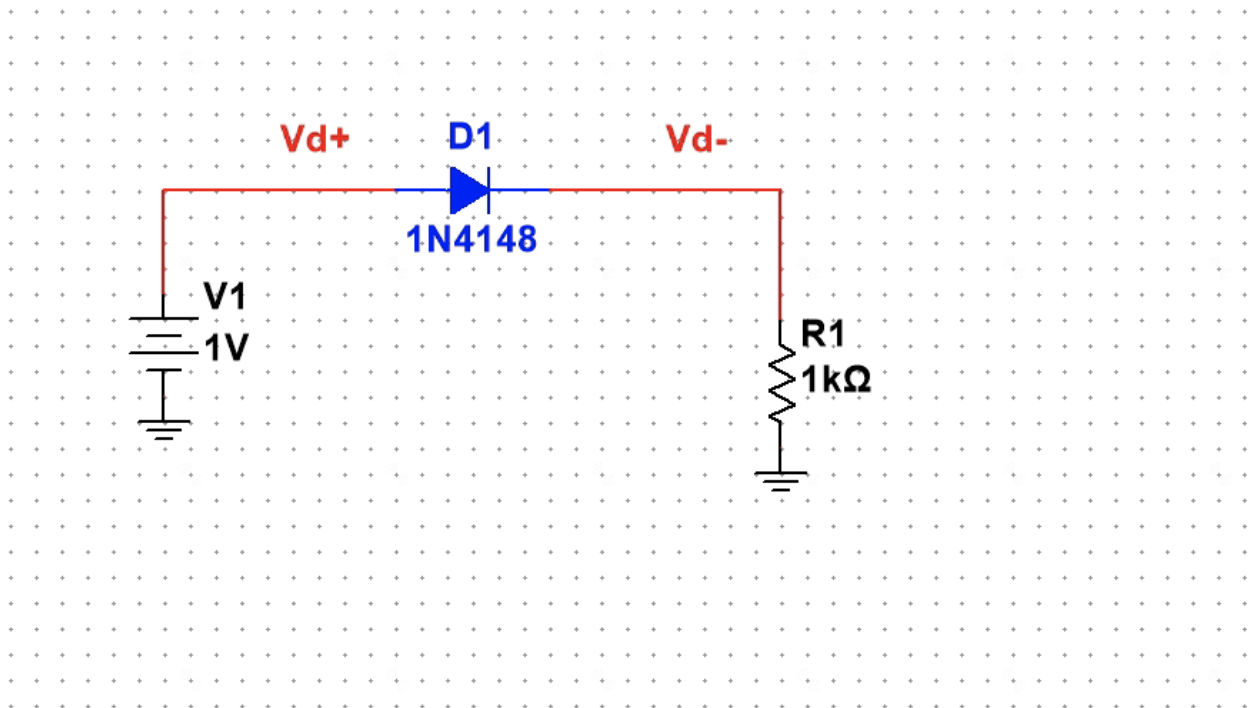


Plot

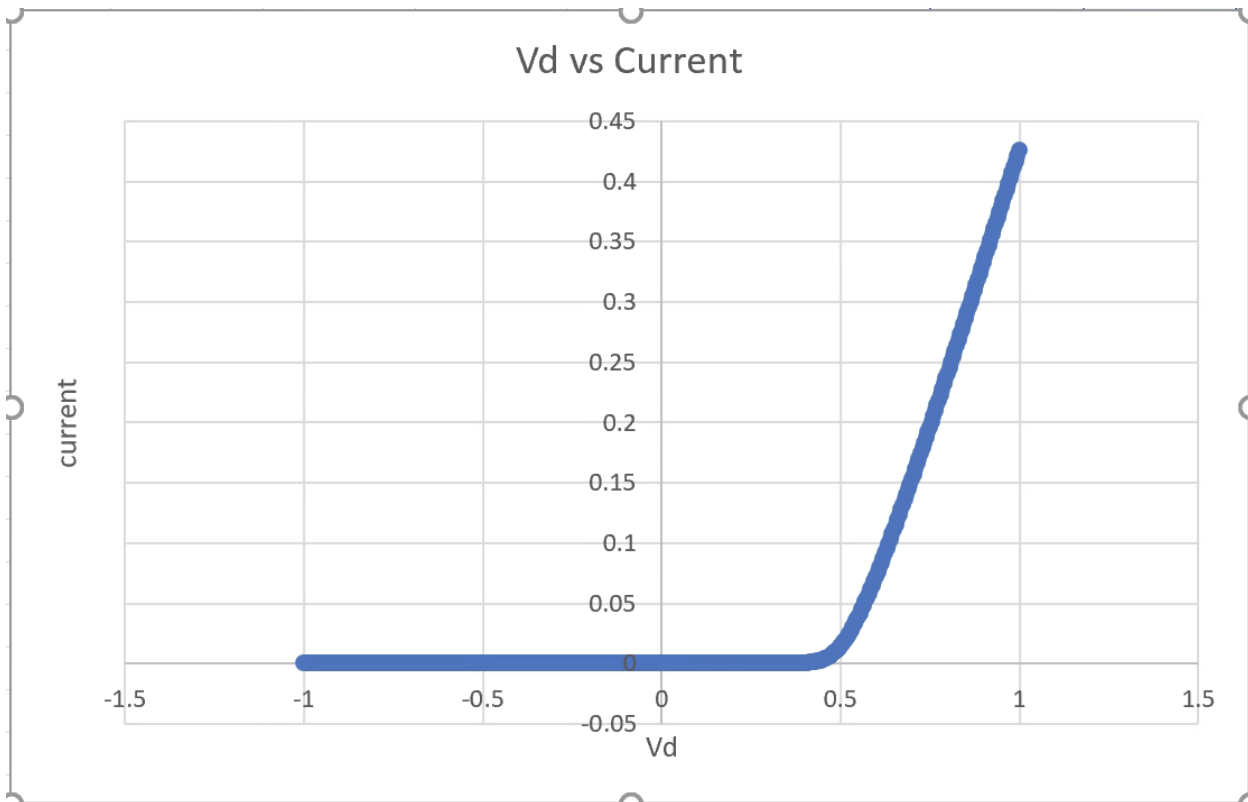

Schematic

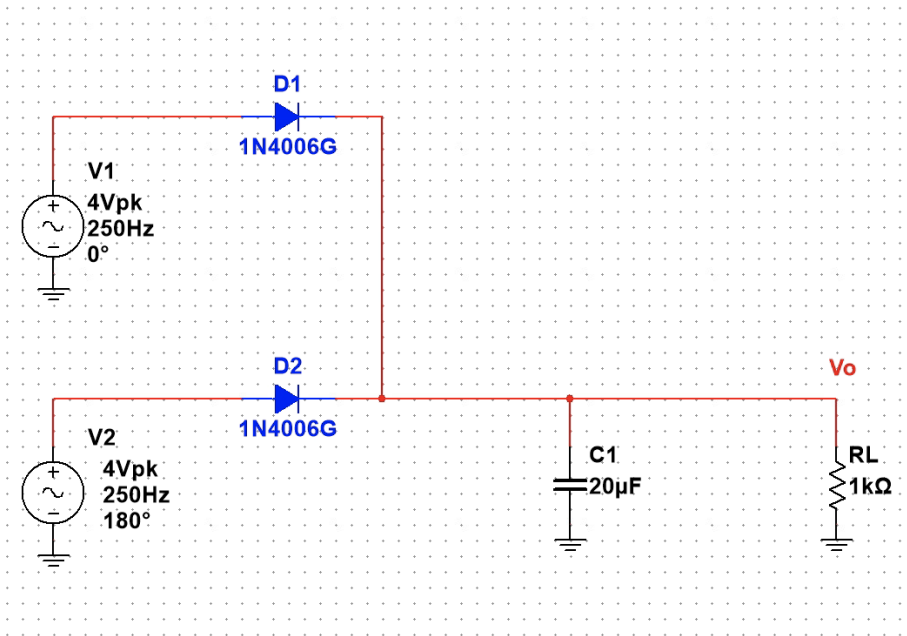

Transient

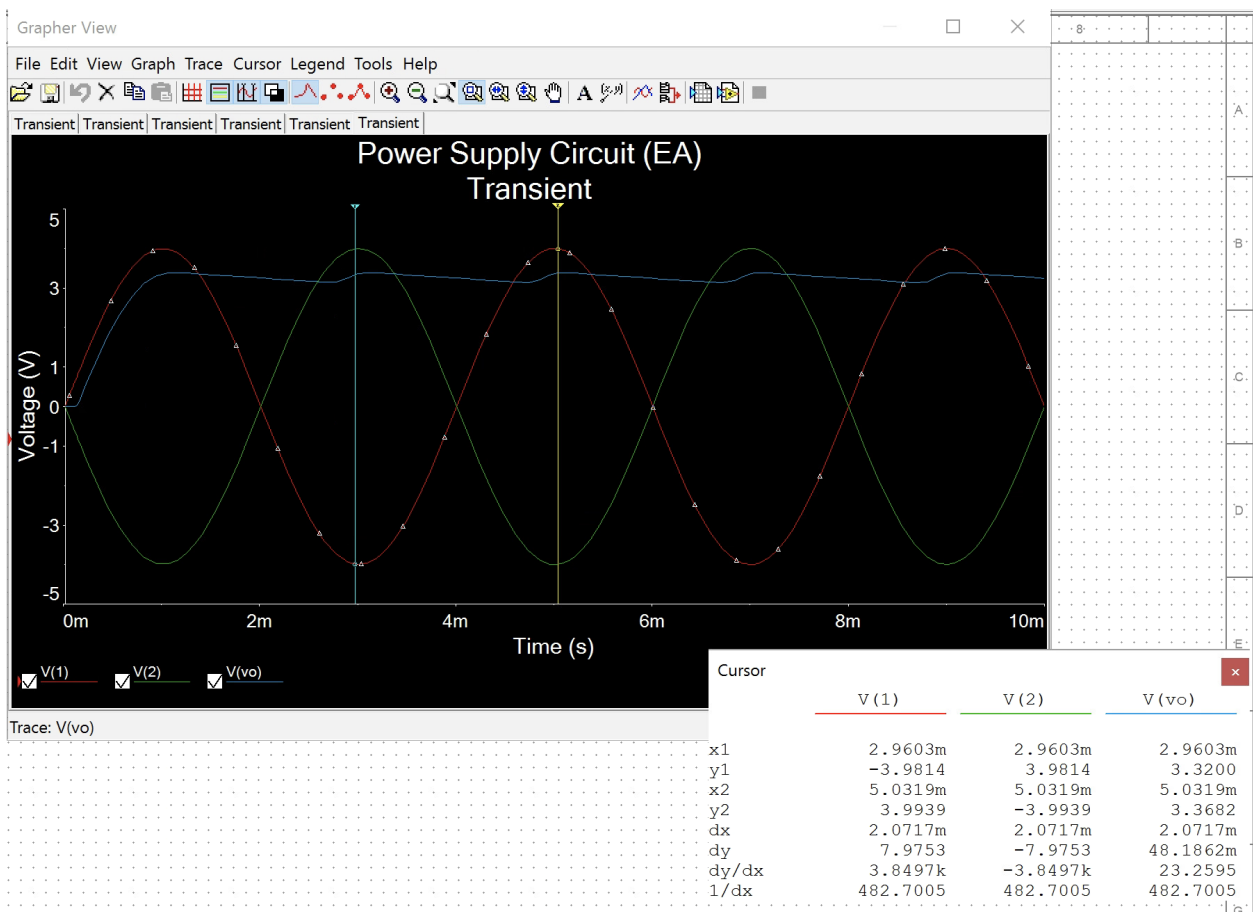

Measurements

Figure 2a Scope Measurements


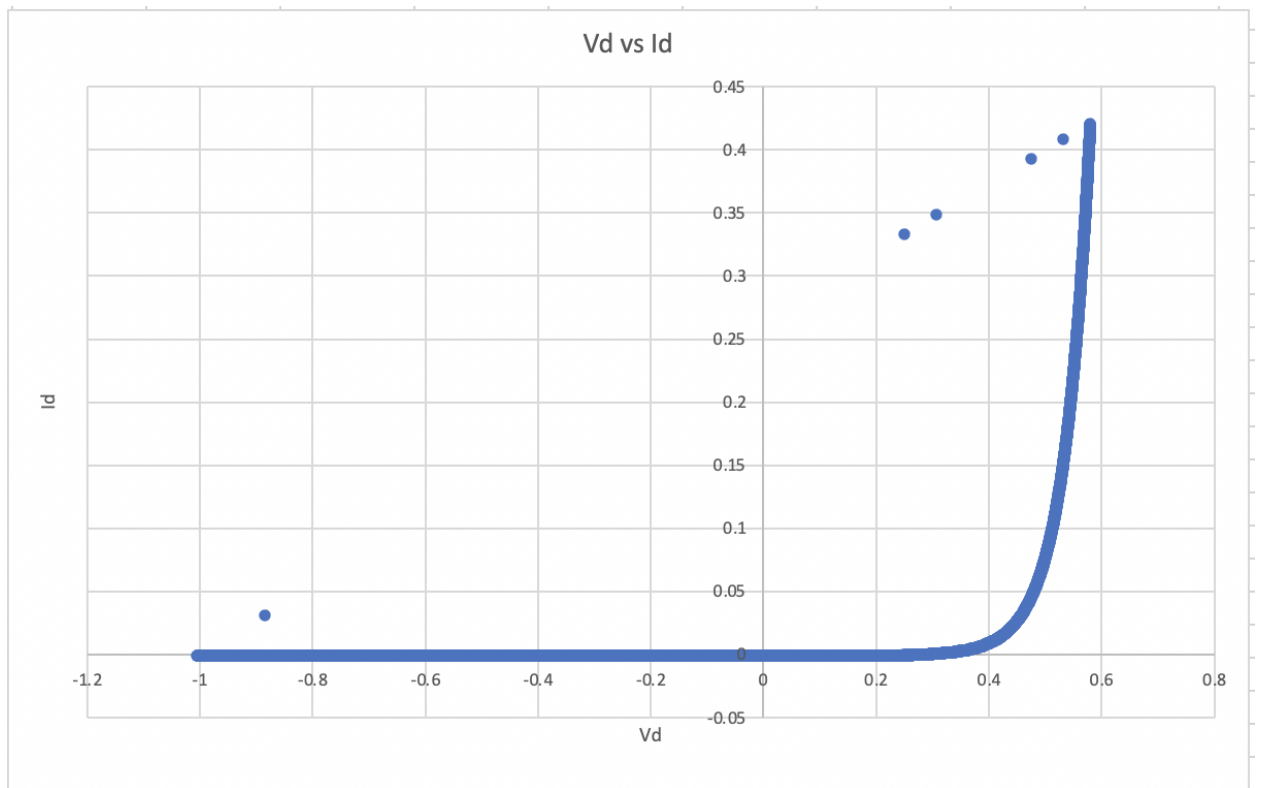
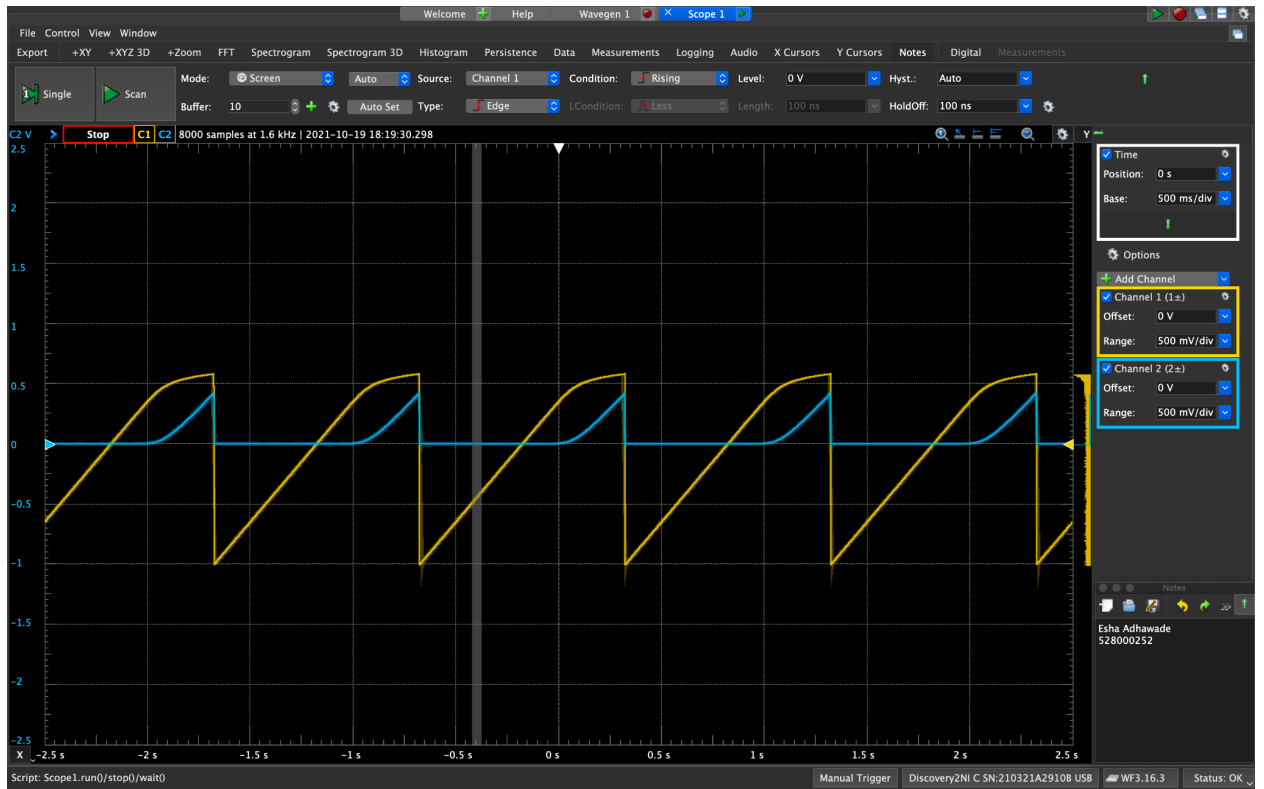


Figure 5 Scope

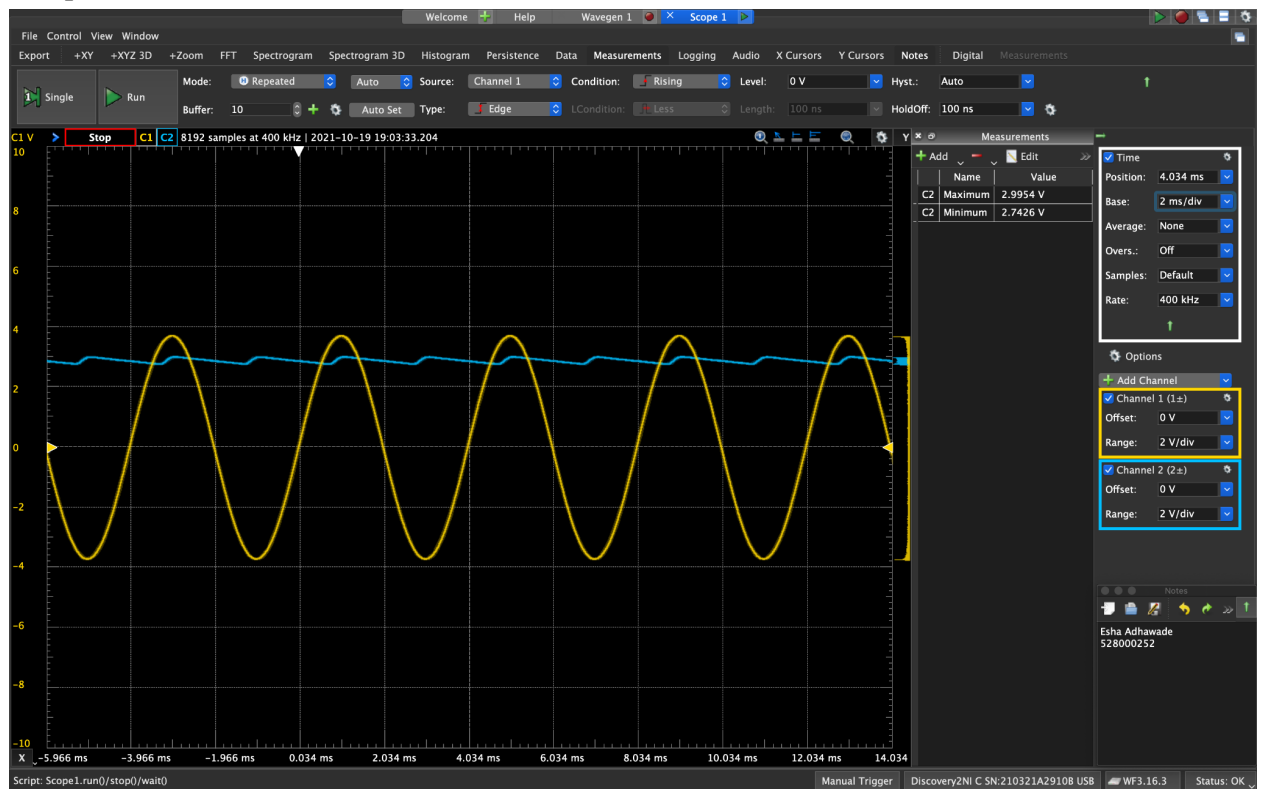

Data Tables

	Calculations	Simulations	Measurements
Peak Output voltage	3.3 V	3.3682 V	2.9954 V
Ripple voltage	300 mV	0.49 V	0.601 V

Discussion

For lab 6, students learned about the basic properties of semiconductors diodes. Most of the values between the simulations and measurements were pretty consistent for the circuits. If there were any minor differences, that's probably because of component differences, old breadboards, or loose wires.