

Lab 7: Characterization and DC Biasing of the BJT

ECEN 325 - 511

TA: Zhiyong Zhang

Date Performed: October 26, 2021


Due Date: November 2, 2021

Purpose

The objective of this lab is to be able to characterize NPN and PNP BJTs and to analyze DC biasing circuits.

Calculations

1) NPN

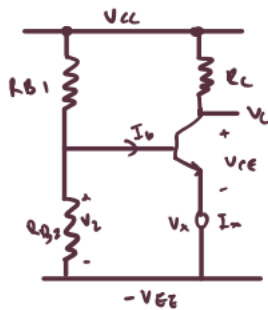

$$V_{CC} = 5V$$

$$V_C = 3.5V$$

$$I_C = 1mA$$

$$V_C = I_C R_C - V_{CC}$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 3.5}{1mA} = 1.5k\Omega$$

$$R_E = \frac{V_{RE}}{I_E} \rightarrow I_E = (1 + \beta) I_B = (1 + \beta) (I_C / \beta)$$

$$I_E = (101) \frac{1mA}{100} = 1.01mA$$

$$I_B = I_E - I_C = 0.01mA$$

$$V_C = V_{RE} + V_{RC} = 3.5V$$

$$V_{RC} = R_C (I_C) = 1.5k(1mA) = 1.5V$$

$$V_{RC} = 1.5V \rightarrow V_{RE} = 2V$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2V}{1.01mA}$$

$$R_E = 1.98k\Omega \approx 2k\Omega$$

$$I_{supply} = 2mA = I + I_C \quad I = 1mA$$


$$V_{B1} + V_{B2} = V_{CC} \rightarrow V_{B2} = 0.7 + V_{RE} = 2.7V$$

$$V_{B1} = 5 - 2.7 = 2.3V$$

$$V_{B1} = I R_{B1} = 2.3 = 1mA(R_{B1}) \rightarrow R_{B1} = 2.3k\Omega$$

$$V_{B2} = (I - I_B) R_{B2} = (2.7)(.99mA) = R_{B2} = 2.7k\Omega$$

1) PNP

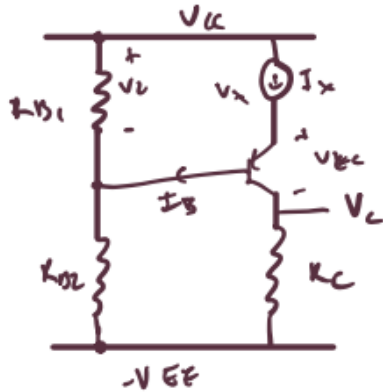

$$V_{EE} = 0V$$

$$V_C = 1.5V$$

$$I_C = 1mA$$

$$R_C = \frac{V_C - V_{EE}}{I_C} = \frac{1.5V}{1mA} = 1.5k\Omega$$

$$I_B = I_C / \beta = \frac{1mA}{100} = 0.01mA$$

$$I_E = I_B + I_C = \underline{1.01mA}$$

$$V_{RE} = V_{CC} - V_{RC} - V_C = 5 - 1.5 - 1.5 = 2V$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2V}{1.01mA} = 1.98k\Omega = 2k\Omega$$


$$V_{R1} + V_{R2} = V_{CC} \rightarrow V_{R2} = 5 - 2.7 = 2.3V$$

$$I_{supply} = I + I_E = 2mA \quad I = 2mA - 1.01mA = 0.99mA$$

$$R_{B2} = \frac{V_{R2}}{I} = \frac{2.3V}{0.99mA} = \underline{2.32k\Omega}$$

$$R_{B1} = \frac{V_{R1}}{I + I_{B1}} = \frac{2.7V}{1mA} = \underline{2.7k\Omega}$$

2) NPN

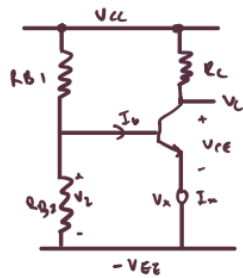


$$I_C = 2 \text{ mA}$$

$$V_C = 3.5 \text{ V}$$

$$V_{CE} \geq 1 \text{ V}$$

$$V_X \geq 1.5 \text{ V}, \quad V_{CC} = 5, \quad V_{EE} = 0$$
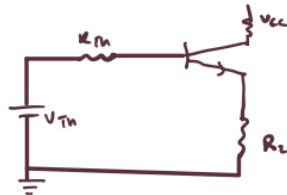
$$\beta = 100, \quad V_T = 25 \text{ mV}, \quad I_{\text{supply}} \leq 5 \text{ mA}$$



$$V_{TH} = V_{CC} \left(\frac{R_2}{R_{B1} + R_{B2}} \right)$$

$$R_{TH} = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}}$$

$$V_{CC} = I_C R_C + V_C \rightarrow R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 3.5}{2 \times 10^{-3}} = 0.75 \text{ k}\Omega = 750 \Omega$$

$$V_{TH} = V_{BE} + I_B R_{TH} + V_{CE} = 0.7 + 20 \times 10^{-6} (R_{TH}) + 1.5 = 2.2 \text{ V}$$

$$V_C \geq 1.5 \text{ V}$$

$$I_B = I_C / \beta = 2 / 100 = 20 \mu\text{A}$$

$$I_C \approx I_E = 2 \text{ mA}$$

$$V_{TH} = V_{CE} \left(\frac{R_2}{R_{B1} + R_{B2}} \right)$$

$$2.2 = 5 \left(\frac{R_2}{R_1 + R_2} \right)$$


$$2.2 (R_1 + R_2) = 5 R_2$$

$$R_1 = 1.27 R_2$$

$$R_{B2} = 1 \text{ k}\Omega \quad R_{B1} = 1.27 \text{ k}\Omega$$


$$R_1 = R_2 = R_3 = 500 \Omega$$

2) PNP

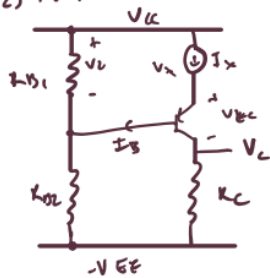

$$\begin{aligned} I_C &= 2 \text{ mA} \\ V_C &= 1.5 \text{ V} \\ V_{BE} &= 2 \text{ V} \\ V_{CE} &= 1 \text{ V} \\ V_{CC} &= 5 \text{ V} \\ V_{EE} &= 0 \text{ V} \end{aligned}$$
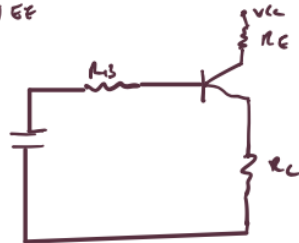
$$\begin{aligned} \beta &= 100 \\ V_T &= 25 \text{ mV} \end{aligned}$$



$$V_C = V_{CC} - V_{CE} - V_{BE} = 5 - 1.5 - 2 = 2.5 \text{ V}$$

$$V_C = 2.5 \text{ V}$$

$$I_E = I_C = 2 \text{ mA}$$

$$R_E = \frac{V_C}{I_E} = \frac{2.5}{2 \times 10^{-3}} \quad R_E = 1.25 \text{ k}\Omega$$

$$R_C = \frac{V_C}{I_C} = \frac{1.5}{2 \times 10^{-3}} \quad R_C = 0.75 \text{ k}\Omega$$

$$V_C = V_C + 0.7 \rightarrow 2.5 + 0.7 \quad V_C = 3.2 \text{ V}$$

$$V_C = \left(\frac{R_1}{R_1 + R_2} \right) V_{CC} \rightarrow 3.2 = \left(\frac{R_1}{R_1 + R_2} \right) 5$$


$$R_1 = 1.77 R_2$$

$$\begin{aligned} R_2 &= 1 \text{ k}\Omega \\ R_1 &= 1.77 \text{ k}\Omega \end{aligned}$$


$$R_1 \approx R_2 + R_3 = 500 \Omega$$

Simulations (on Multisim)


Schematic NPN

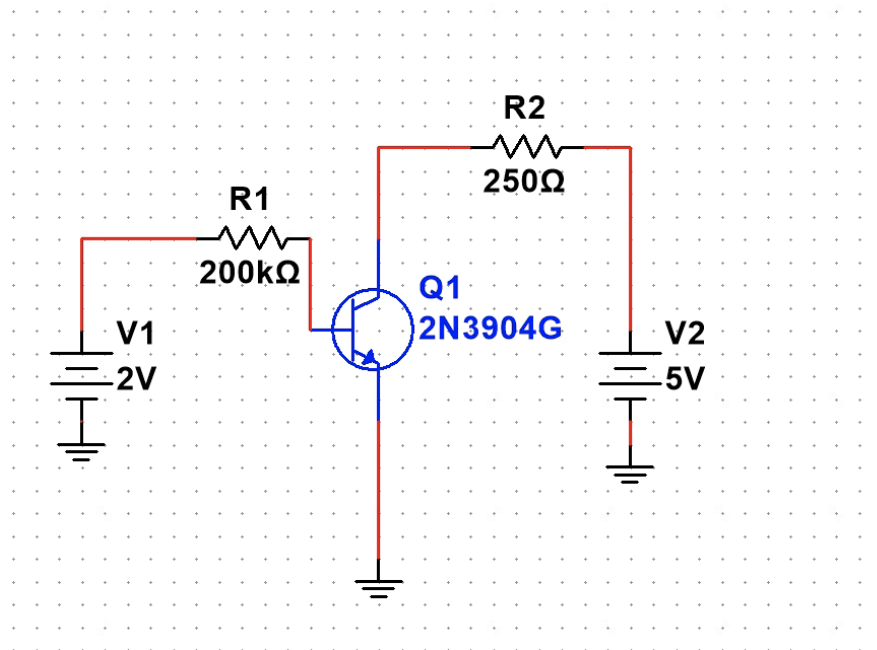


I_c vs V_{BE}

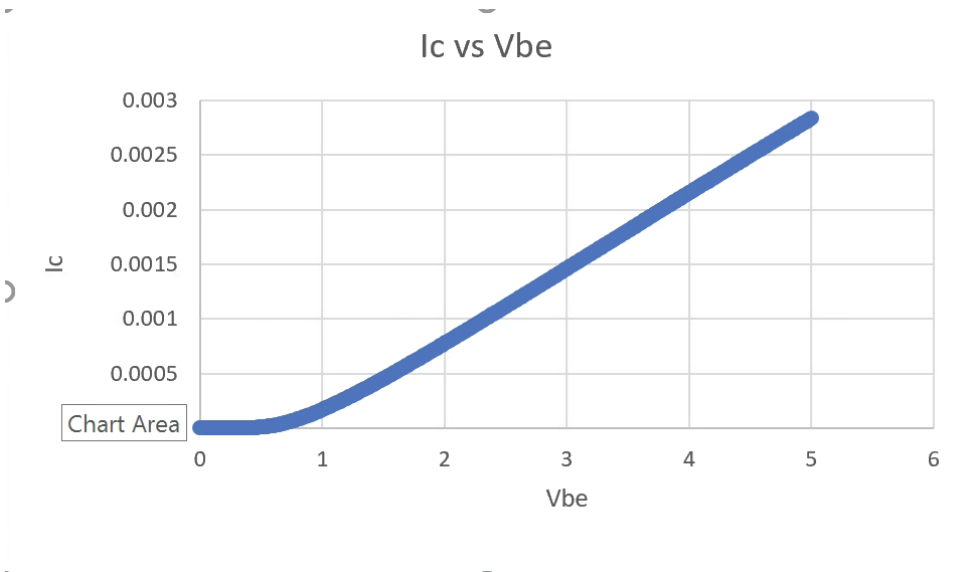


I_c vs V_{CE}

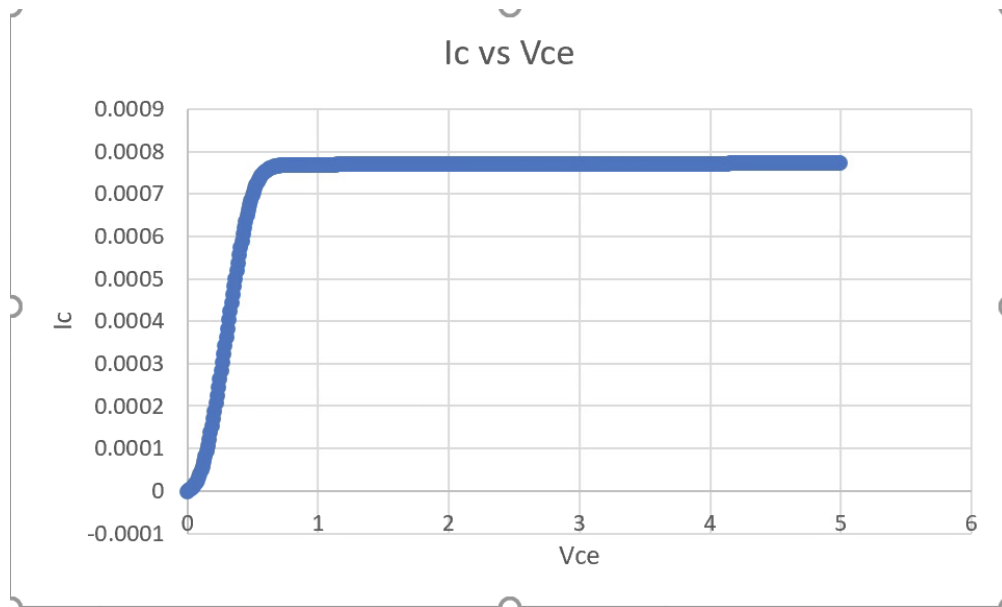


Schematic PNP

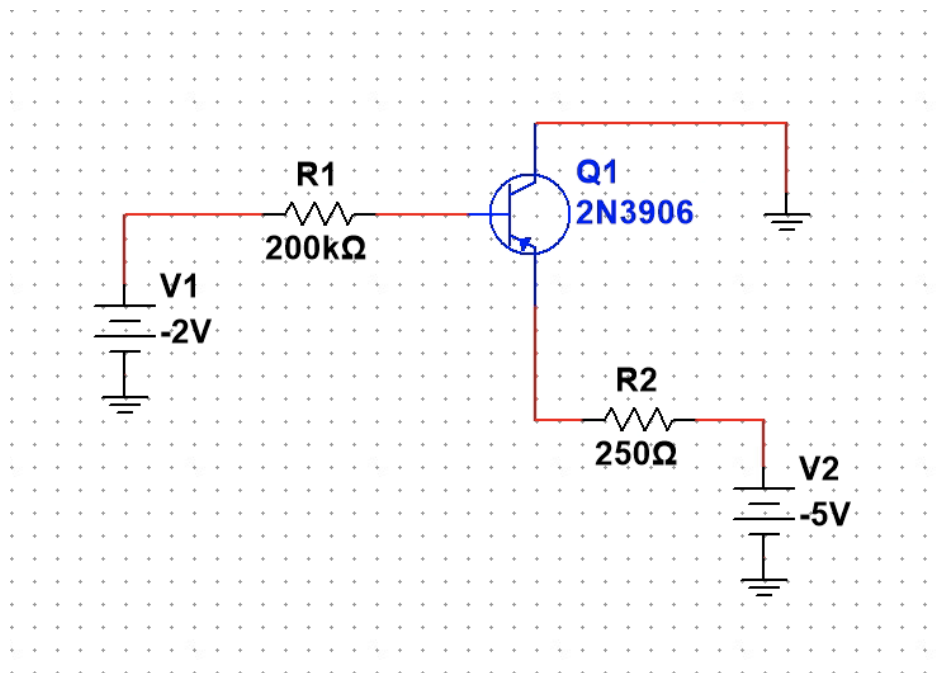


I_c vs V_{EB}

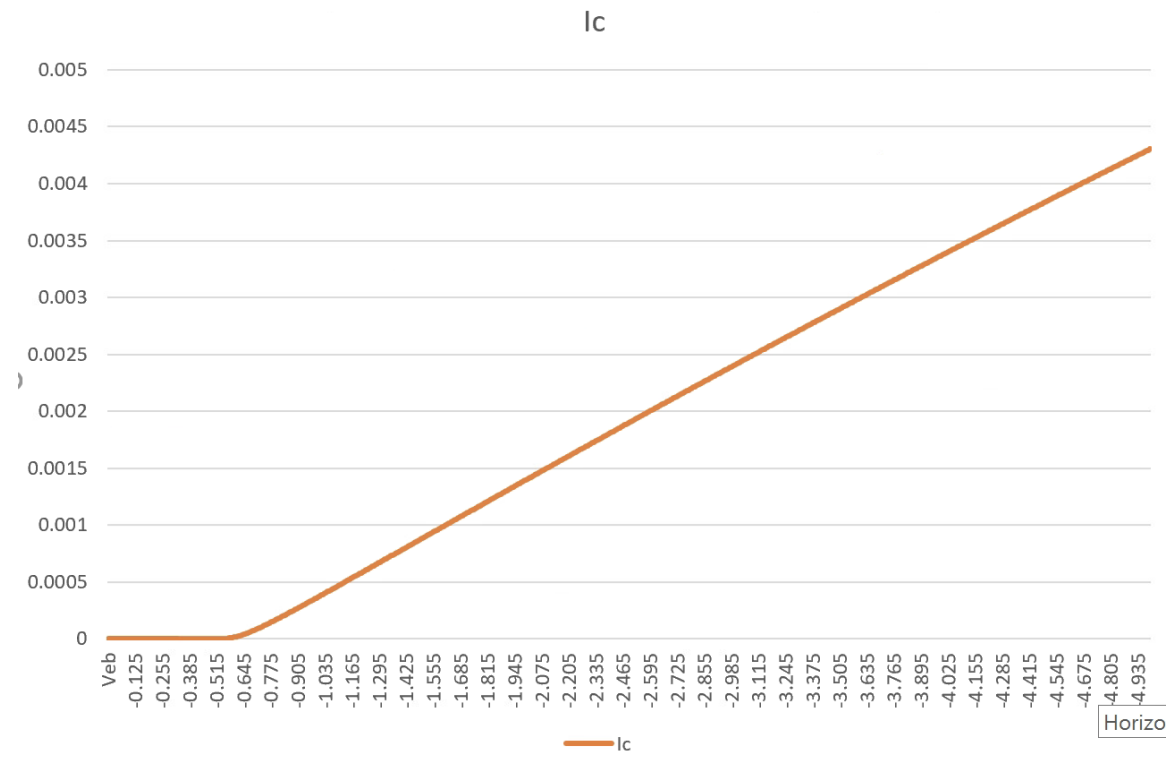


I_c vs V_{EC}

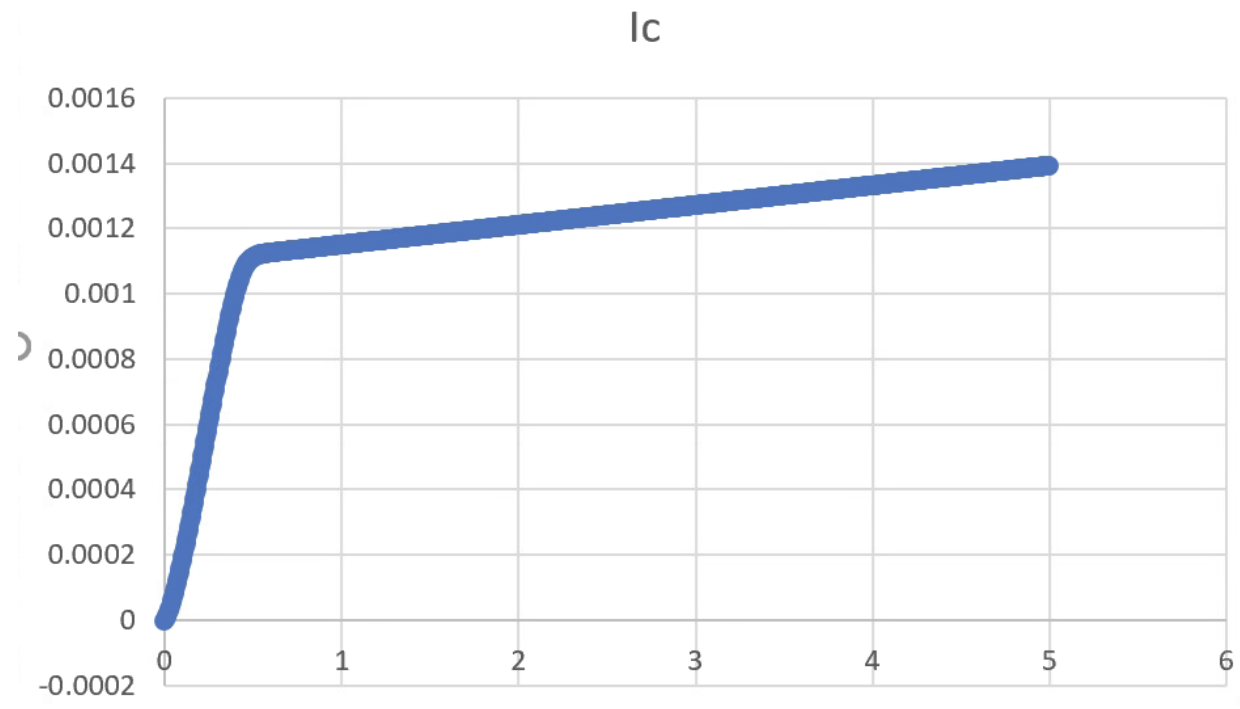


Schematic 6a

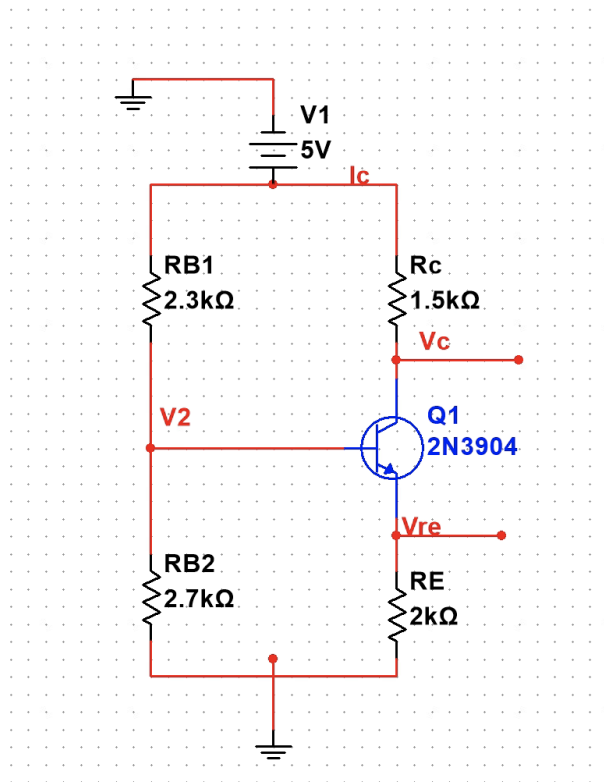


DC operating point or interactive simulation for 6a

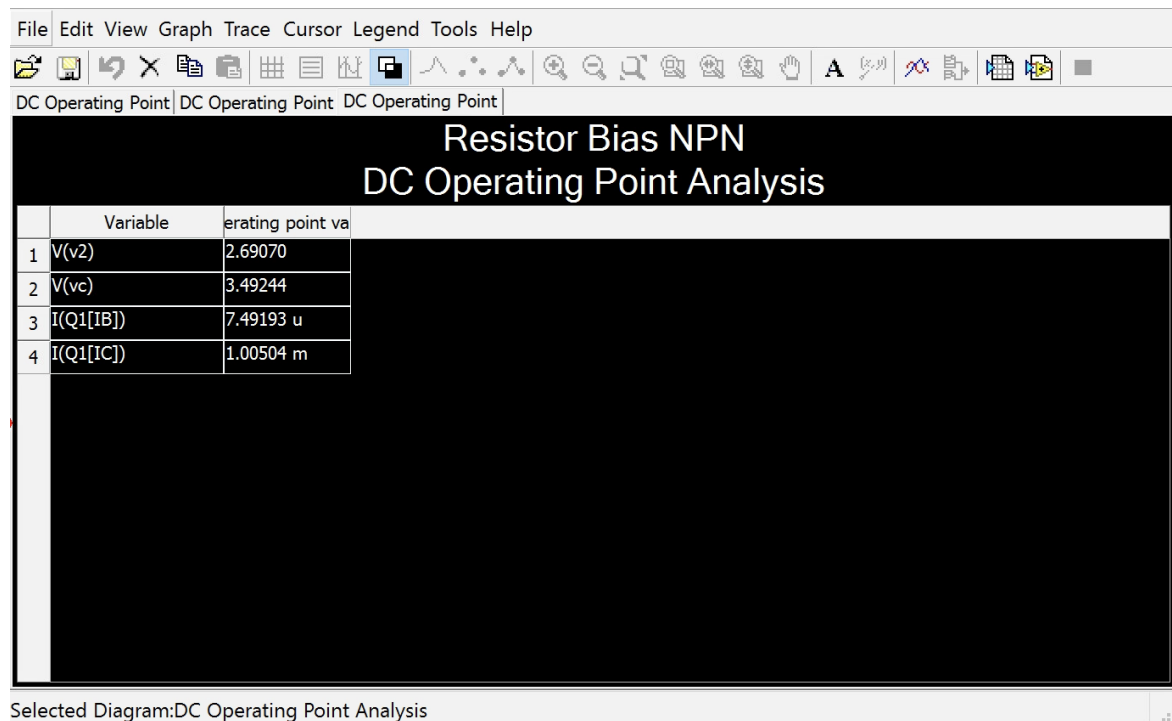


Schematic 6b

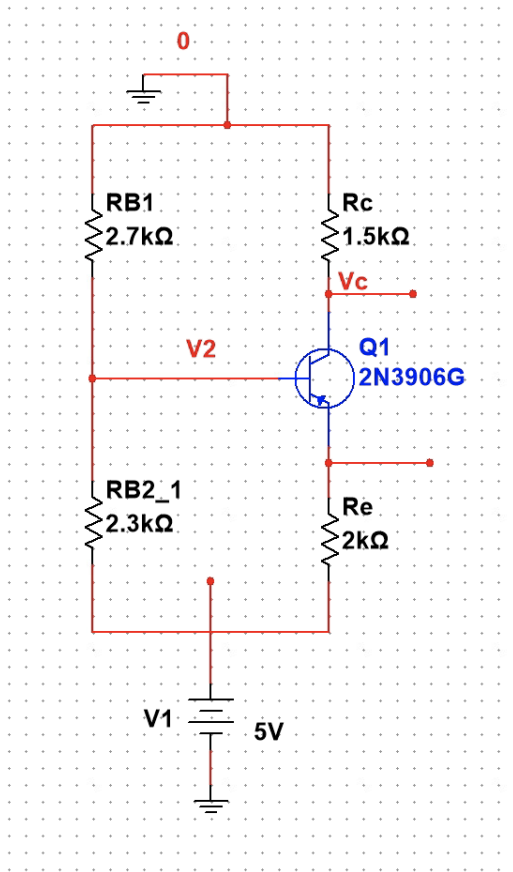


DC operating point or interactive simulation for 6b

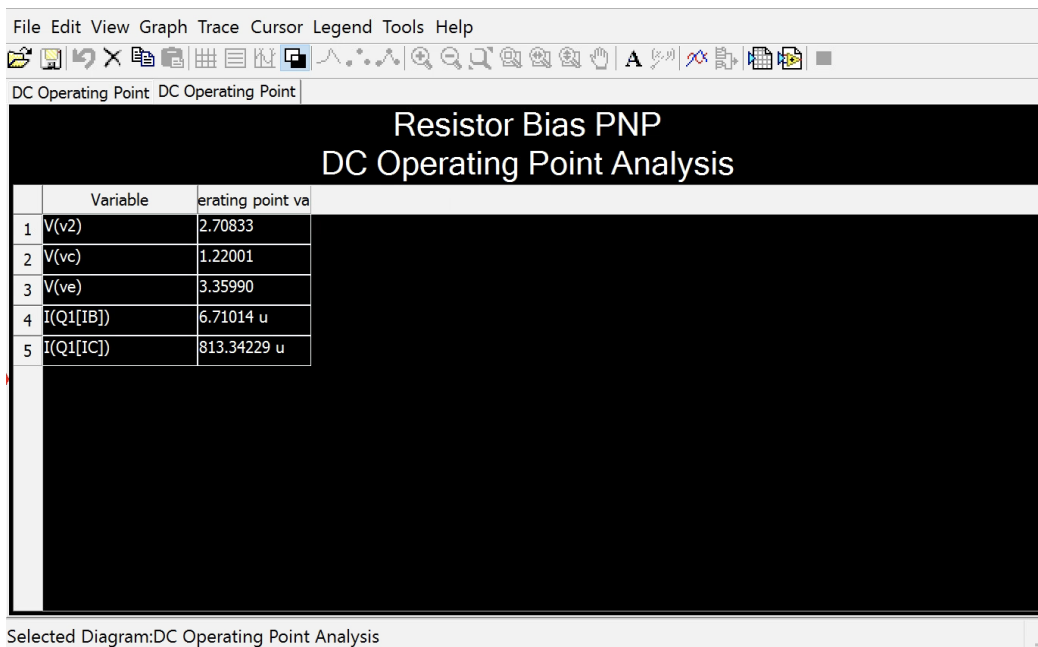


Schematic 7a

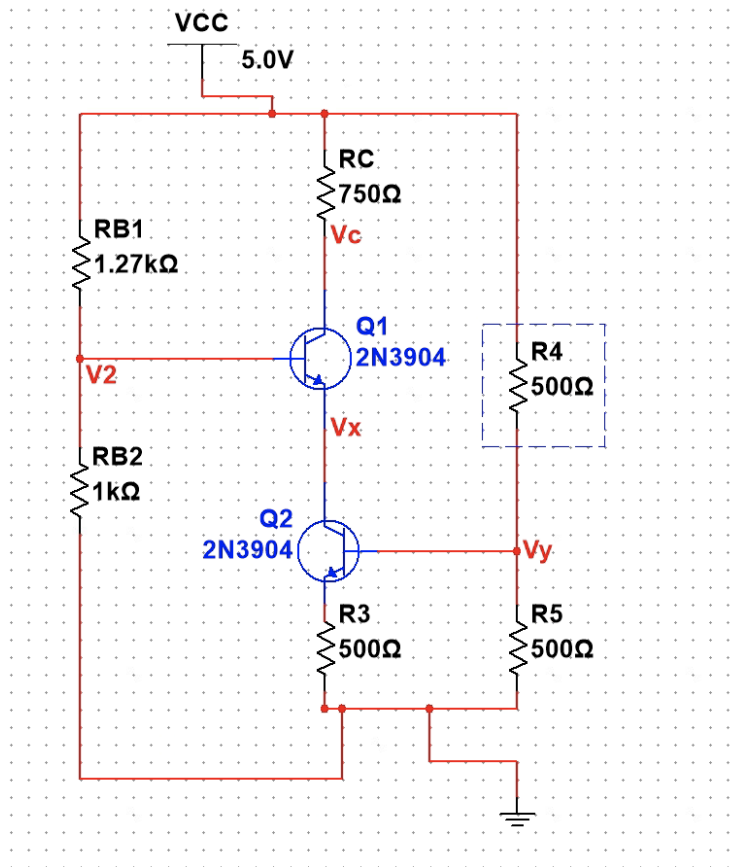


DC operating point or interactive simulation for 7a

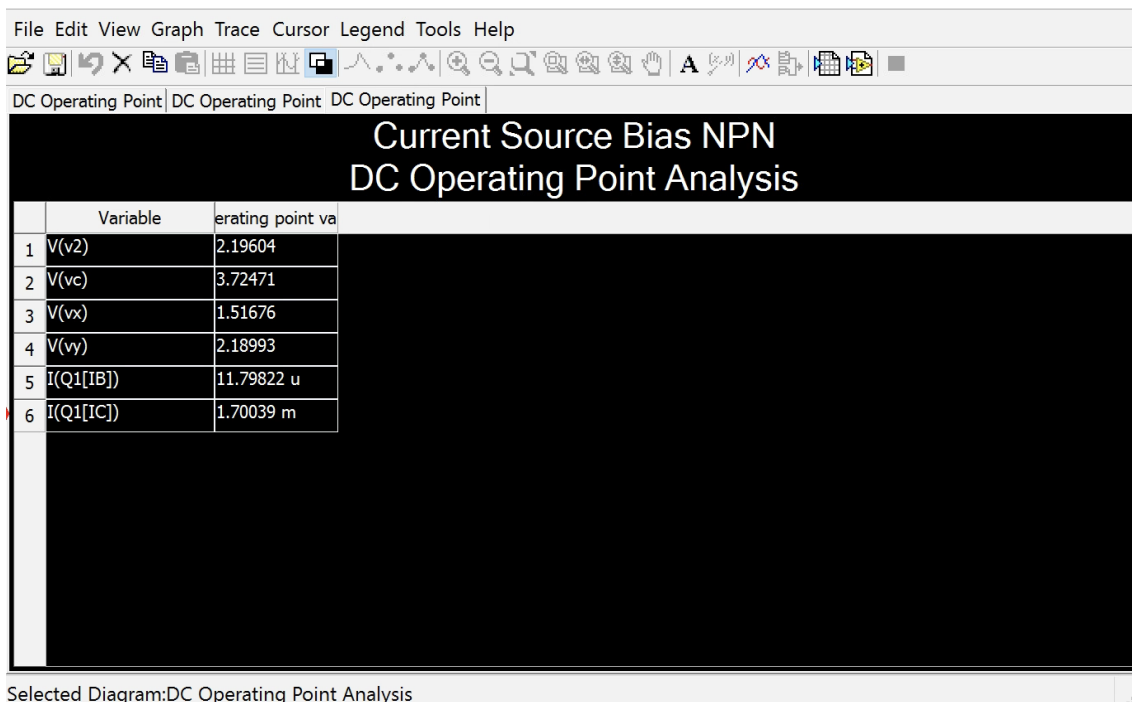

Schematic 8a

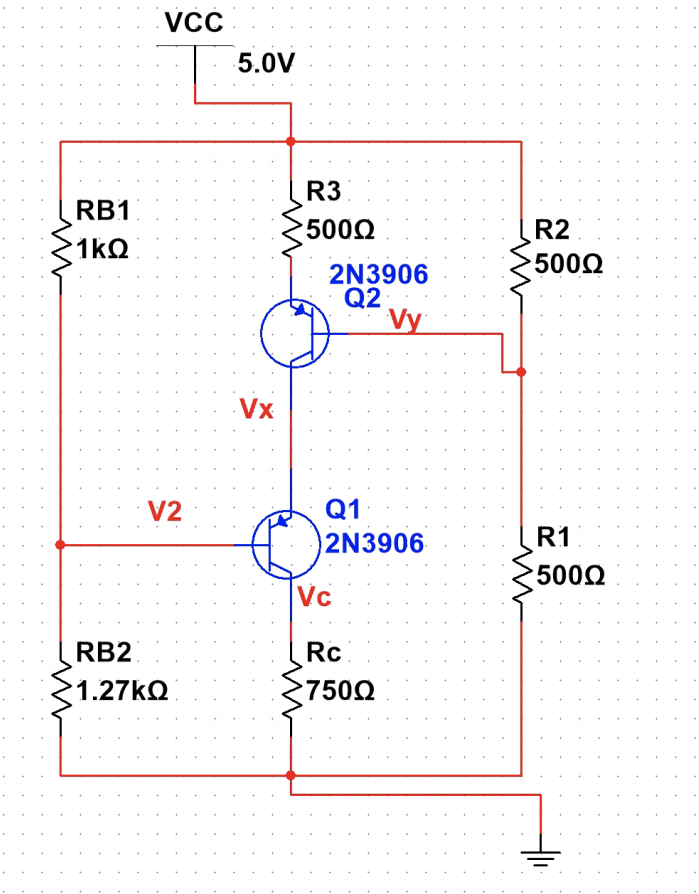


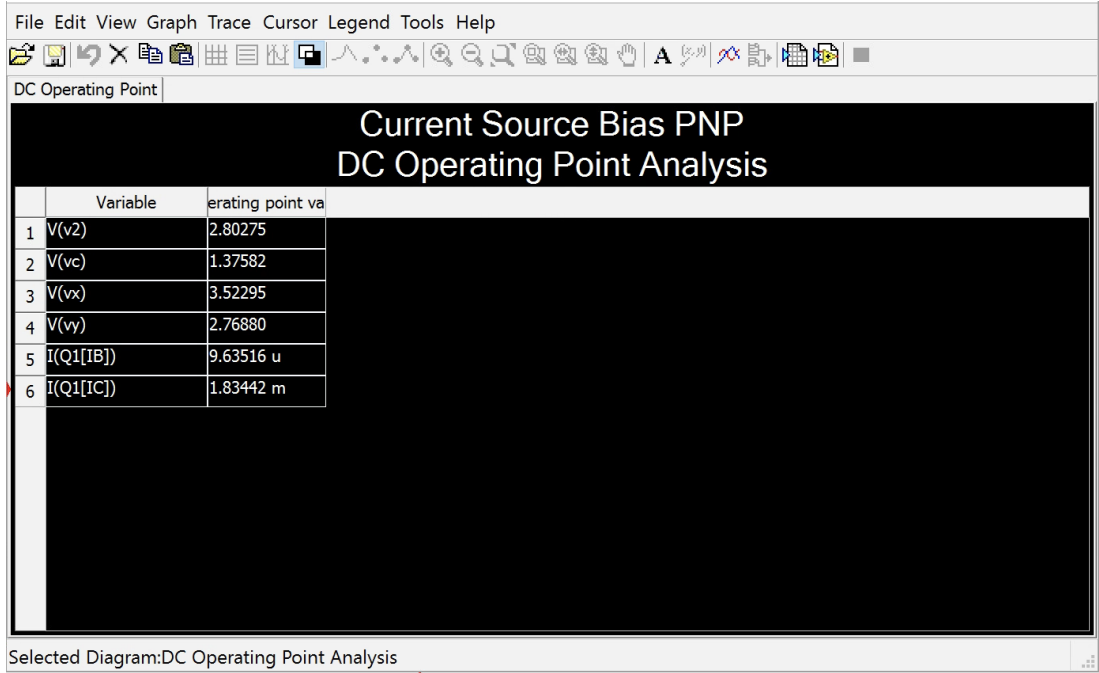DC operating point or interactive simulation for 8a




Measurements


NPN: I_c vs V_{BE}

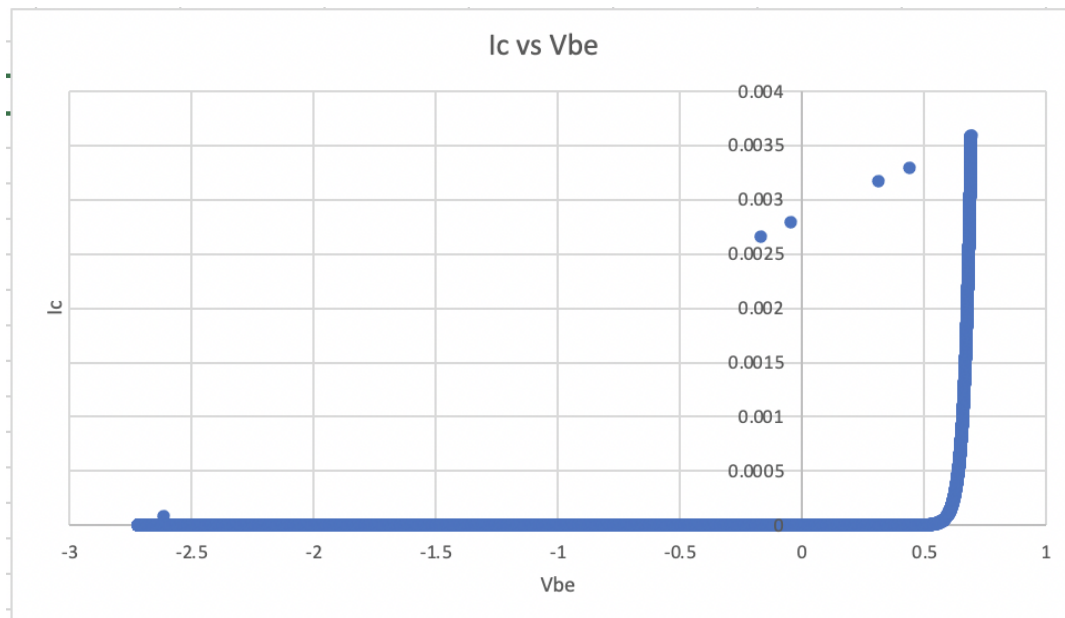

NPN: I_c vs V_{CE}

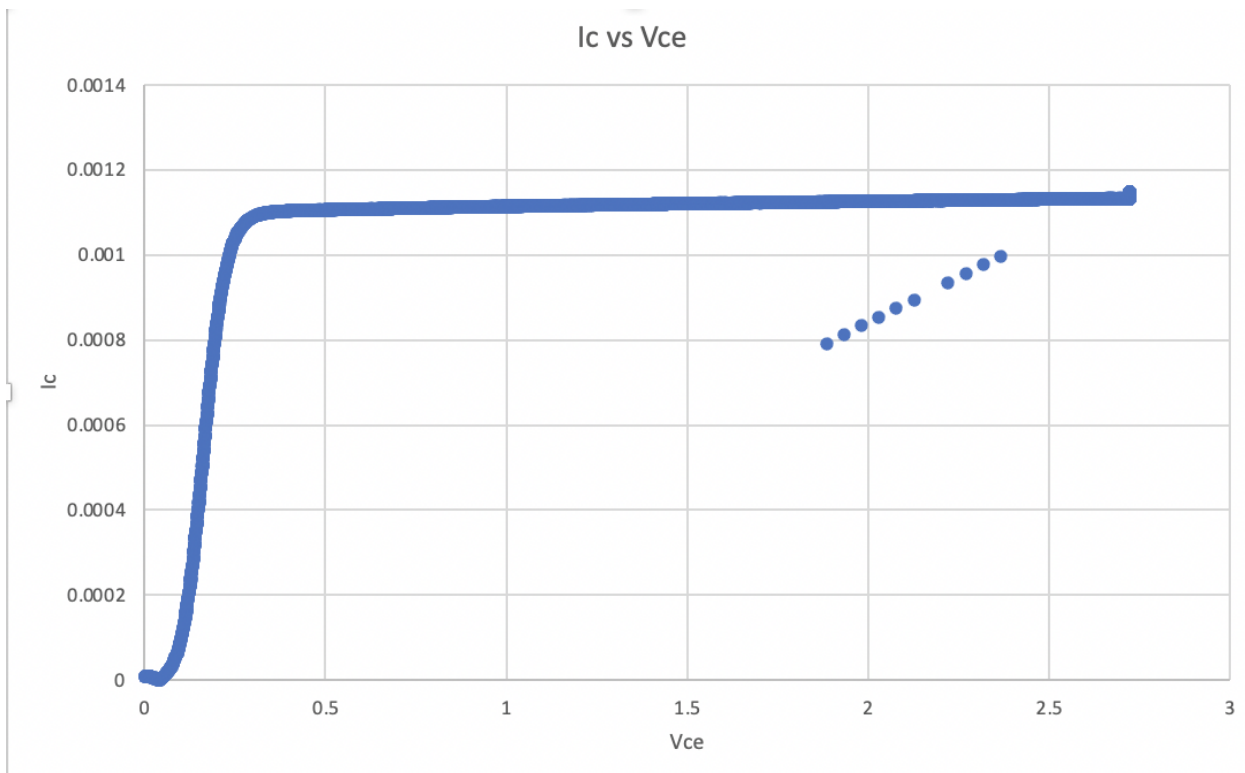

PNP: I_c vs V_{EB}

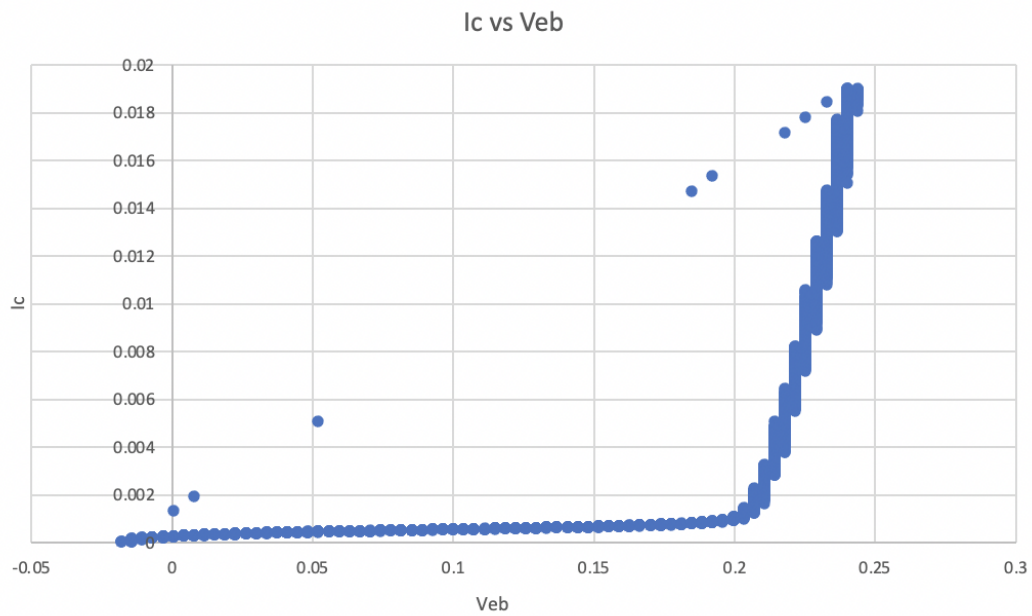

PNP: I_c vs V_{EC}

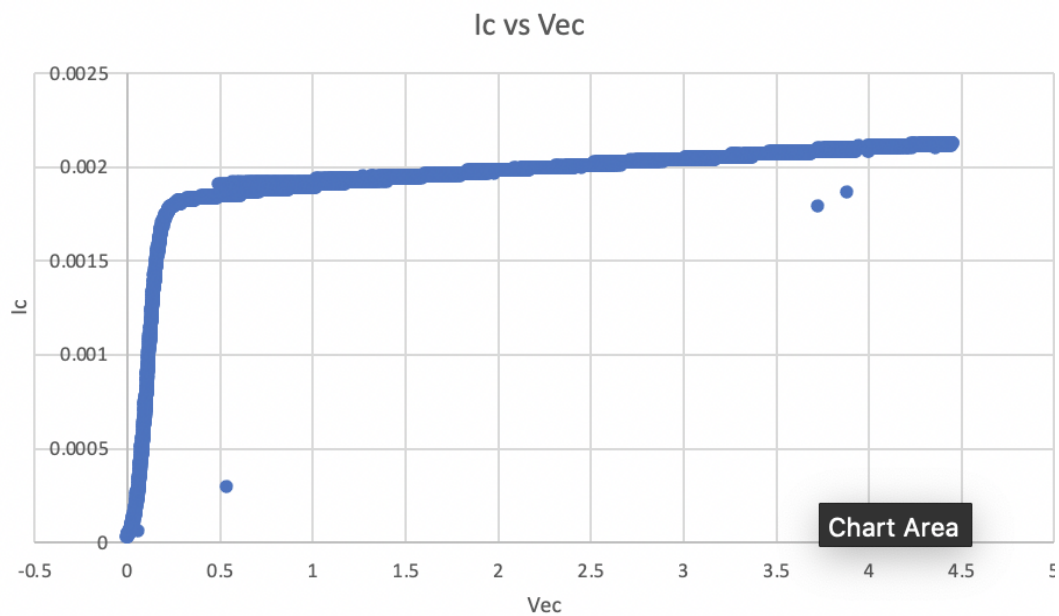


Figure 6 in Data Tables

Figure 7 in Data Tables

Figure 8 in Data Tables

Data Tables

Figure 6a

	I_C	V_B	V_C	V_E	V_2
Simulations	1.00504 mA	1.95601	3.49244	1.80342	2.69070
Measurements	1.17 mA	1.76	3.321	1.611	2.114

Figure 6b

	I_C	V_B	V_C	V_E	V_2
Simulations	813.34229 μ A	1.43678	1.22001	3.35990	2.70833
Measurements	8.966 μ A	1.345	1.258	3.41	2.711

Figure 7

	I_C	V_C	V_2	V_X	V_Y
Simulations	1.70039 mA	3.72471	2.19604	1.51676	2.18993
Measurements	1.836 mA	3.541	2.314	1.211	2.241

Figure 8

	I_C	V_C	V_2	V_X	V_Y
Simulations	1.83442 mA	1.37582	2.80275	3.52295	2.7688
Measurements	1.932 mA	1.455	2.731	3.431	2.873

Discussion

For lab 7, students learned about DC biasing and characterization of NPN and PNP BJTs. Most of the values between the simulations and measurements were pretty consistent for the circuits. If there were any minor differences, that's probably because of component differences, old breadboards, or loose wires.