

Pre-Lab 3: Operational Amplifiers Part 1

ECEN 325 - 511

TA: Zhiyong Zhang

Due Date: September 28, 2021

Calculations


1. Read the datasheet for the UA741 opamp and write down the typical values of the following parameters:

Supply Voltage	5V to 15 V -5V to -15 V
Input Offset Voltage	1mV
Voltage Gain	106dB
Power Consumption	50mW
Output Resistance	75Ω
Bandwidth	1MHz
Input Resistance	2MΩ
Input Offset Current	20nA
Slew Rate	0.5V/μs

2. Derive voltage gains

Circuit A:

Circuit A :

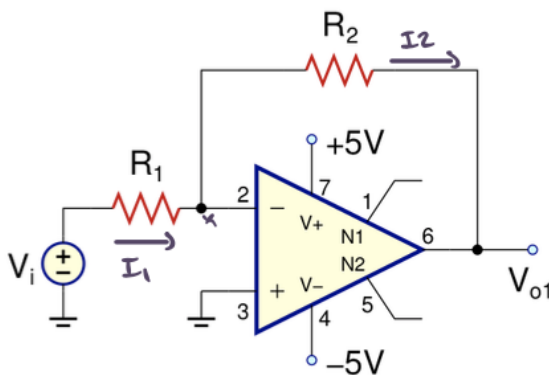


$$V_x = 0 \quad \text{and} \quad I_1 = I_2$$
$$\frac{V_i - V_x}{R_1} = \frac{V_x - V_{o1}}{R_2}$$

$$\boxed{\frac{V_{o1}}{V_i} = -\frac{R_2}{R_1}}$$

Circuit B:

Circuit B:

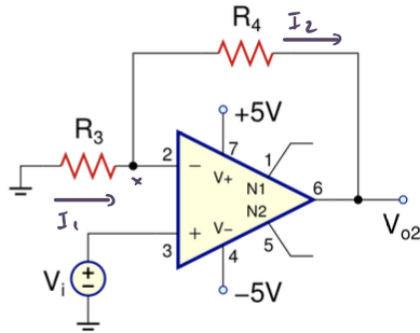

$$V_x = V_i$$

$$\text{node: } \frac{V_i}{R_3} + \frac{V_i + V_{02}}{R_4} = 0$$


$$V_i \left(\frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{V_{02}}{R_4} = 0 \Rightarrow V_i \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = -\frac{V_{02}}{R_4}$$

$$= \frac{V_{02}}{V_i} = \frac{R_4}{R_3 + R_4}$$

$$\frac{V_{02}}{V_i} = 1 + \frac{R_4}{R_3}$$

Circuit C:

Circuit C:

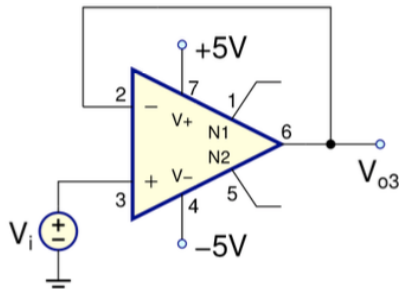

$$V_x = V_i$$

$$V_{03} = V_i$$

$$\frac{V_{03}}{V_i} = 1$$

3. If $R_1 = R_3 = 10\text{k}\Omega$, find R_2 and R_4 such that $V_{01}/V_i = -3$ and $V_{02}/V_i = 6$.


$$3) \quad \frac{V_{01}}{V_i} = \frac{-R_2}{R_1} = -3 = \frac{-R_2}{10\text{k}} \Rightarrow R_2 = 30\text{k}\Omega$$

$$\frac{V_{02}}{V_i} = 1 + \frac{R_4}{R_3} = 6 = 1 + \frac{R_4}{10\text{k}} \Rightarrow R_4 = 50\text{k}\Omega$$


Simulations (on Multisim)

Circuit A


1. Schematic

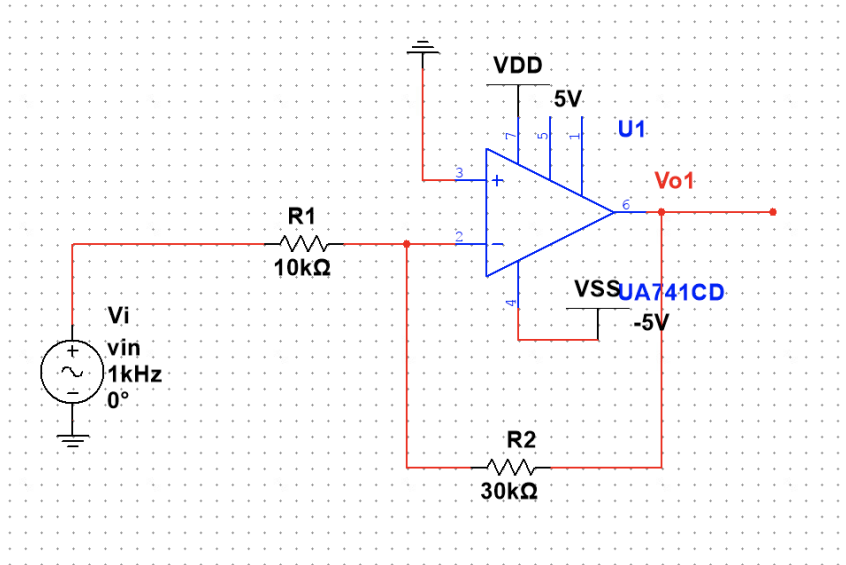


2. AC Sweep

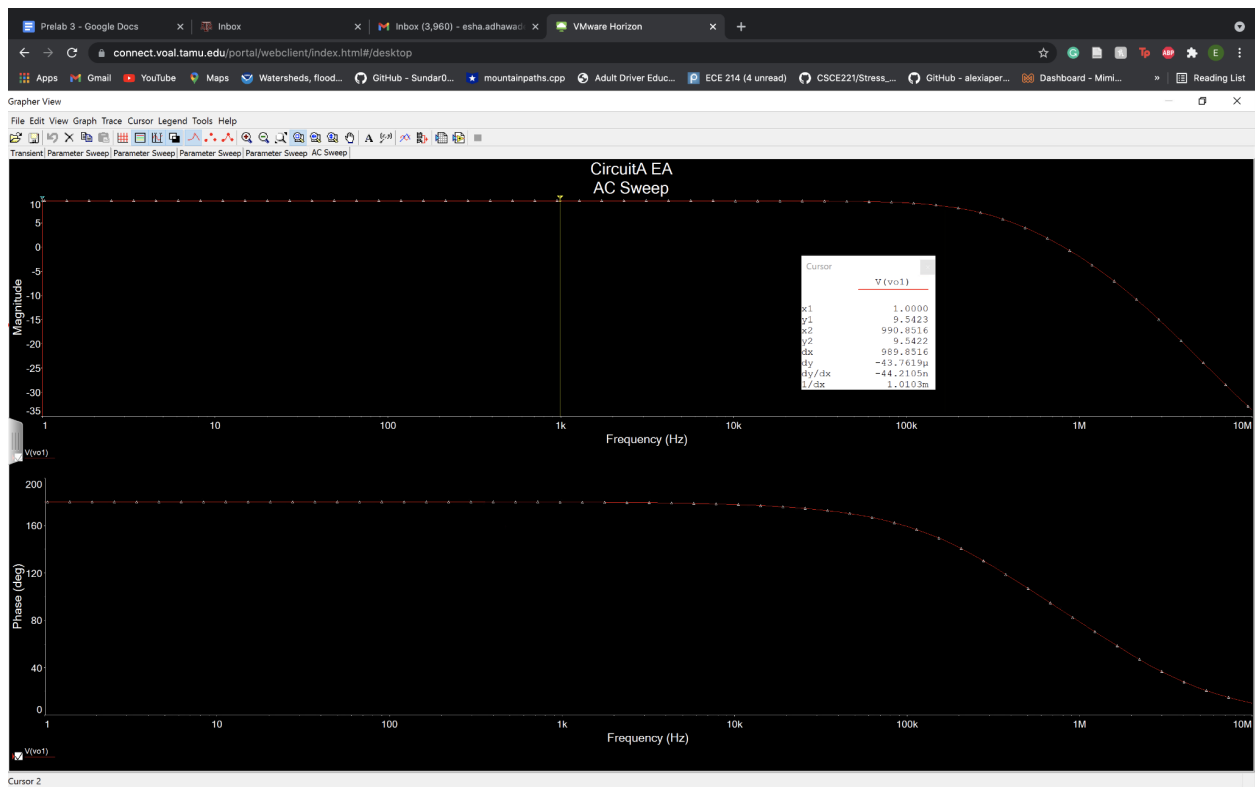


3. Transient

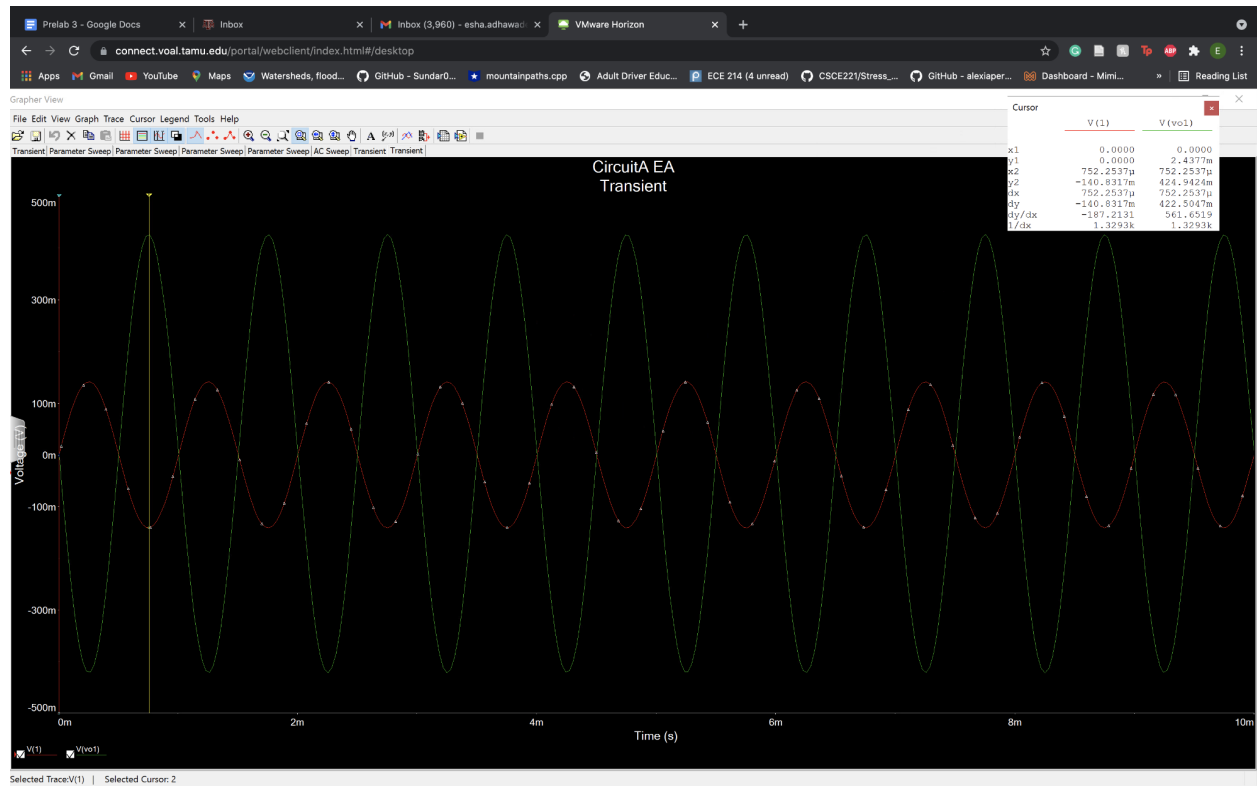

4. Circuit Parameter Sweep

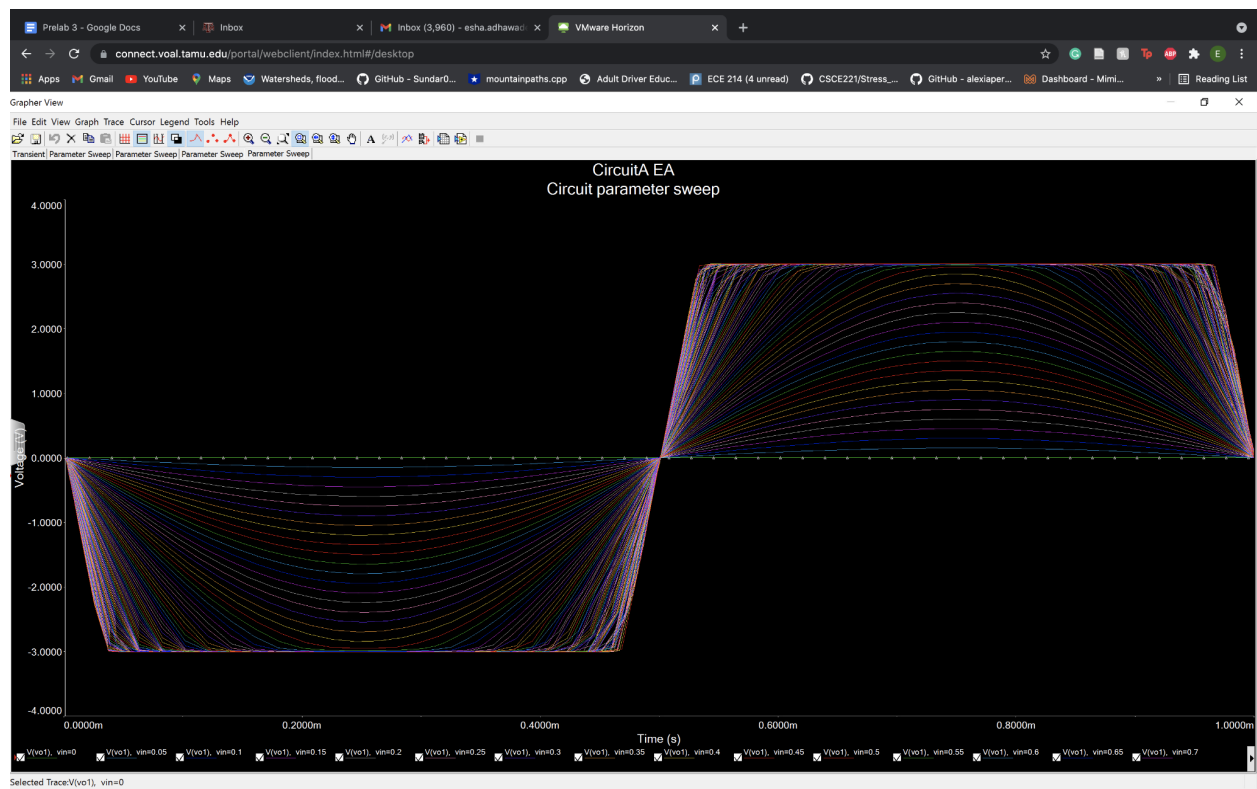


5. Fourier Simulation

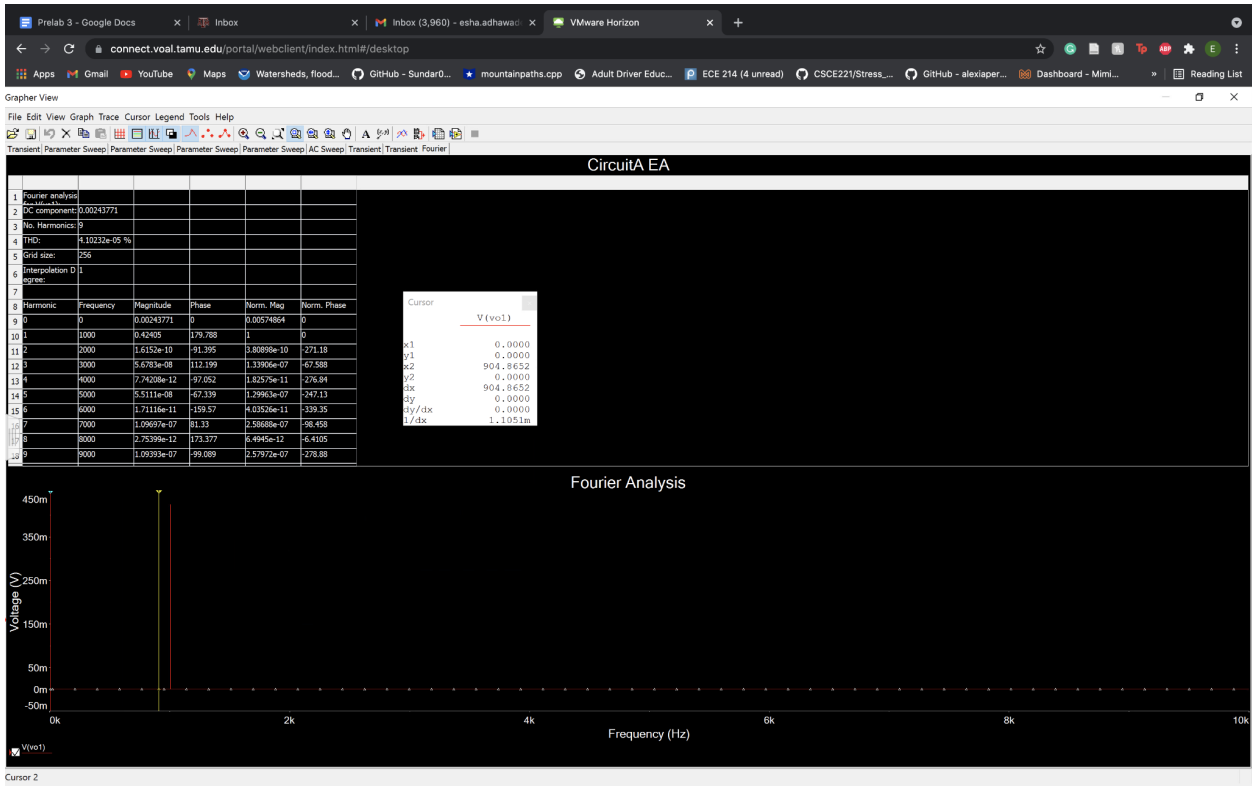


Circuit B


1. Schematic

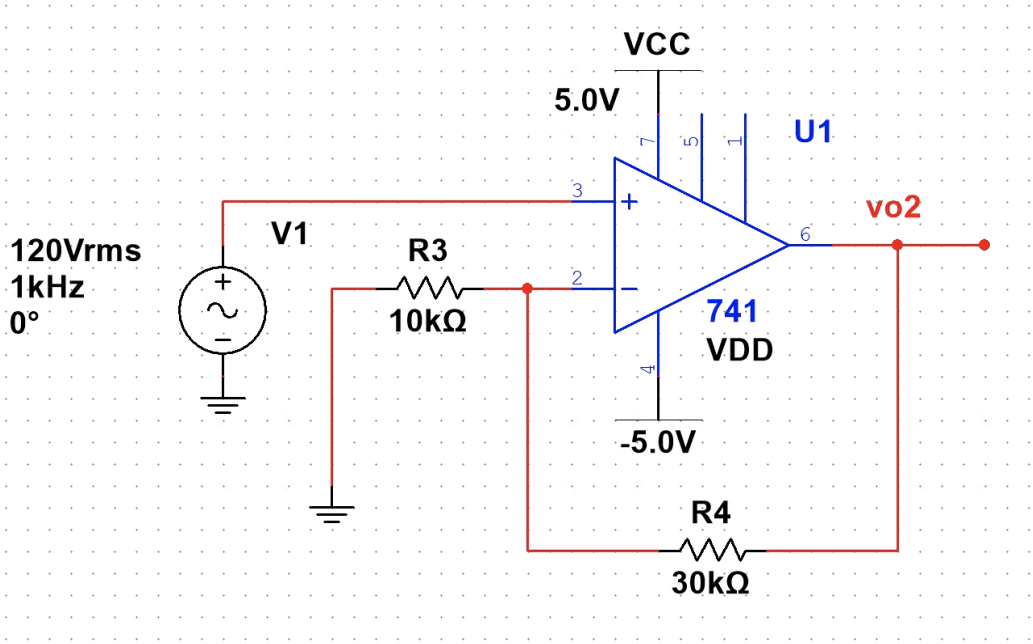


2. AC Sweep

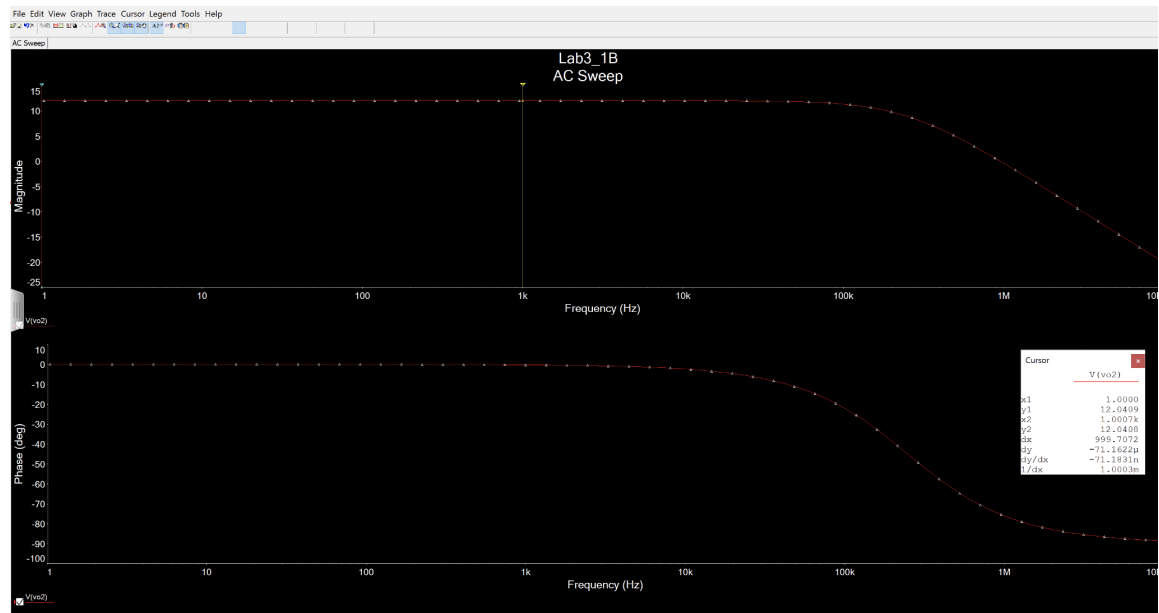


3. Transient

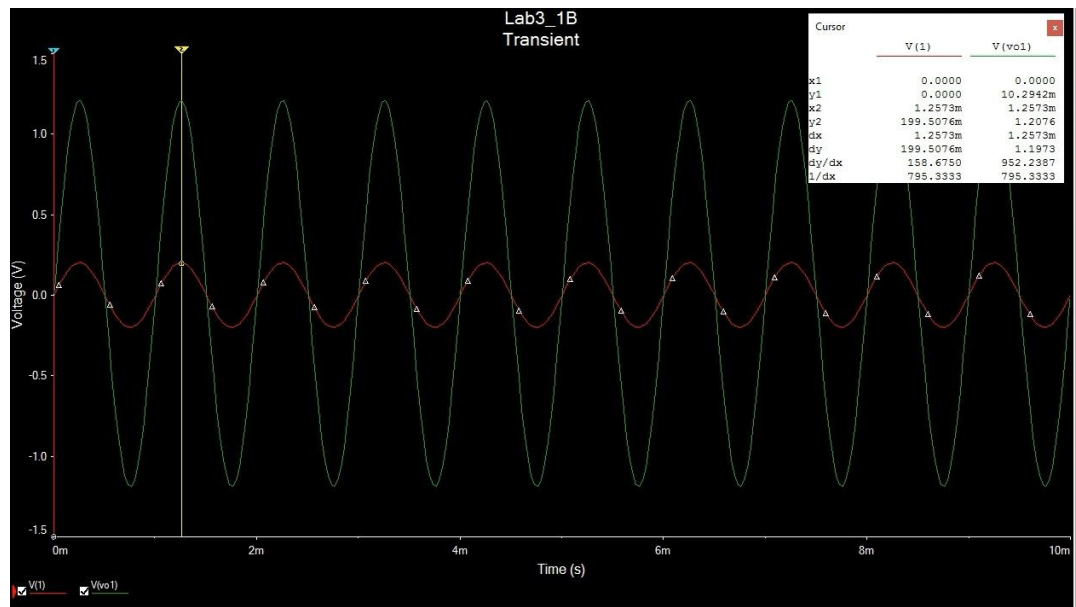

4. Circuit Parameter Sweep

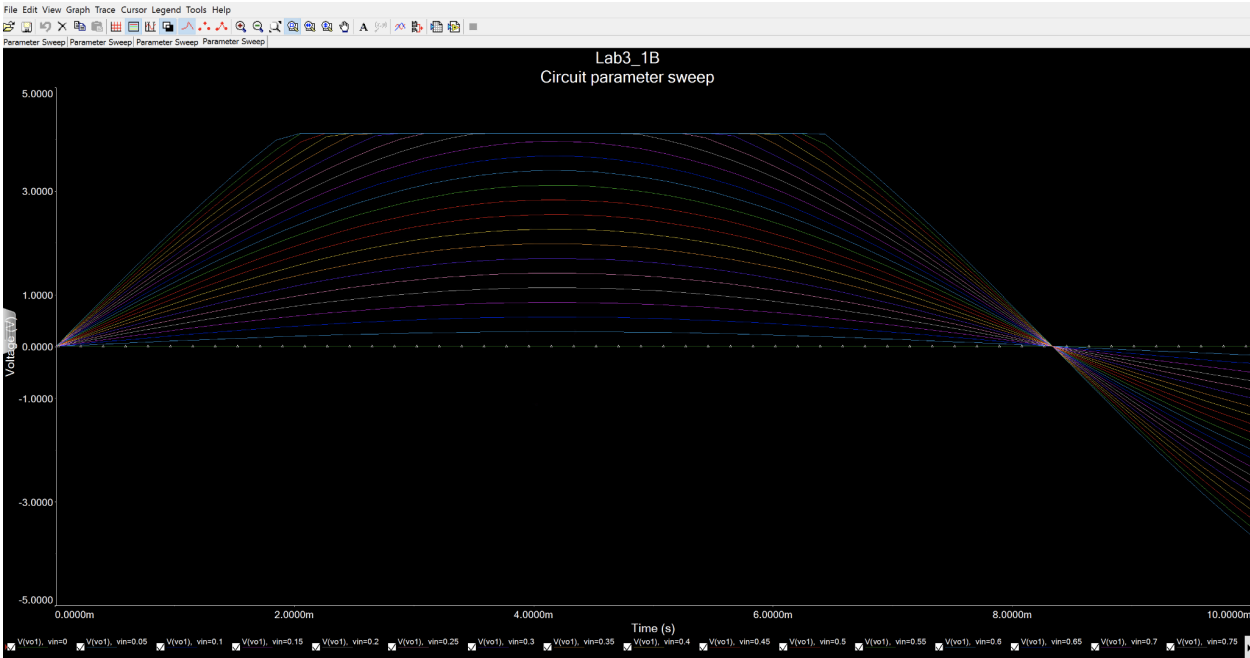


5. Fourier Simulation

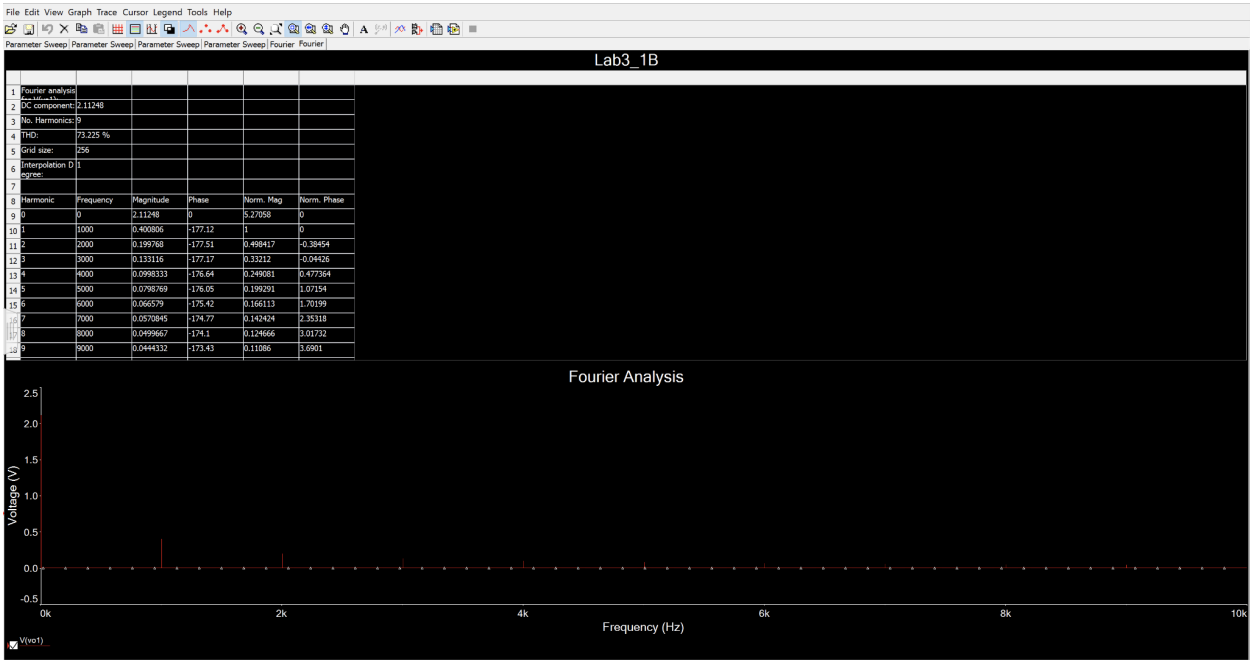


Circuit C


1. Schematic

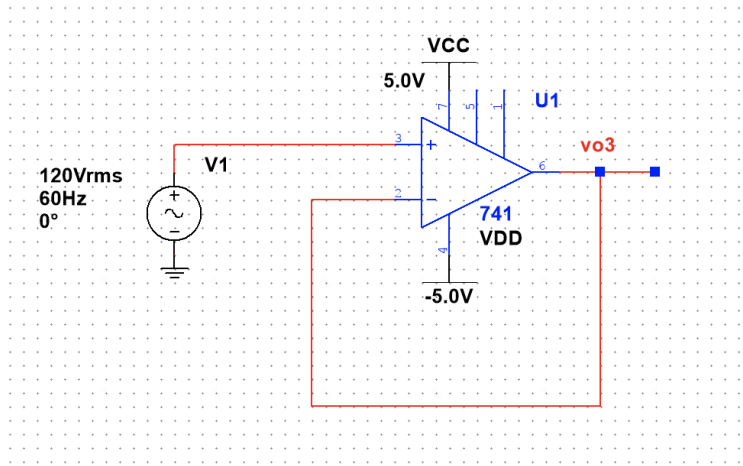


2. AC Sweep

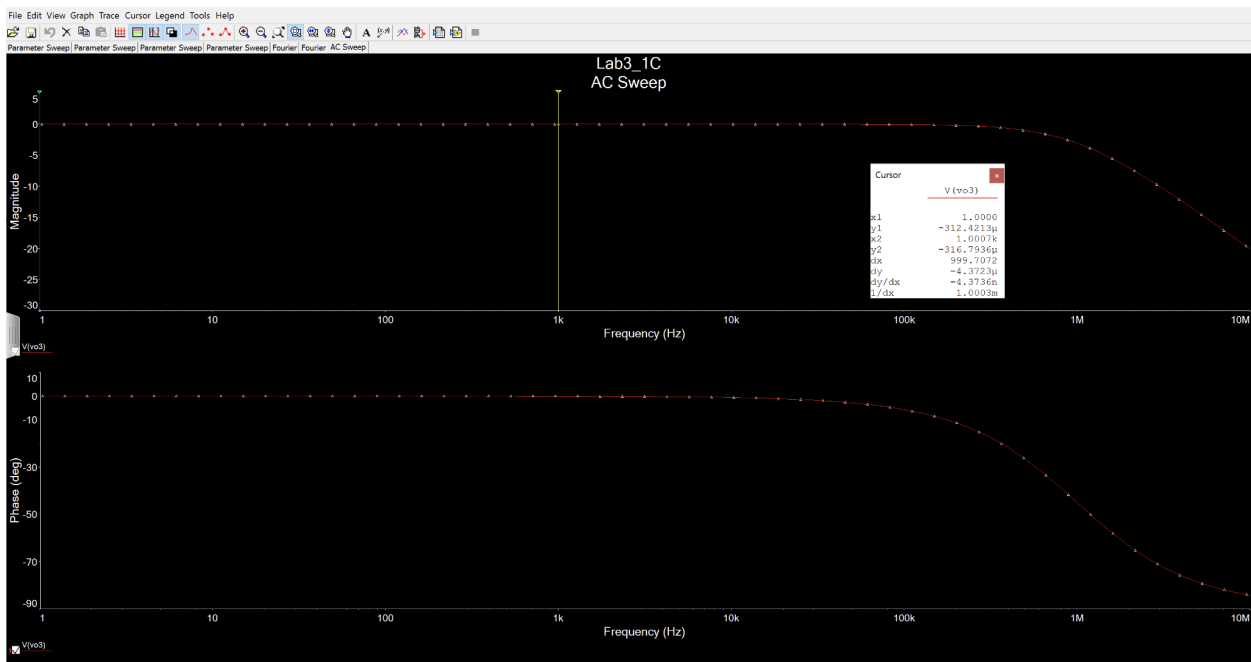

3. Transient

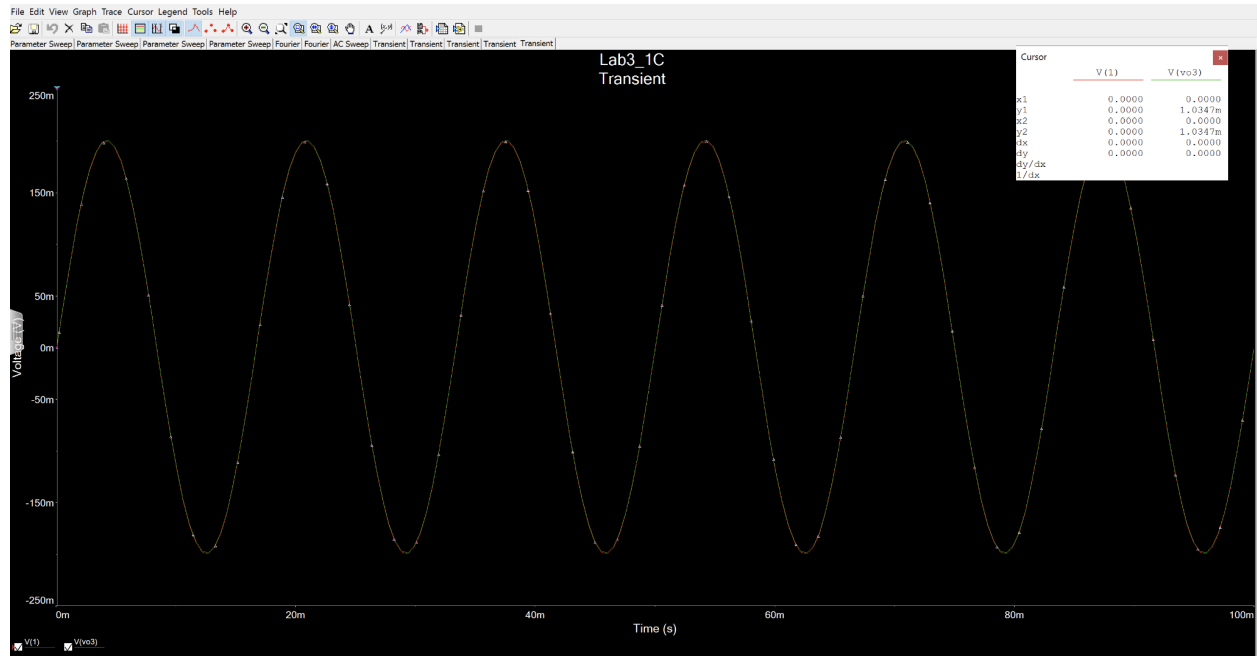

4. Circuit Parameter Sweep

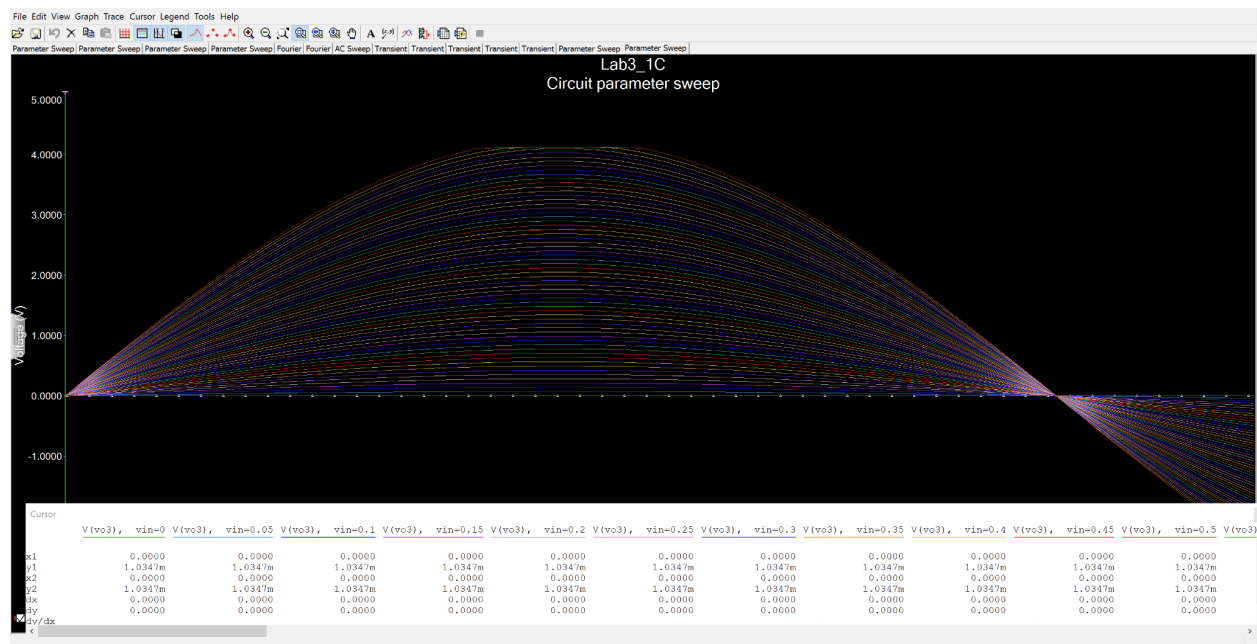

5. Fourier Simulation

