

# Lab 5: Operational Amplifiers Part 3

ECEN 325 - 511

TA: Zhiyong Zhang

Date Performed: October 12, 2021


Due Date: October 19, 2021

## Purpose

The purpose of this lab was to learn about some more op-amp configurations and understand the non-idealities of op-amps. For this lab, students built Lossy Integrator, Pseudo Differentiator, Finite GBW Limitations, Slew Rate Limitations.

## Calculations

### Lossy Integrator

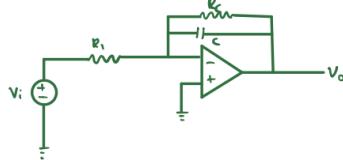

we have  $R_1 = 22\text{ k}\Omega$ ,  $C = 220\text{ nF}$ ,  $\frac{V_o(s)}{V_i(s)} = 22$

$$V_o(s) = V_c(s) + C \cdot V_c(s) - V_c(0) e^{-sT}$$

$\Rightarrow$  constant time

$V_c(t) = \text{voltage across capacitor}$

To get thevenin voltage across  $C$  we have

Voltage across  $R_2$  will be  $V_{TH}$  and  $R_{TH} = R_1 || R_2$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_i \quad \text{--- (1)}$$

$$V_c(0) = 0 \quad V_o(t) = V_{TH} e^{-t/T}$$

we have  $T = R_{TH} C = \frac{R_1 R_2 C}{R_1 + R_2} \quad \text{--- (2)}$

$$1) \quad V_o(t) = \frac{R_2}{R_1 + R_2} e^{-t \left( \frac{R_1 + R_2}{R_1 R_2 C} \right)}$$

$$2) \text{ Voltage Gain} \quad \frac{V_o(s)}{V_i(s)} = \frac{-R_2 || Z_L}{R_1}$$

$$= \frac{R_2 Z_L}{R_2 + Z_L} \frac{1}{R_1}$$

$$= \frac{-R_2}{R_1} \left( \frac{1/C_s}{R_2 + 1/C_s} \right) = \frac{-R_2}{R_1} \left( \frac{1}{R_2 (s+1)} \right)$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{-R_2}{R_1}}$$

Finite gain

now  $-22 = -R_2/R_1$

$12_2 = 22\text{ k}\Omega$

$R_1 = 1\text{ k}\Omega$

the 3dB frequency  $= \frac{1}{T} = \frac{R_1 + R_2}{R_1 R_2 C}$

$$= \frac{1\text{ k}\Omega + 22\text{ k}\Omega}{22\text{ k}\Omega * 1\text{ k}\Omega * 220\text{ nF}}$$

$$= 4.75\text{ kHz}$$

$$3) \frac{V_o(s)}{V_i(s)} = \frac{-R_2}{R_1} \left( \frac{1}{206.61s + 1} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-22k\Omega}{1k\Omega} \left( \frac{1}{22k\Omega s + 22.061} \right)$$


$$= \frac{-22}{4.84 \times 10^{-3}s + 1} = \frac{-22}{\frac{s}{206.61} + 1} = \frac{-22}{1 + \frac{s}{206.61}}$$

compare  $\omega = \frac{-s}{1 + \frac{s}{206.61}} \quad f = 206.61 \quad \omega = 22$

only one pole at 206.61


$$\text{so } |T_o(s)| = +20 \log(22)$$

$$\lim |T_o(s)| = +20 \log(22) = 26.85$$

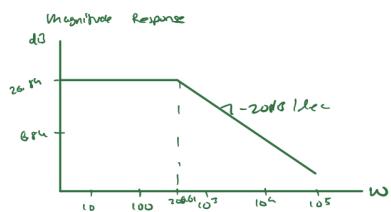

$$\text{phase } [T(s)] = -\tan^{-1} \left( \frac{s}{206.61} \right)$$
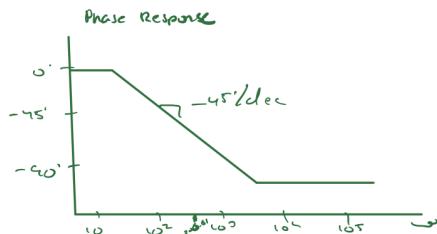
$$\lim_{s \rightarrow 0} \text{phase } [T(s)] = -\tan^{-1} \left( \frac{0}{206.61} \right) = 0^\circ$$



$$4) \frac{V_o(s)}{V_i(s)} = \frac{22}{1 + \frac{s}{206.61}} = \frac{22}{\sqrt{1 + \frac{s^2}{206.61^2}}} < -\tan^{-1} \left( \frac{\omega}{206.61} \right)$$

at  $\omega = 2\pi + 1000\text{rad/s}$


$$= \frac{22}{\sqrt{1 + \frac{(2000\pi)^2}{(206.61)^2}}} < -\tan^{-1} \left( \frac{2000\pi}{206.61} \right) = -0.723 < -88.11$$

$$V_o = -0.723 < -88.11 \times 0.5 < 0^\circ$$


$$V_o = -3615 < -88.11$$

$$V_o(t) = -0.3615 \sin(2\pi 1000t - 88.11)$$

5) Given square wave

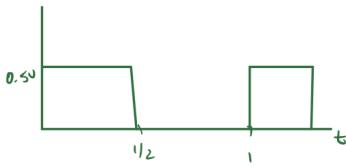

From Thevenin circuit

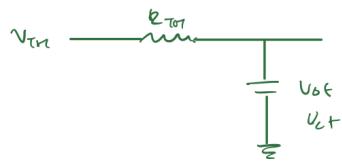


$$V_{TH} = \frac{R_L}{R_1 + R_L} V_i = \frac{22}{1+22} V_i = 0.95 V_i$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 0.95 \text{ k}\Omega$$


$$T = R_{TH} C = 0.95 \times 220 \text{ nF} = 210.43 \text{ }\mu\text{s}$$

$$\text{Since } V_i = 0.5 \text{ V} \quad V_{TH} = 0.9 \times 0.5 \text{ V} \\ = 0.475 \text{ V} \approx 475 \text{ mV}$$
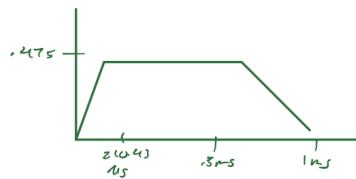
$$V_o(t) = (V_{TH} - V_{TH} e^{-t/T}) = 475 - 475 e^{-t/210.43 \text{ }\mu\text{s}}$$



Pseudo Differentiator

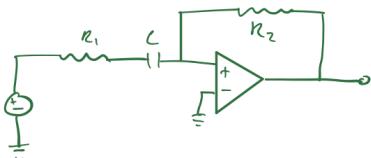

we have  
gain  $\approx -22$   
 $R_1 = 1 \text{ k}\Omega$   
 $C = 33 \text{ nF}$

$$V_i \xrightarrow{R_1, C} V_o \xrightarrow{R_2} V_o$$

$$\text{As } t \rightarrow \infty \quad V_o = 0 \quad T(R_1 + R_2)C$$

$$V_o(t) = V_o(0) \left( \frac{R_2}{R_1 + R_2} \right) \text{ for } t = 0 \text{ to } T$$

$$V_o(t) = V_o(0) \times \frac{R_2}{R_1 + R_2} \text{ for } t = 0 \text{ to } T$$

$$V_o(t) = V_o(0) \times \frac{R_2}{R_1 + R_2} e^{-t/(R_1 + R_2)C}$$

$$V_o(t) = V_o(0) \frac{R_2}{R_1 + R_2} e^{-t/(R_1 + R_2)C}$$

for high freq  $\omega \rightarrow \infty$   $i_c = \frac{1}{sC} = 0$  and C acts as a short circuit

$$\frac{V_2}{V_1} = A_v = -\frac{R_2}{R_1} = -22, \quad R_2 = 22 \times 1k = 22k\Omega$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \frac{R_2}{R_2 + (R_1 + 1/C)s} = \frac{\frac{R_2}{C}s}{1 + (R_2 + R_1)s}$$

$$= \frac{7.26 \times 10^{-4} s}{1 + 7.54 \times 10^{-4} s} = \frac{7.26 \times 10^{-4}}{1 + \frac{s}{7.54}}$$

here the transfer function has zero at 1317.3 and pole at 0

3dB freq at 1317.3 rad/sec



$$\frac{1}{T} = (R_1 + R_2)C$$

$$= (23k)(33nF) = 7.59 \times 10^{-4} \text{ Hz}$$

$$\text{for magnitude: } \lim_{\omega \rightarrow 0} \left| \frac{V_o(s)}{V_i(s)} \right| = -20 \log (7.26 \times 10^{-4})$$

$$= -62.78 \text{ dB}$$
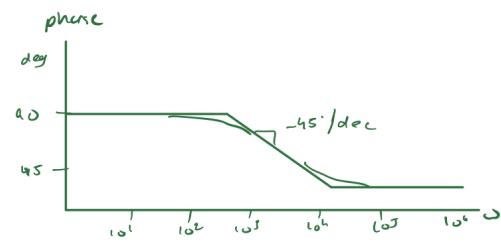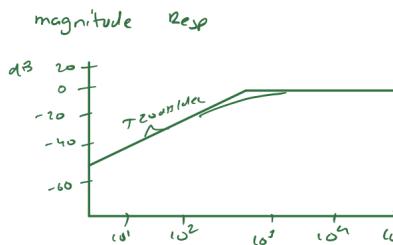
$$\text{for phase: } \lim_{\omega \rightarrow 0} \angle \frac{V_o(s)}{V_i(s)} = \tan^{-1}(0) - \tan^{-1}\left(\frac{0}{1317.3}\right) = 90^\circ$$



4)  $V_i = 0.1 \sin(2\pi 1000t)$   
 $V_i = 0.1 \angle 0^\circ$   $\rightarrow$  transfer func.  $1317.5 \text{ Hz}$

$$\frac{V_o(1317.5)}{V_i(1317.5)} = \frac{7.26 \times 10^{-4} \times 2000\pi j}{(1 + 7.26 \times 10^{-4} \times 2000\pi j)}$$



$$= 0.936$$

$$\angle \frac{V_o}{V_i} = \tan^{-1} \left( \frac{7.26 \times 10^{-4} \times 2000\pi}{1} \right) - \tan^{-1} \left( \frac{7.26 \times 10^{-4} \times 2000\pi}{1} \right)$$

$$= 11.84$$

$$V_o = 0.0936 \angle 11.84$$
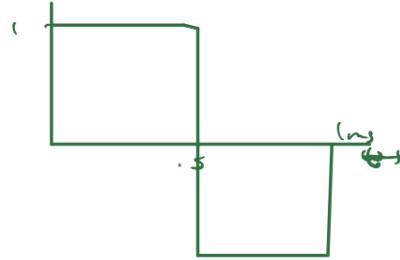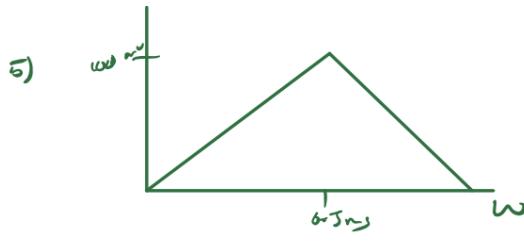
$$= \boxed{0.0936 \sin(2\pi 1000t + 11.84)}$$



## Finite GBW Limitations

D) gain = 23       $R_2 = 1k\Omega$   
 $\text{gain} = 1 + \frac{R_2}{R}$   
 so  $R_2 = 22k\Omega$

gain = 57       $57 = 1 + \frac{R_2}{1k\Omega}$   
 $R_2 = 56k\Omega$


gain for P3       $83 = 1 + \frac{R_2}{1k\Omega}$   
 $R_2 = 82k\Omega$

2)  $\frac{V_o}{V_i} = \frac{G_o}{1 + j\omega/\omega_0}$

for 23  $\rightarrow \frac{V_o}{V_i} = \frac{23}{1 + j\frac{\omega}{\omega_0}}$

for 57  $\rightarrow \frac{V_o}{V_i} = \frac{57}{1 + j\frac{\omega}{\omega_0}}$

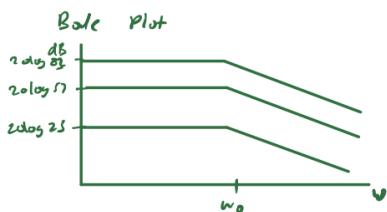
for P3  $\rightarrow \frac{V_o}{V_i} = \frac{83}{1 + j\frac{\omega}{\omega_0}}$  , phase resp. =  $-\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$



Slew rate limitation

from circuit  $\frac{V_o}{W} = 1$

Bode Plot

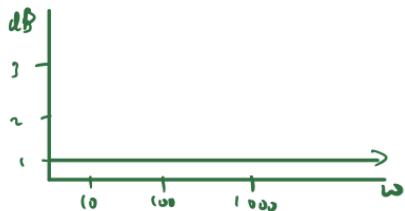

Here slew rate =  $0.5V/\mu s$

$$V_{in} = 1V$$

$$V_{in} = \sin \omega t = V_0$$

$$\frac{dV_o}{dt} = \omega \cos \omega t = 0.5V/\mu s \quad (j) \quad f = \frac{0.5}{2\pi} = \frac{0.5 \times 10^6}{2\pi} = 79.58 \text{ kHz}$$

slew rate =  $0.5V/\mu s$

$$V_{max} = ?$$

$$f = 75 \text{ kHz}$$

$$0.5V/\mu s = 2\pi \times 75 \text{ kHz}$$


$$V_m = \frac{0.5 \times 10^6}{2\pi \times 75 \text{ kHz}}$$

$$V_m = 1.0610$$


## Simulations (on Multisim)

### Lossy Integrator


#### Schematic

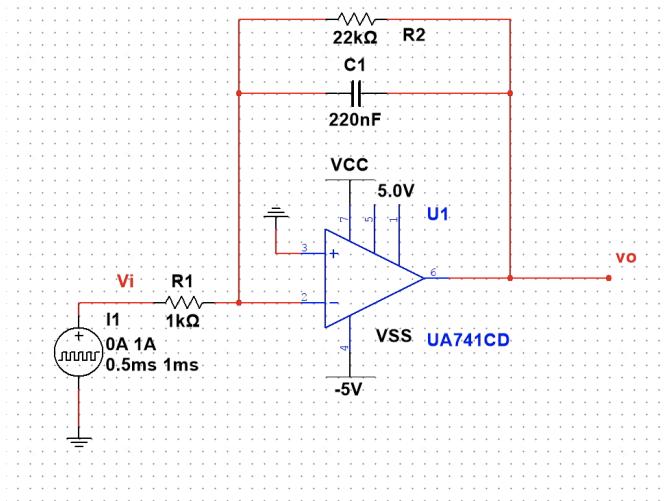


#### Bode

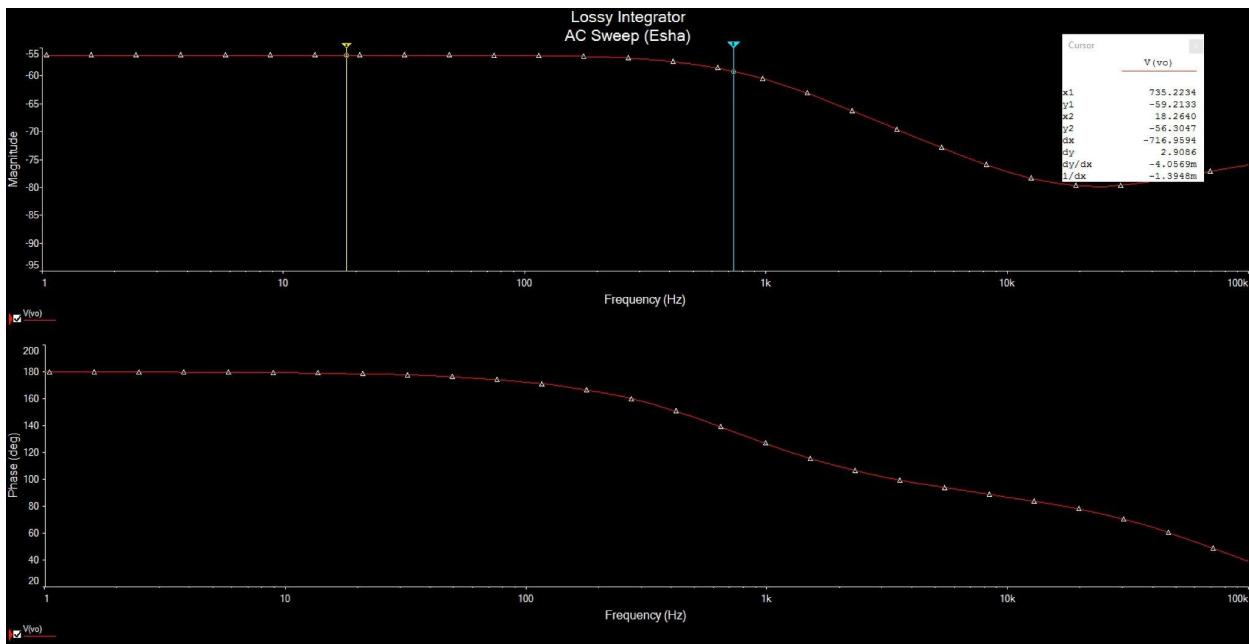

### Sin Transient

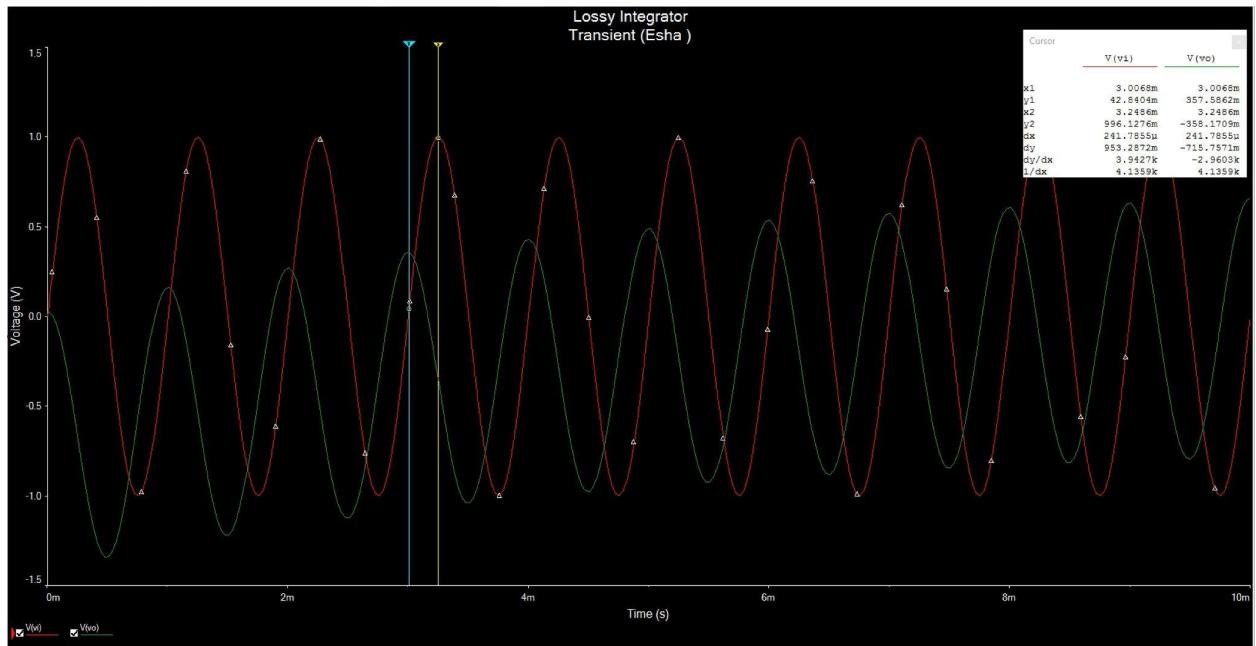


### Square Transient

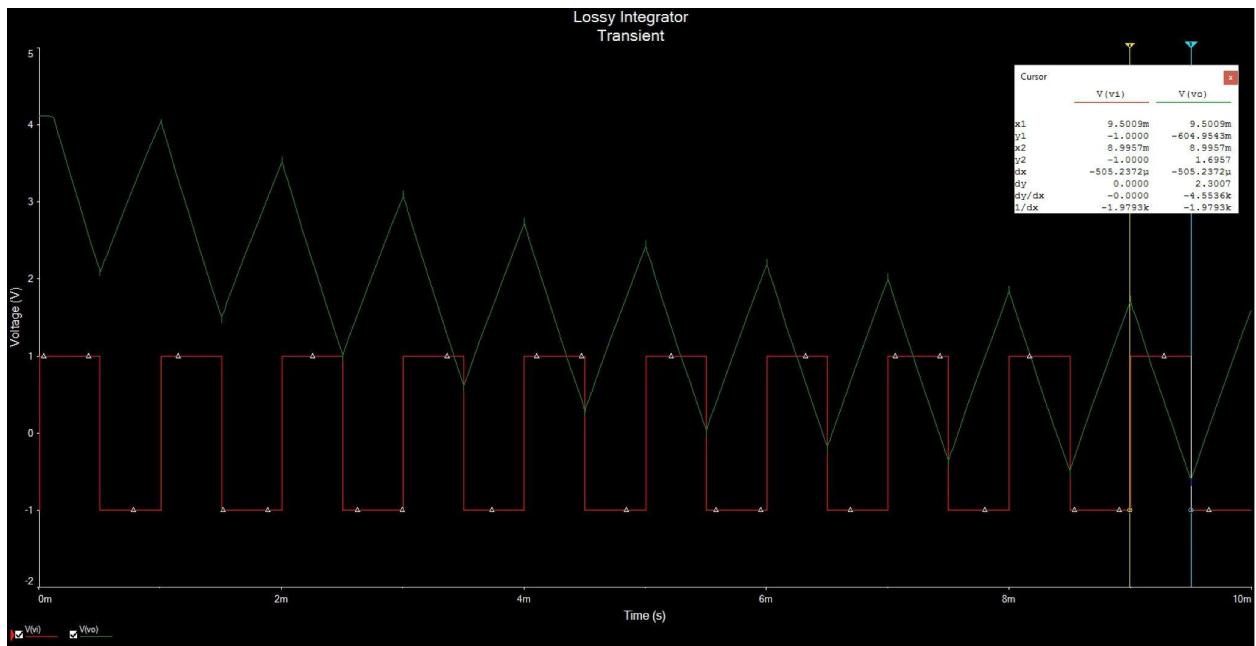


## Pseudo Differentiator


### Schematic

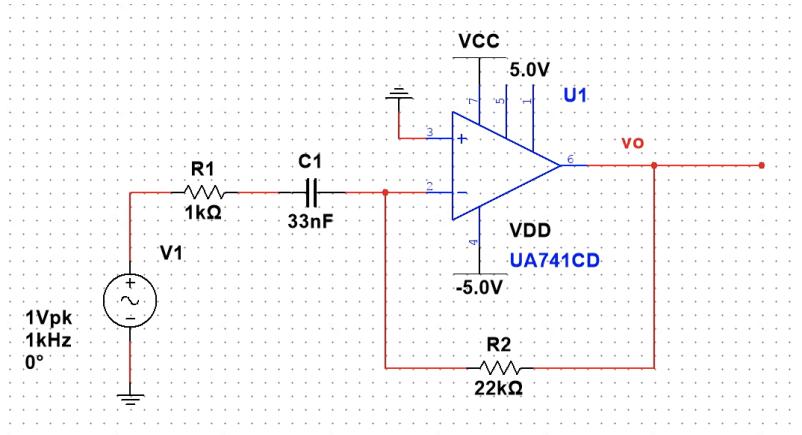


### Bode

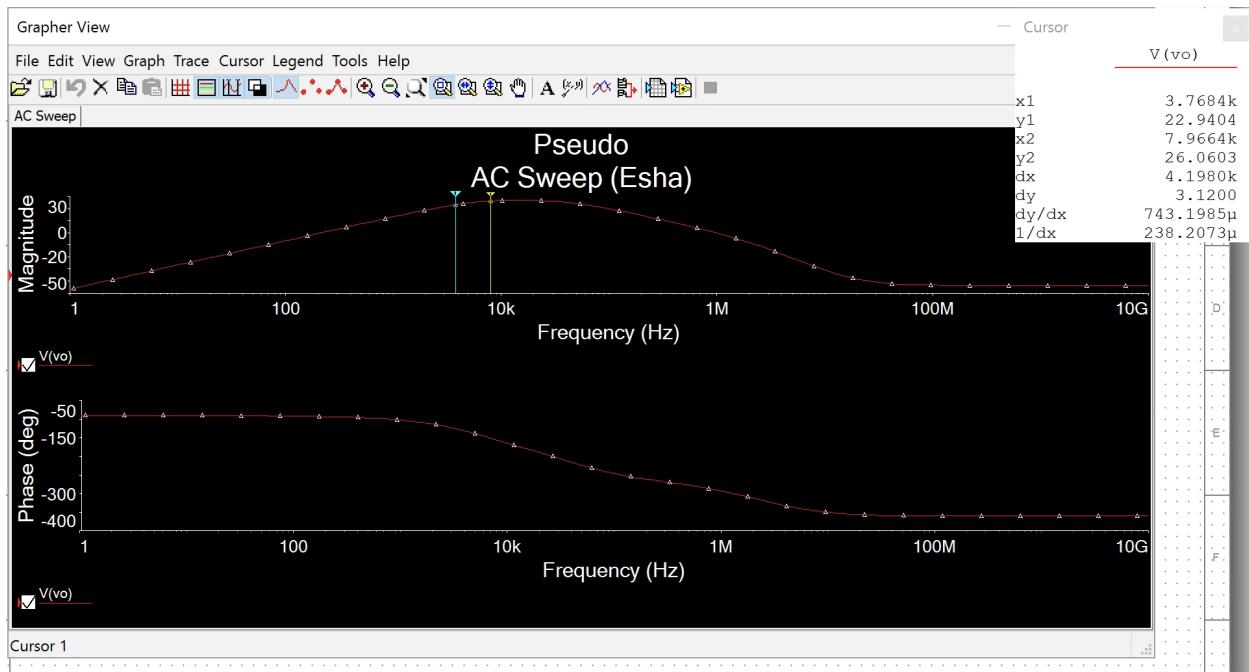

## Sin Transient

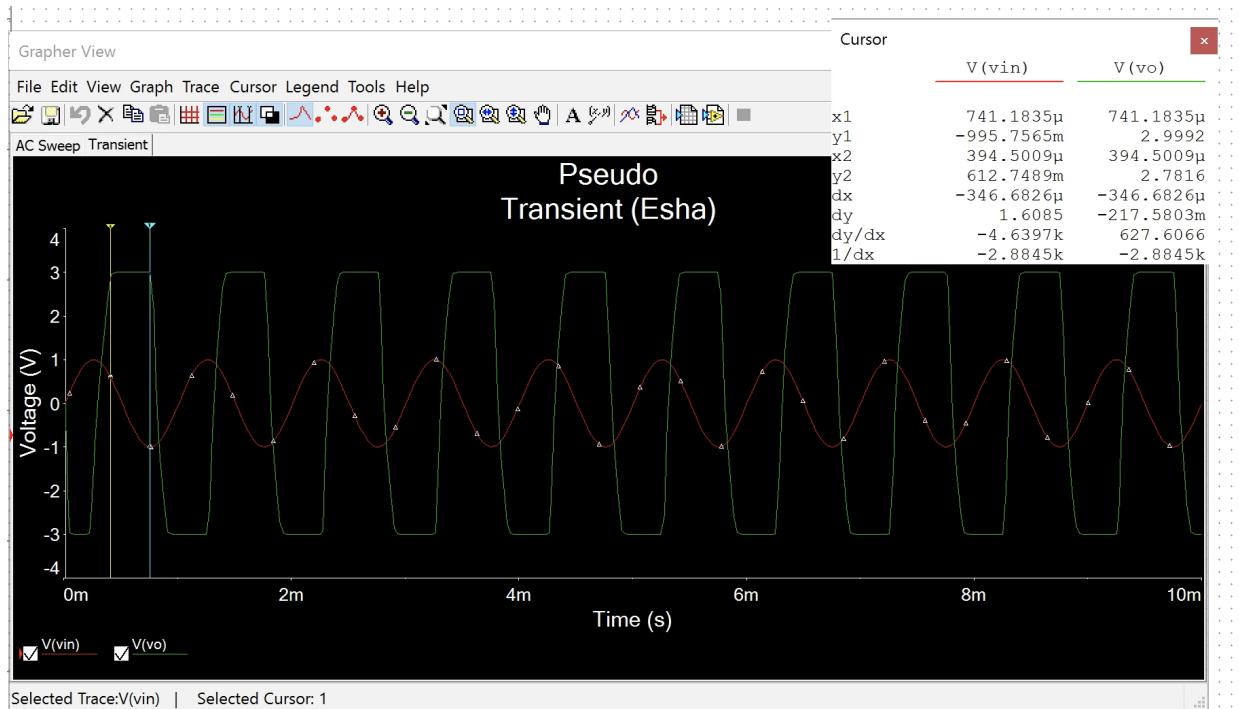


## Triangle Transient

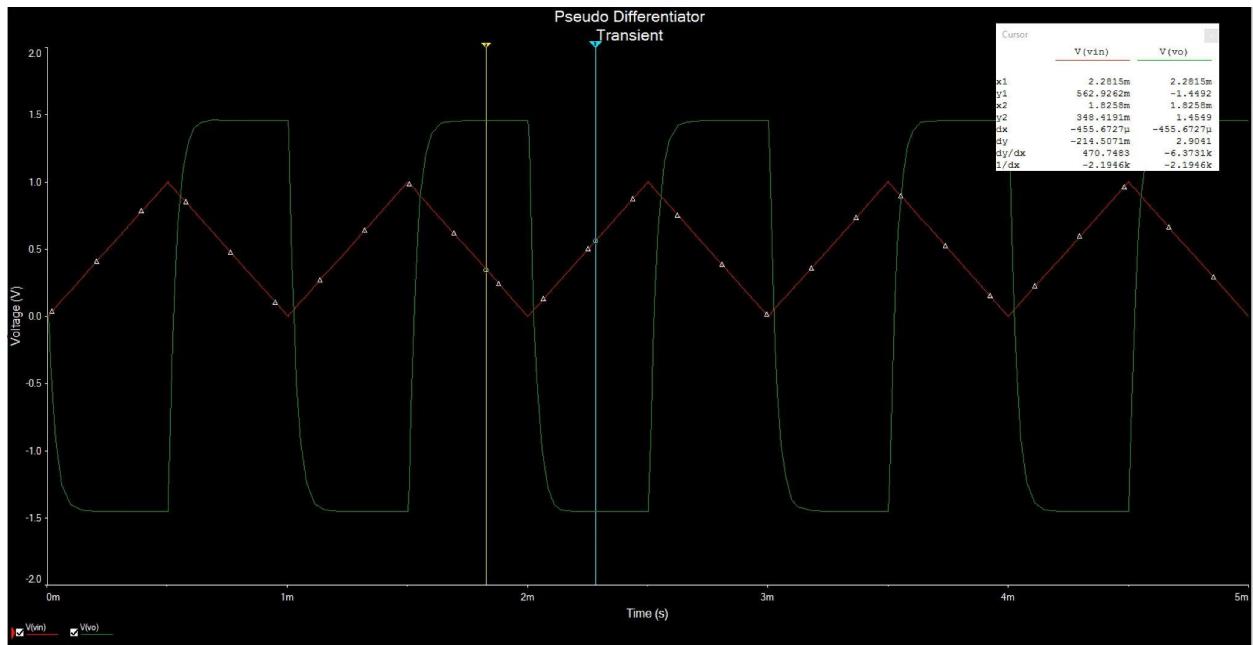


## Finite GBW Limitations

### Schematic

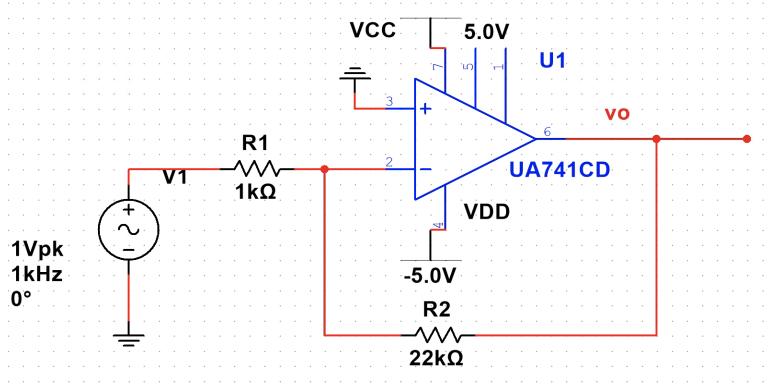


### Bode

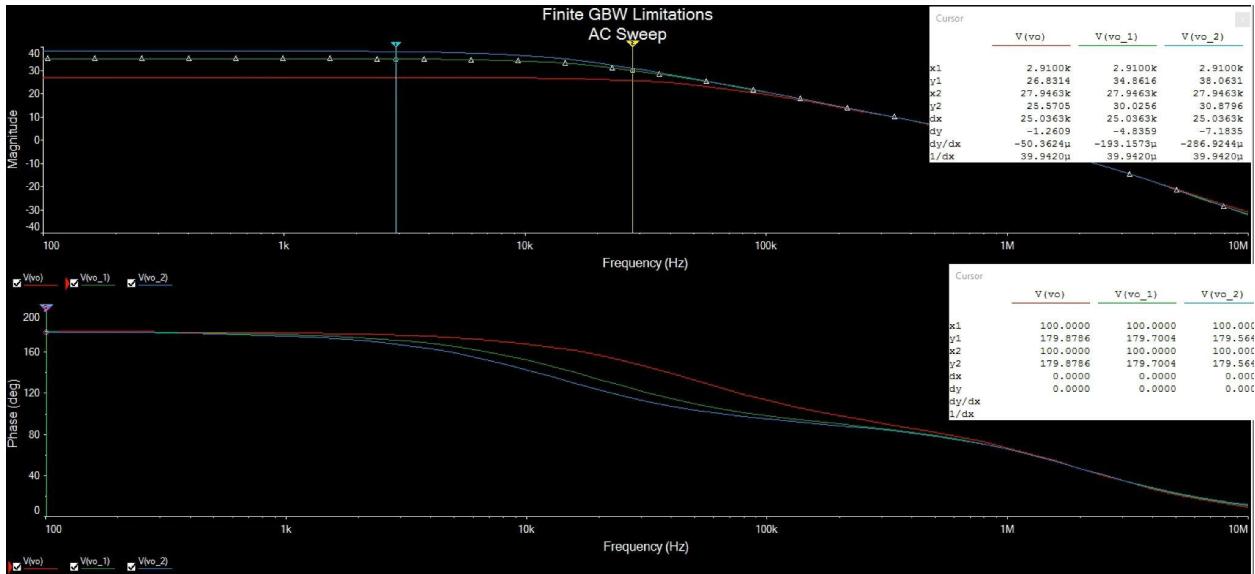


## Slew Rate Limitations


### Schematic

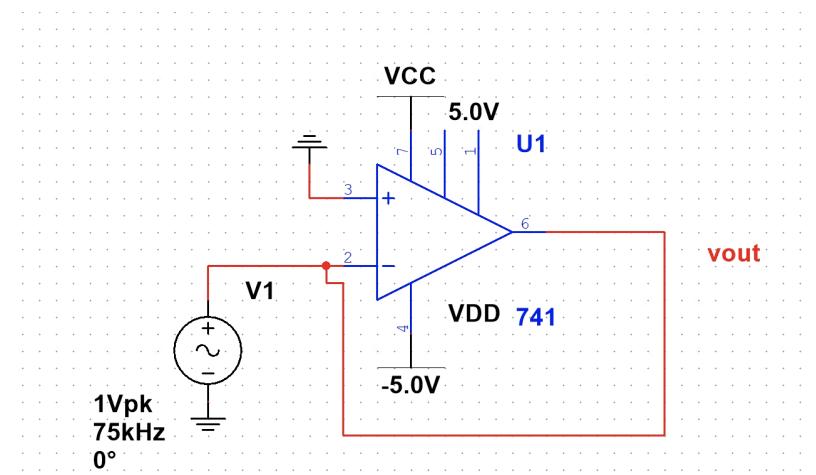


### Bode

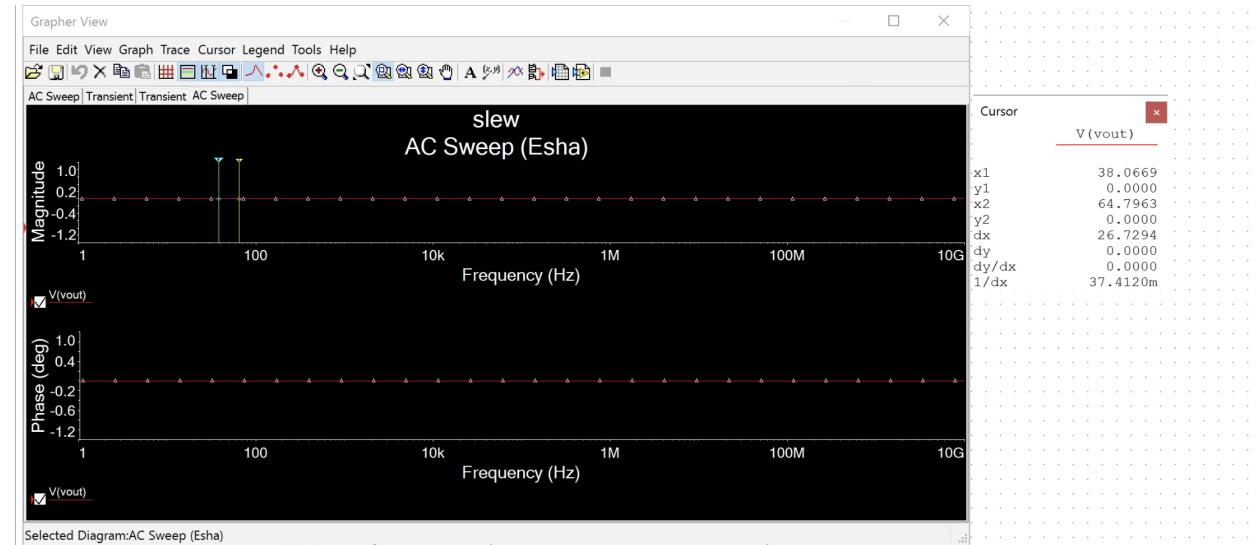


## Sin Transient 75K 1V

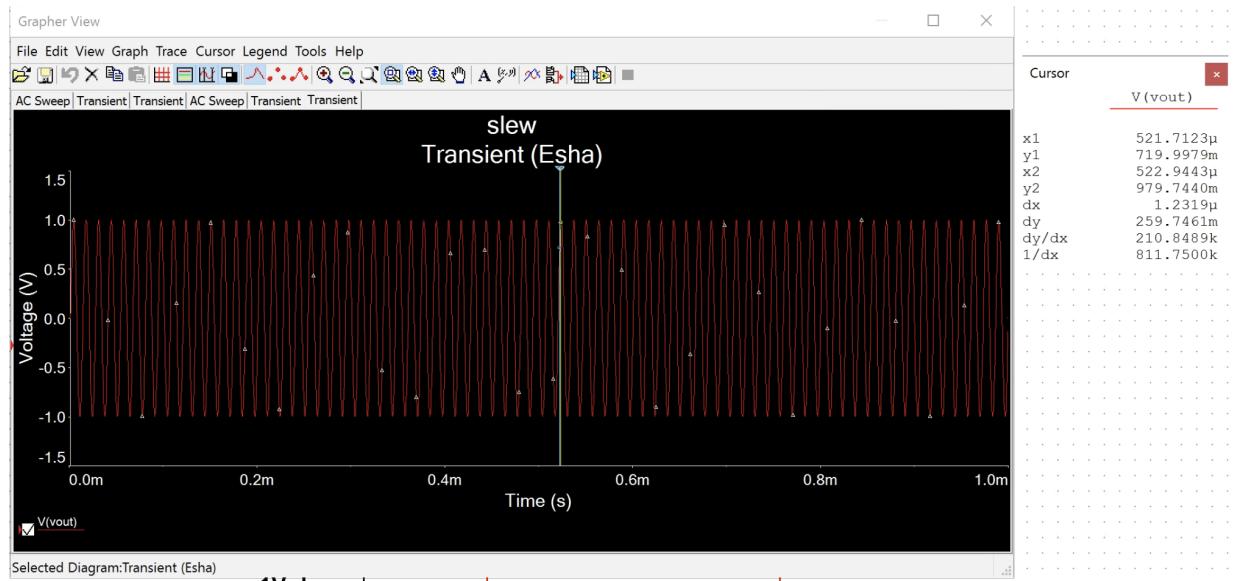


## Fourier 75K 1V

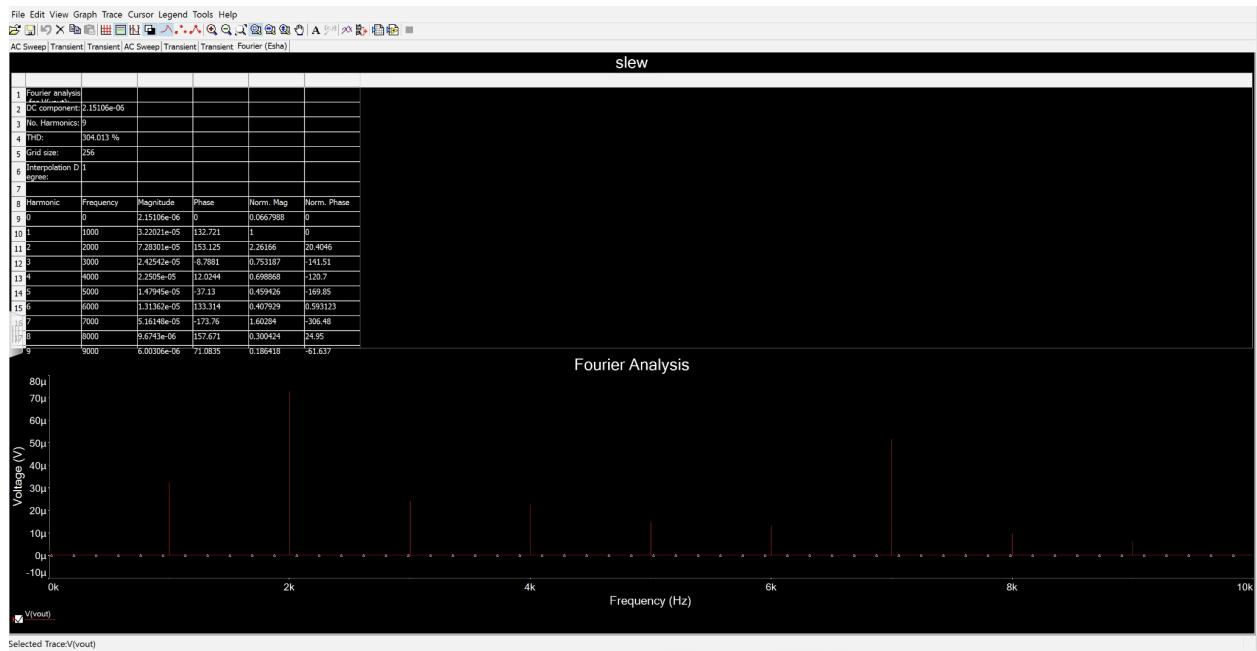


## Sin Transient 75K 2V

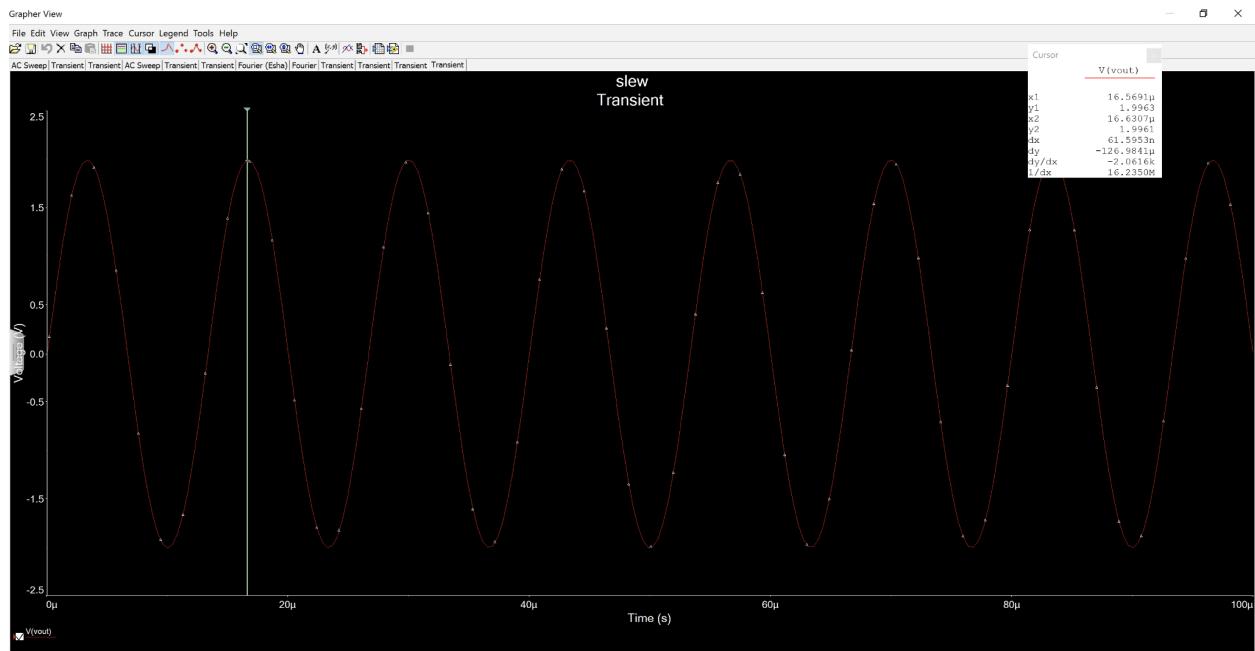


## Fourier 75K 2V

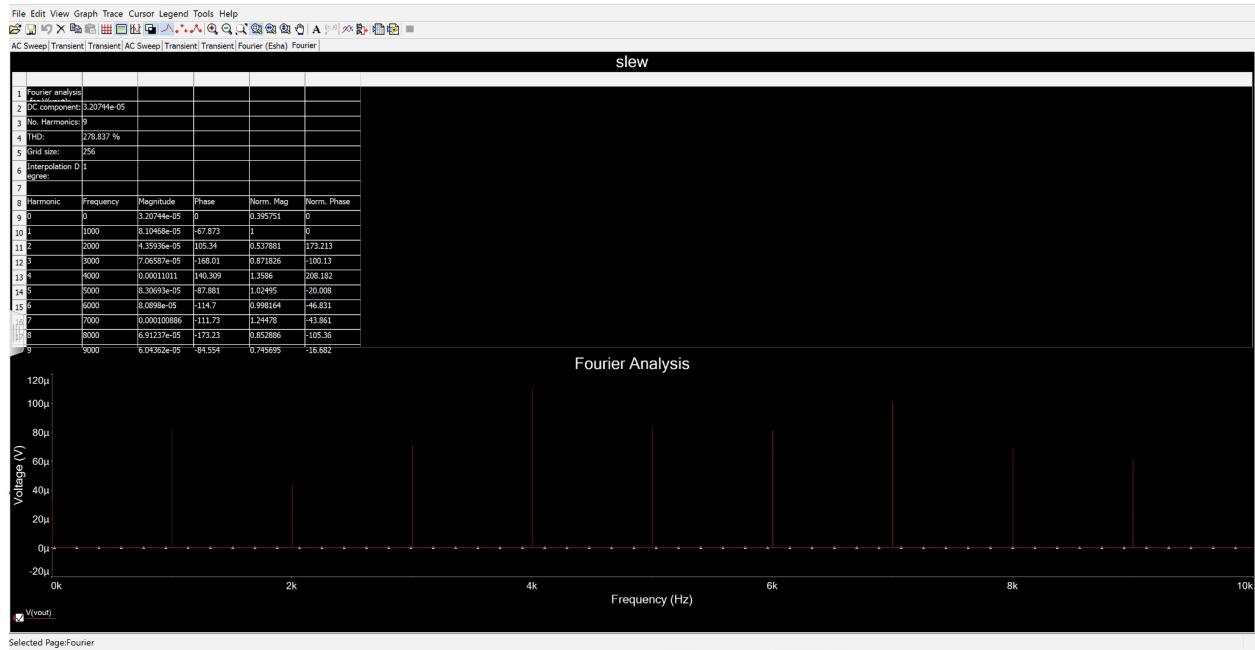

### *Sin Transient 150K 1V*

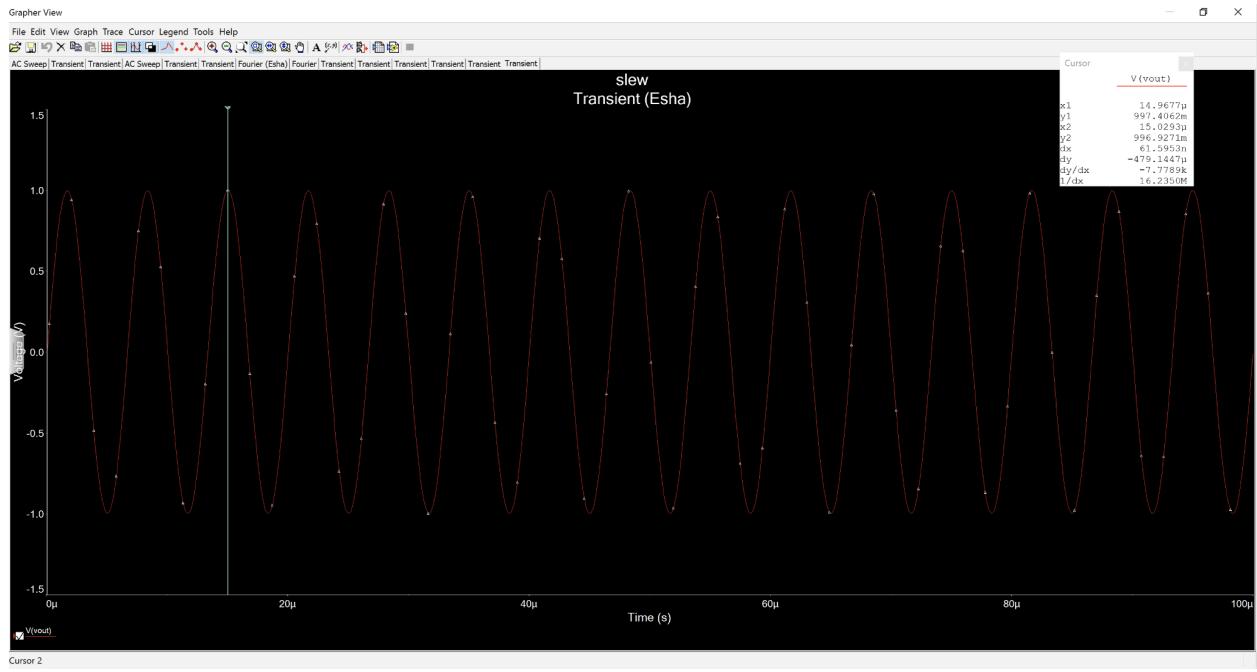


*Fourier 150K IV*

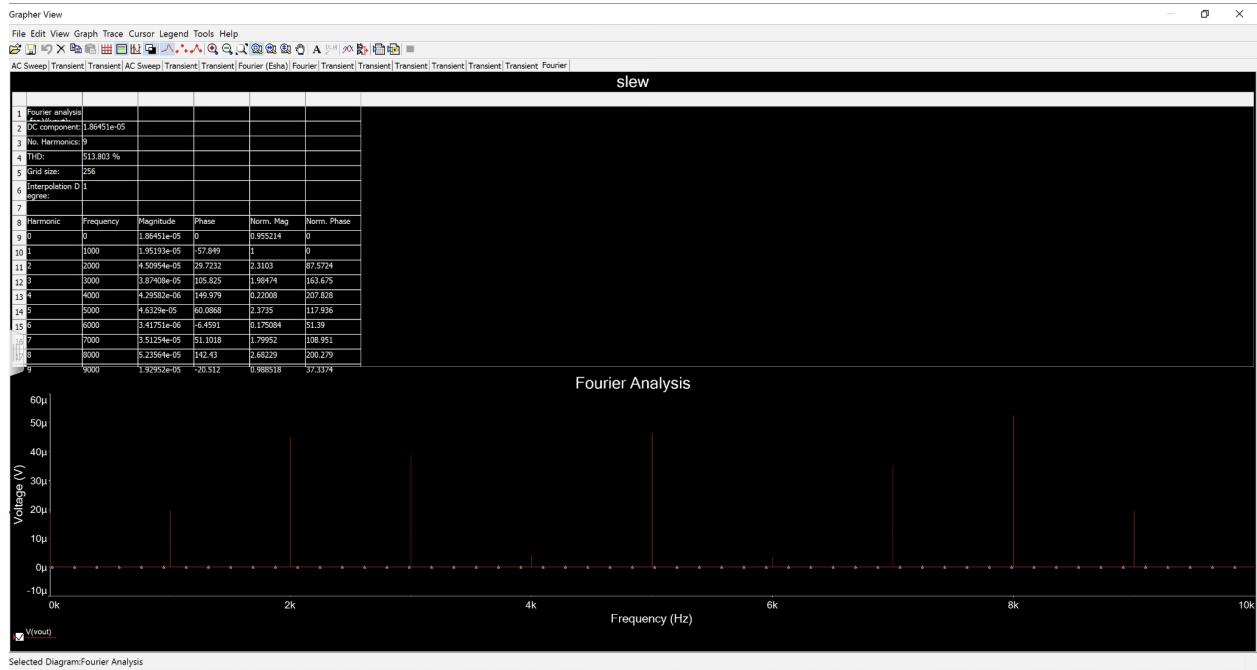


## Measurements

### Lossy Integrator


#### Bode

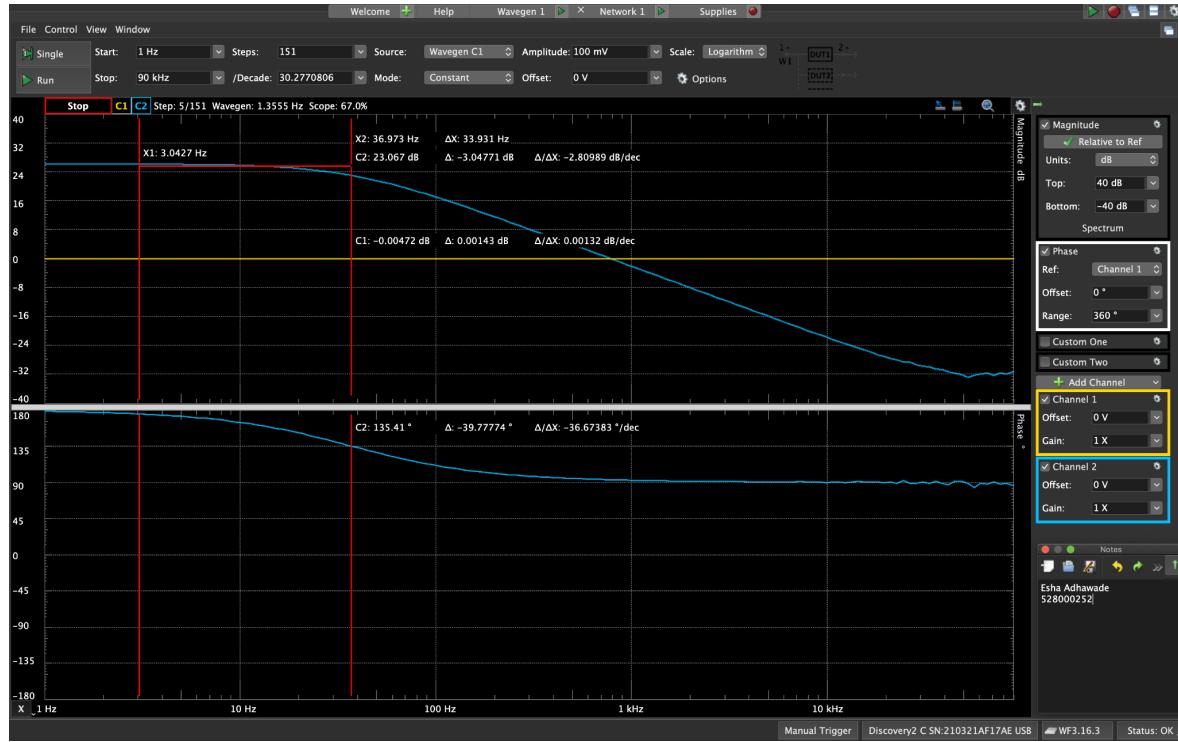


#### Sin Time Domain

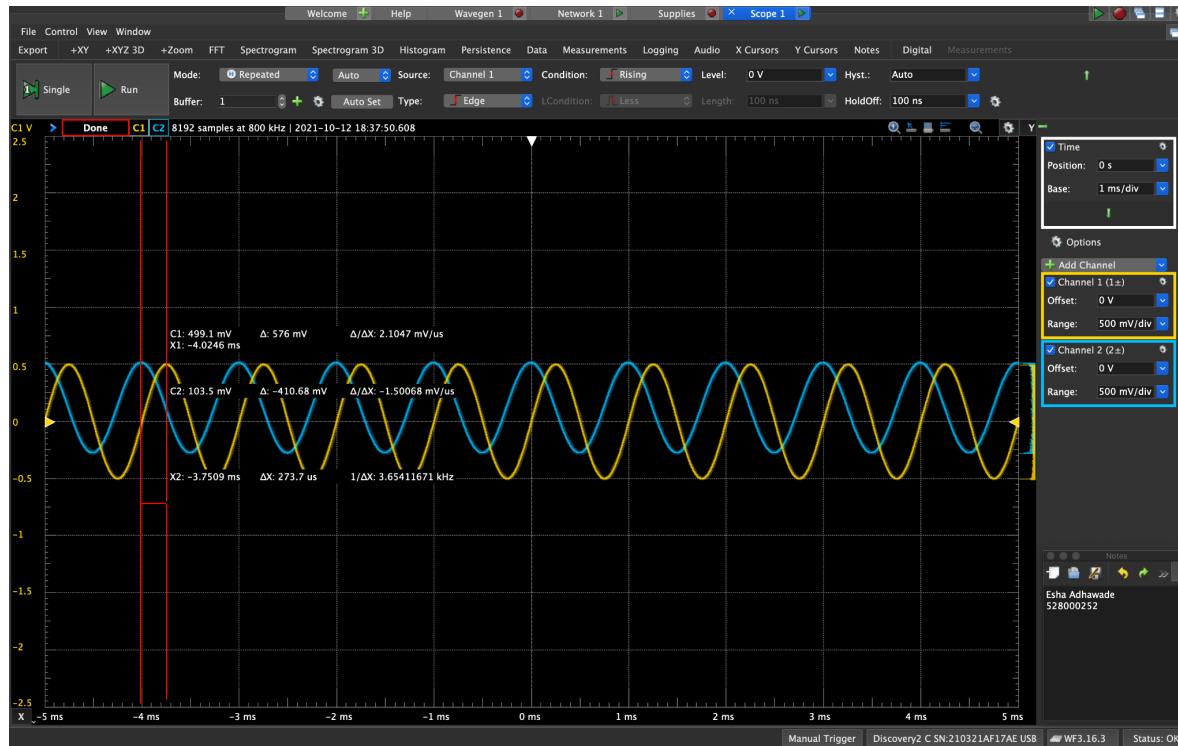

## Square Time Domain

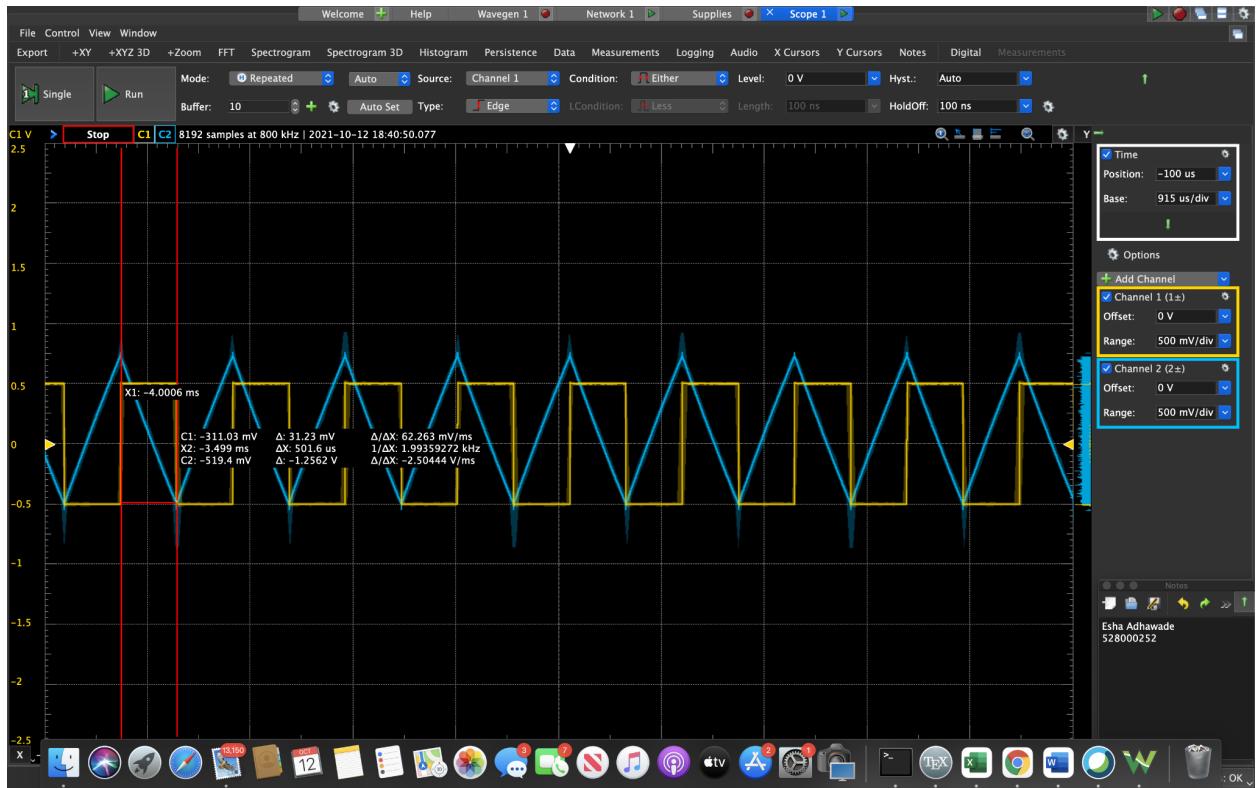


Without R2 (without R2 C2 moves up)

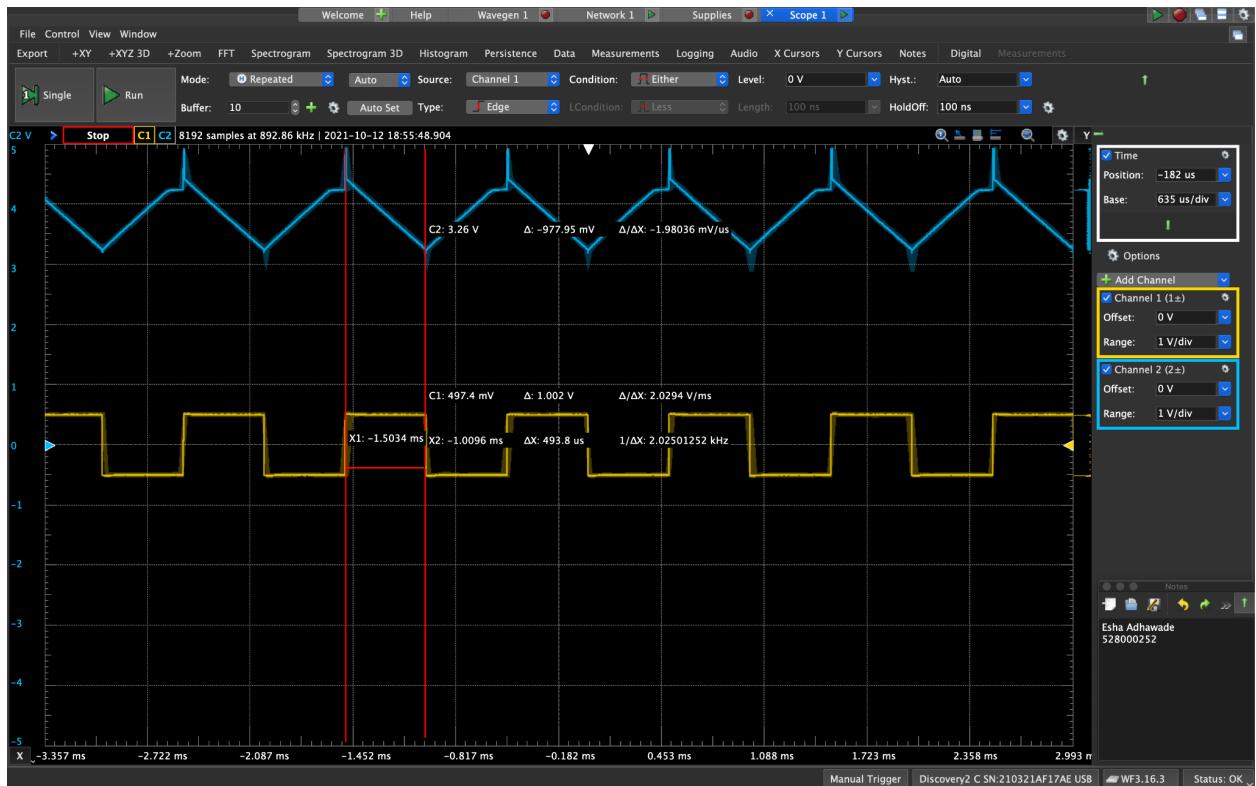


## Pseudo Differentiator


### Bode

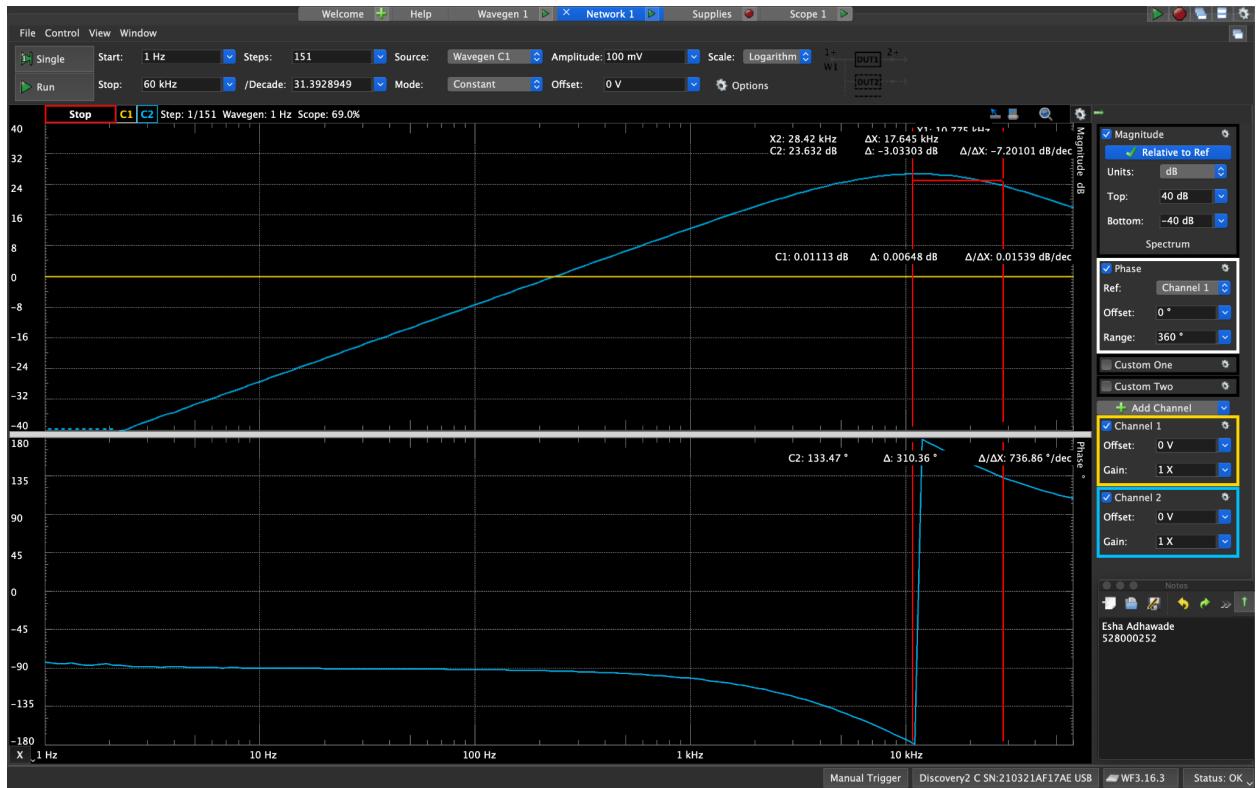

### Sin Time Domain

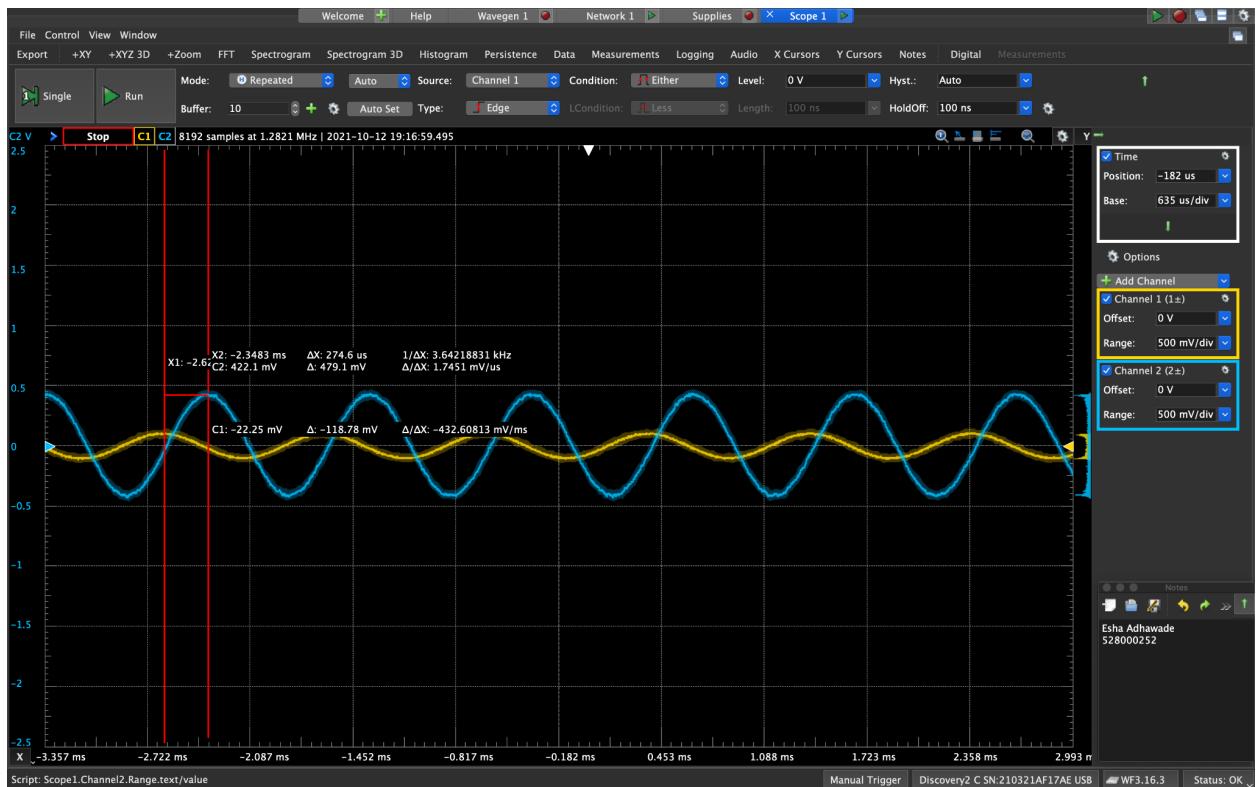


## Triangle Time Domain

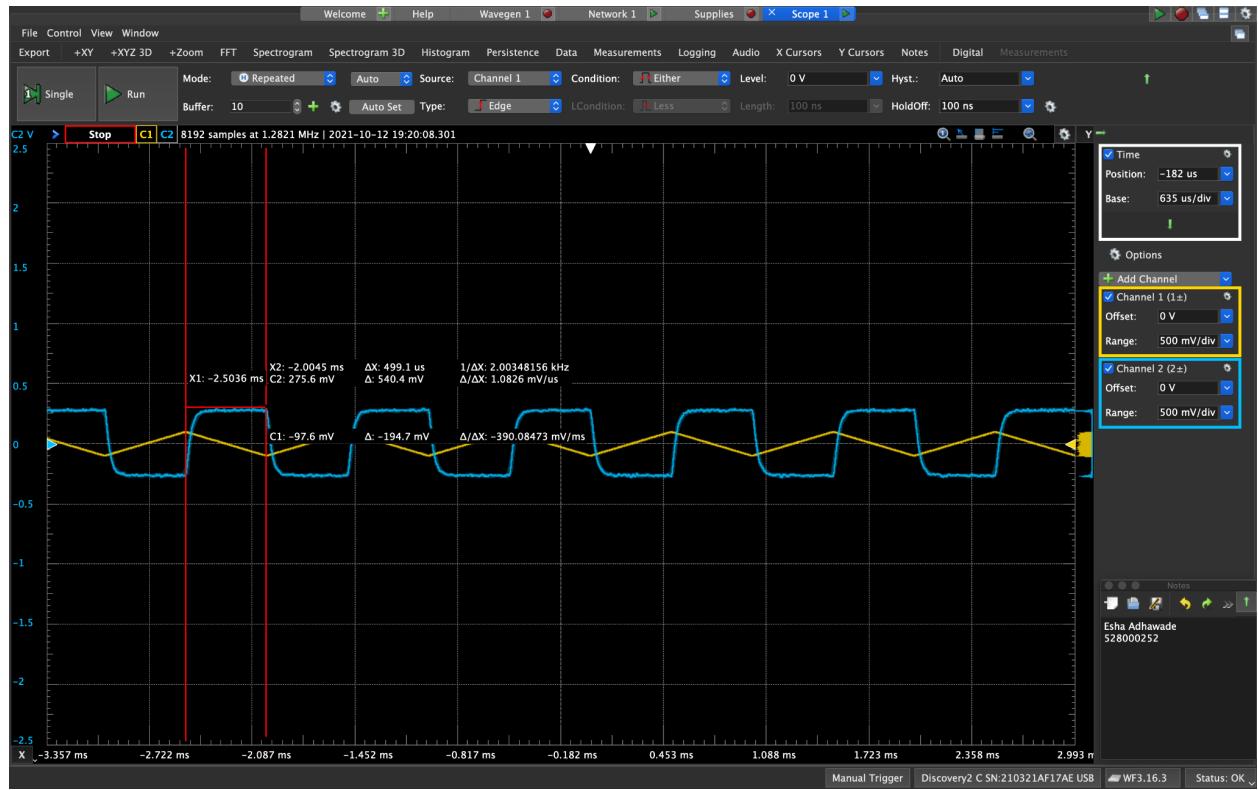


## Finite GBW Limitations


Bode for 23

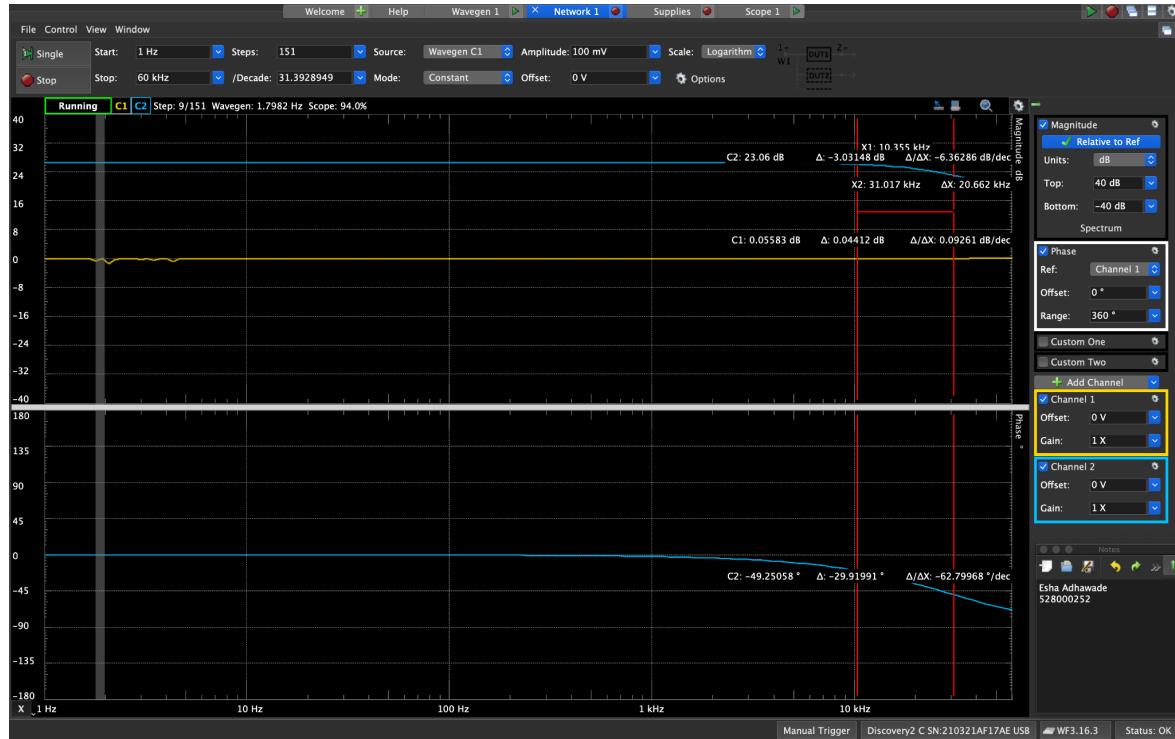

## Bode for 57

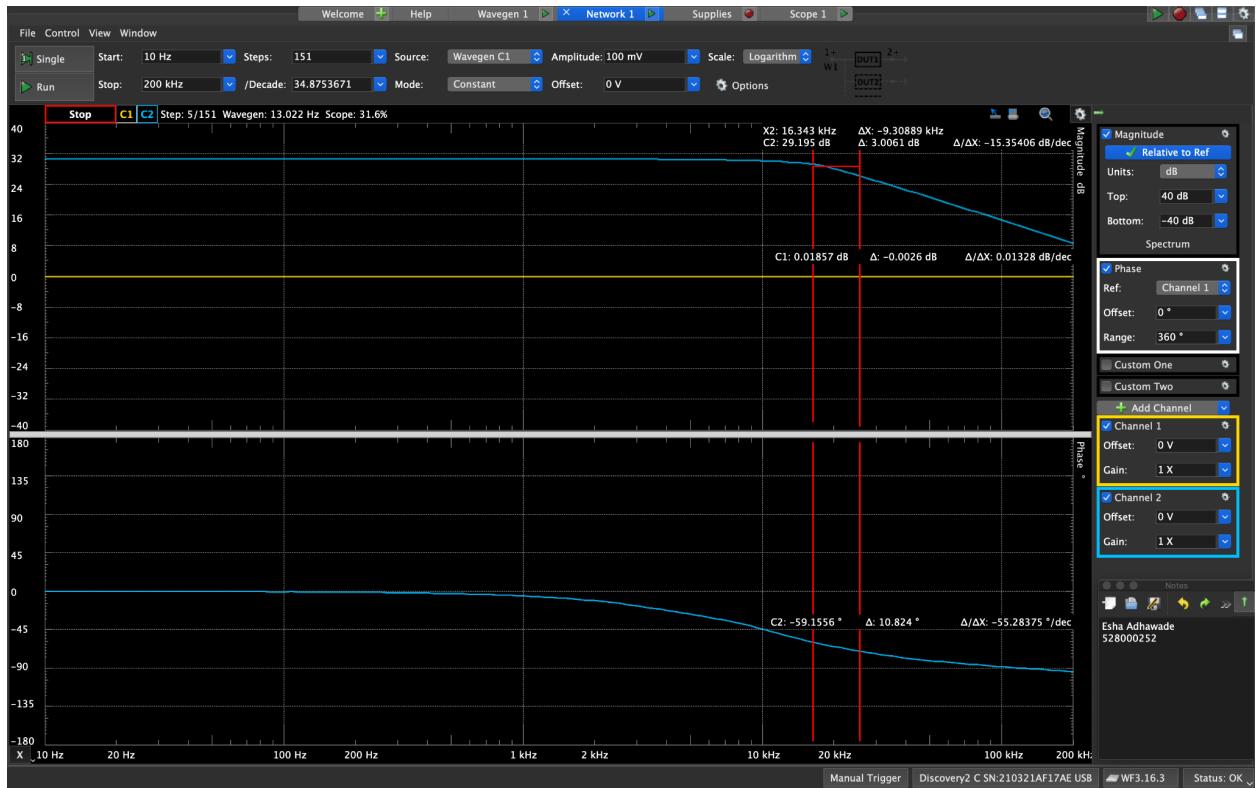


## Bode for 83

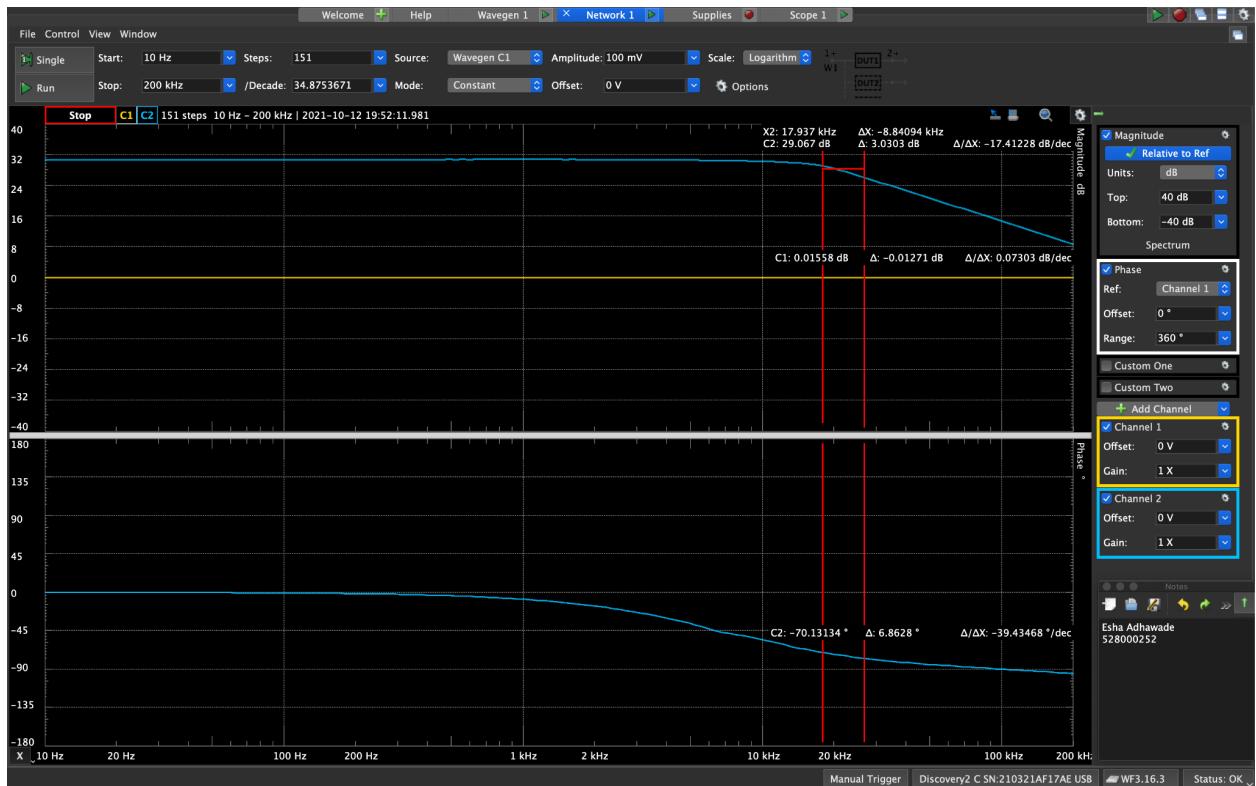


## Slew Rate Limitations


*Bode*

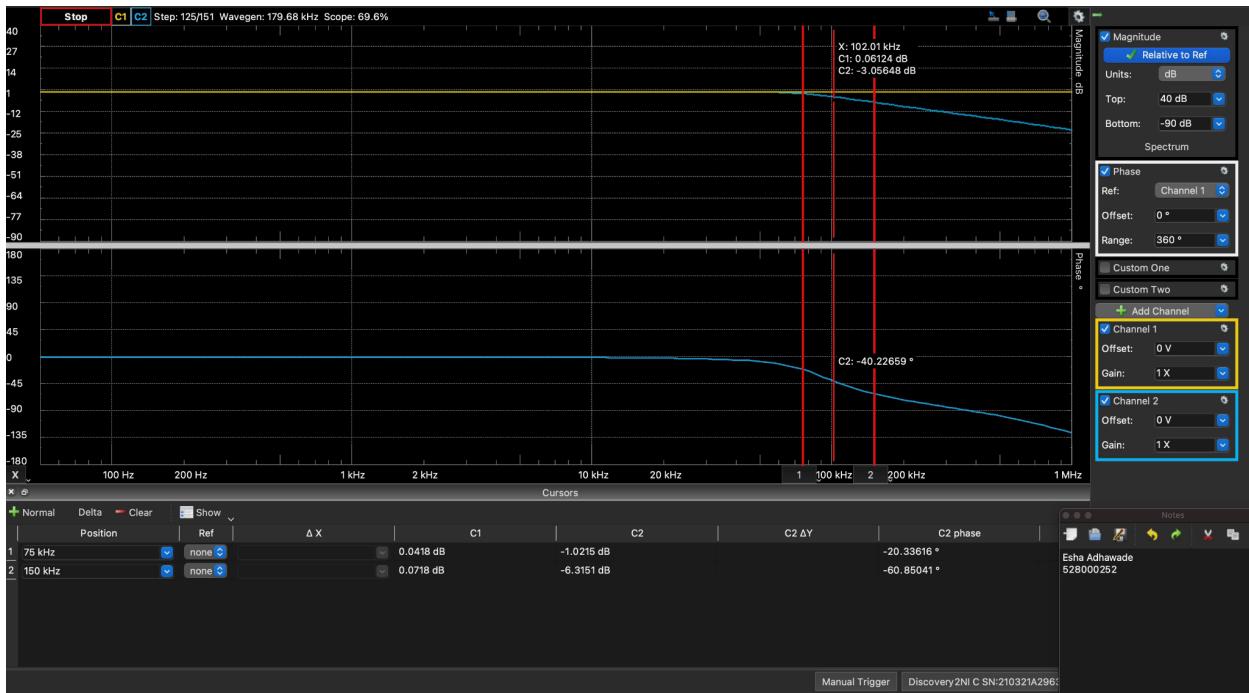


*Time Domain 75k 1V*

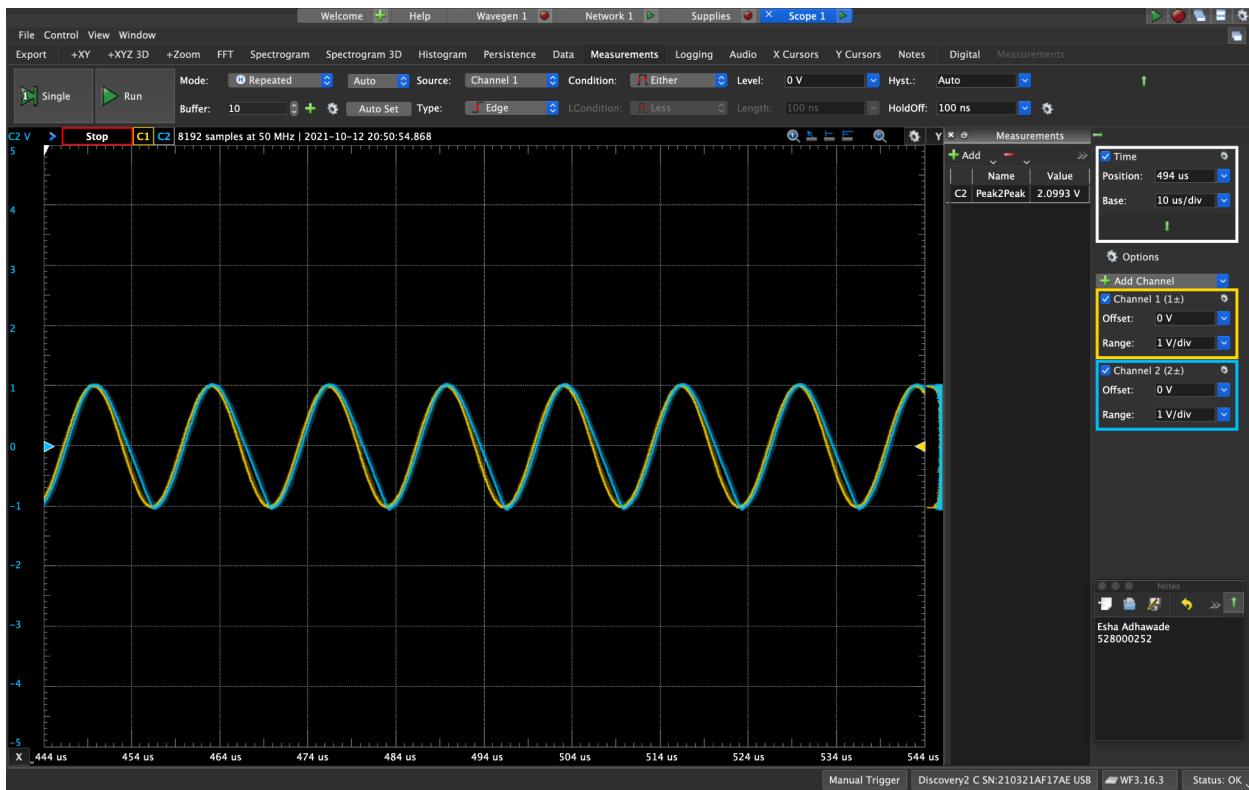


## THD 75k 1V

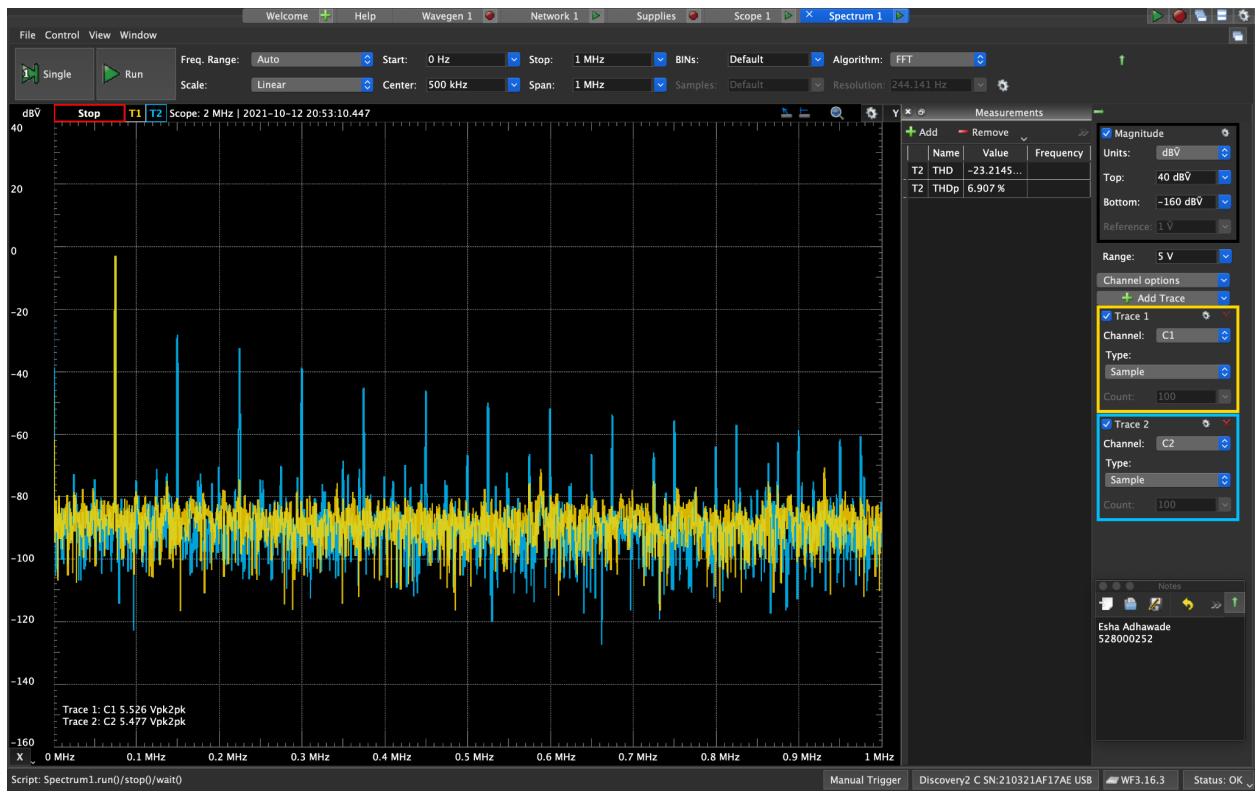


## Time Domain 75k 2V

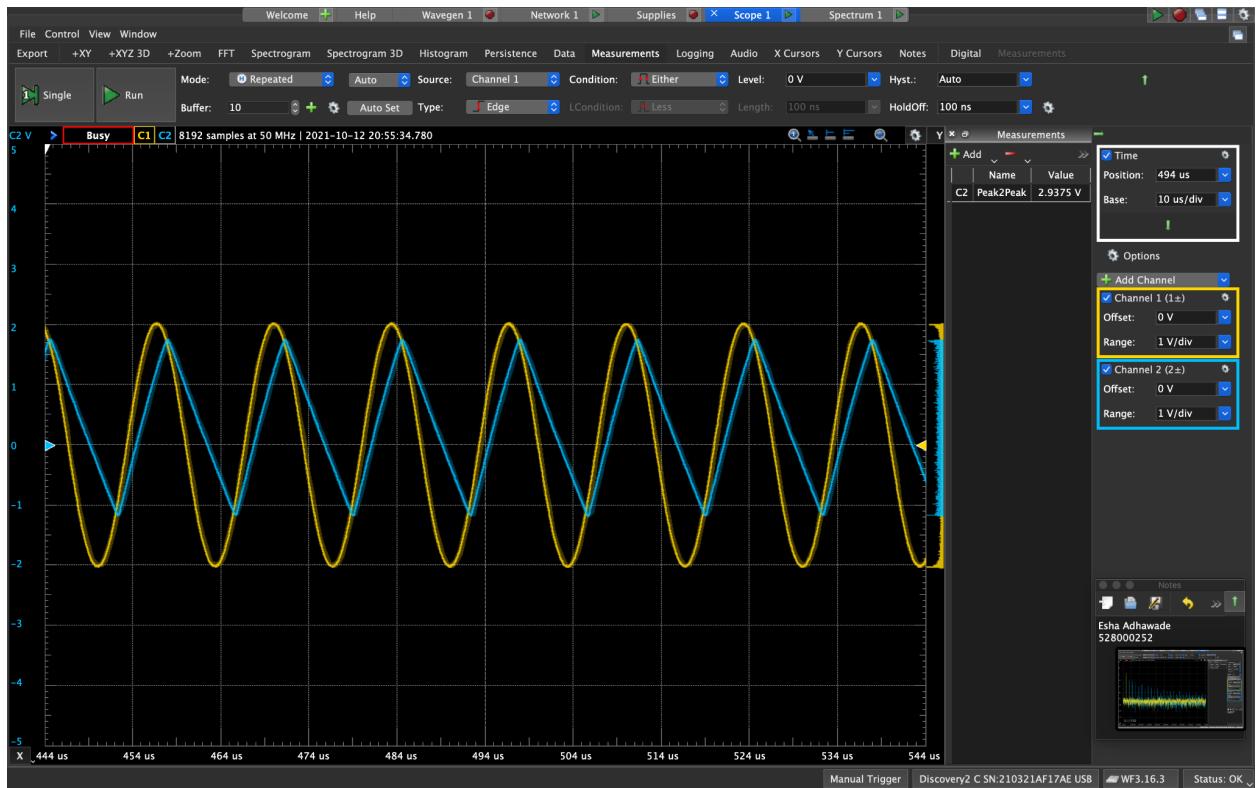


## THD 75k 2V

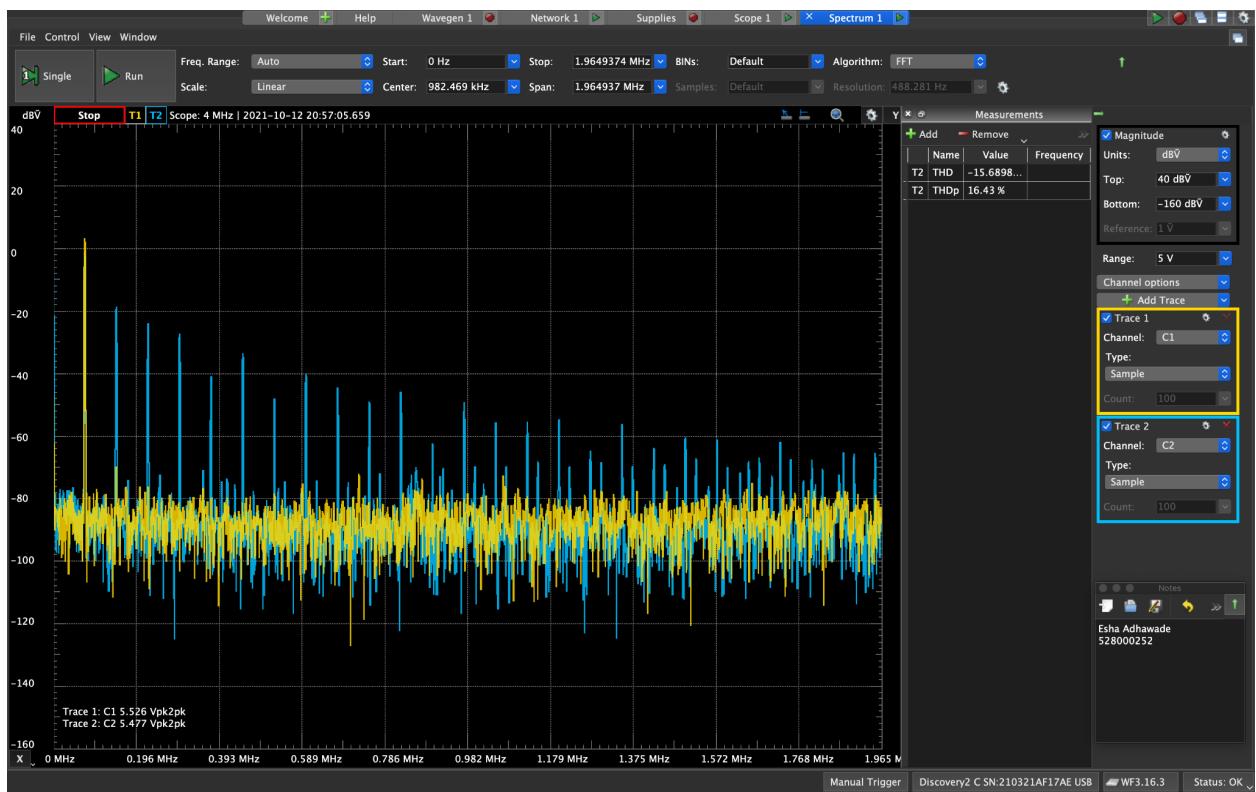

## Time Domain 150k 1V

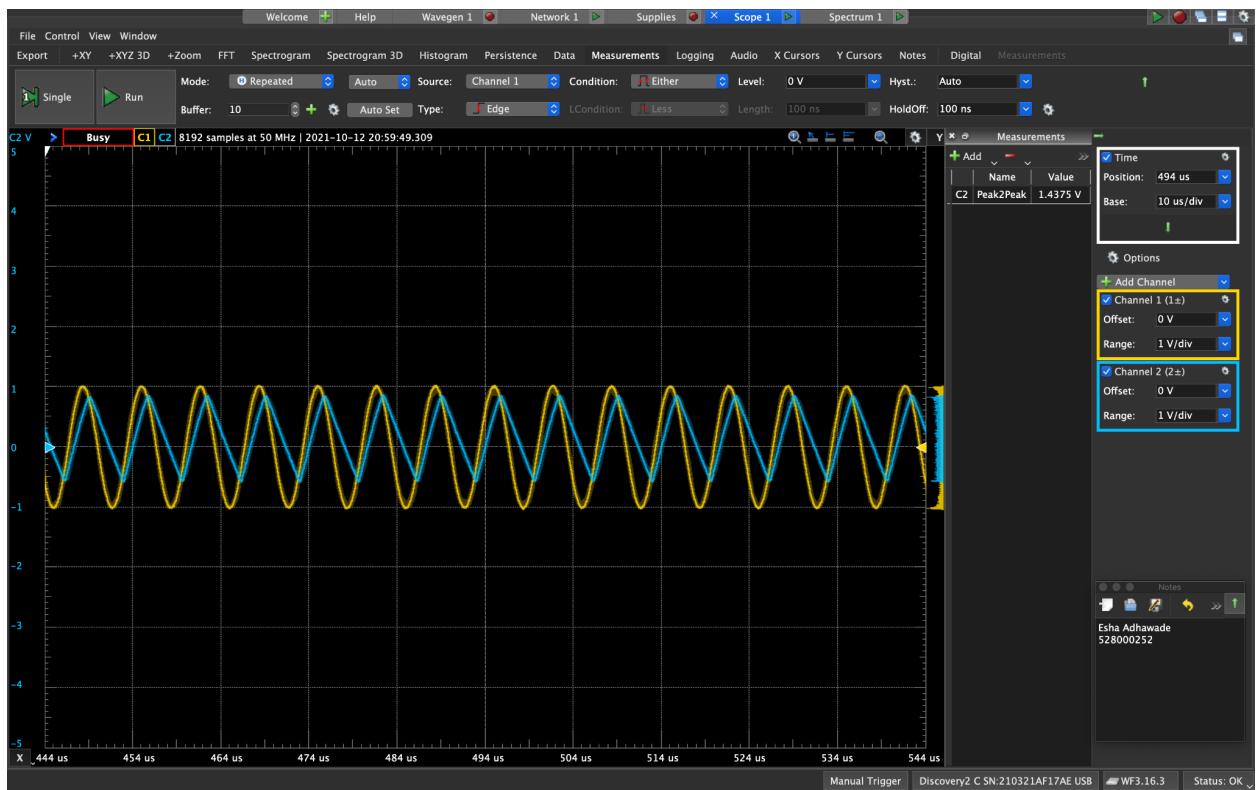

## THD 150k 1V

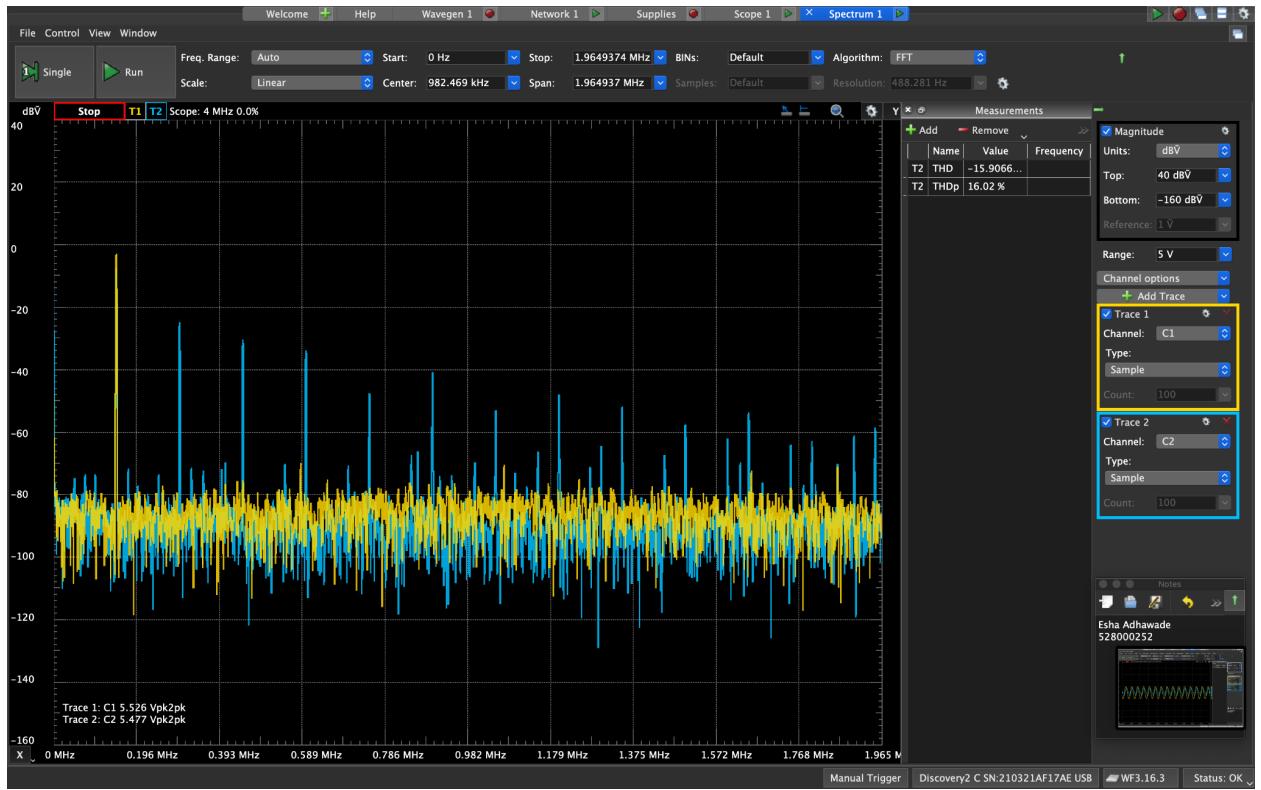

## Data Tables

### Lossy Integrator

	Low Frequency Gain	3dB Frequency	Vout Magnitude	Vout Phase
<b>Calculations Lossy Integrator</b>	22	206.61	0.3615	-88.11
<b>Simulations Lossy Integrator</b>	-8.36051	18.264	0.358	-87.042
<b>Measurements Lossy Integrator</b>	-3.26	36.793	0.468	-98.53

### Pseudo Differentiator

	Low Frequency Gain	3dB Frequency	Vout Magnitude	Vout Phase

<b>Calculations Pseudo Differentiator</b>	-22	1317.5	0.0936	11.89
<b>Simulations Pseudo Differentiator</b>	4.901	3.7684k	2.7816	124.81
<b>Measurements Pseudo Differentiator</b>	-18.97	10.775k	0.4221	98.856

### Finite GBW Limitations

	<b>3dB Frequency</b>
<b>Calculations Finite GBW Limitations (23)</b>	---
<b>Simulations Finite GBW Limitations (23)</b>	29.964k
<b>Measurements Finite GBW Limitations (23)</b>	31.017k
<b>Calculations Finite GBW Limitations (57)</b>	---
<b>Simulations Finite GBW Limitations (57)</b>	18.234k
<b>Measurements Finite GBW Limitations (57)</b>	16.343k
<b>Calculations Finite GBW Limitations (83)</b>	---
<b>Simulations Finite GBW Limitations (83)</b>	15.672k

<b>Measurements</b>	17.937k
<b>Finite GBW</b>	
<b>Limitations (83)</b>	

### Slew Rate Limitations

There is no transfer function for slew rate, so there cannot exist a 3dB frequency. For magnitude and phase response between 75k and 150k will be the same.

### Discussion

For lab 5, students learned about the different configurations for op amps and their non-idealities. Most of the values between the simulations and measurements were pretty consistent for the circuits. If there were any minor differences, that's probably because of component differences, old breadboards, or loose wires. My simulation for lossy integrator, used VSS instead of VDD so my 3db is different from measurements.